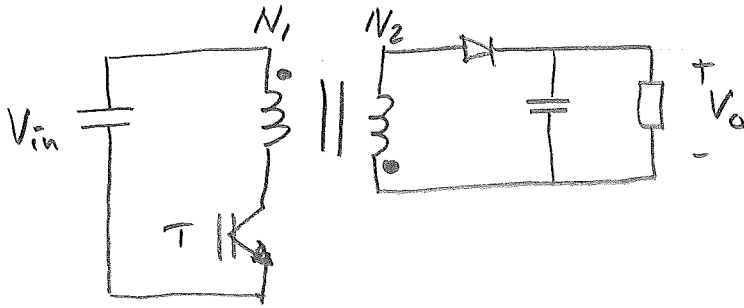


BWW Uppg. 17.13



$$T = \text{ON: } V_{in} - L_m' \frac{di_m'}{dt} = 0 \Rightarrow \Delta i_m' = \frac{V_{in}}{L_m'} \cdot t_T$$

$$T = \text{OFF: } -L_m'' \frac{di_m''}{dt} - V_o = 0 \Rightarrow |\Delta i_m''| = \frac{V_o}{L_m''} \cdot t_D$$

↑
negativ derivata

Överför till primärsidan:

$$\Delta i_m' \cdot \frac{N_1}{N_2} = \frac{V_o}{L_m' \left(\frac{N_2}{N_1}\right)^2} \cdot t_D \Rightarrow$$

$$\Delta i_m' = \frac{V_o}{L_m' \frac{N_2}{N_1}} \cdot t_D = \frac{V_o}{L_m'} \cdot \frac{N_1}{N_2} \cdot t_D$$

LIKHET:

$$\frac{V_{in}}{L_m'} \cdot t_T = \frac{V_o}{L_m'} \cdot \frac{N_1}{N_2} \cdot t_D$$

$$V_{in} \cdot t_T = V_o \cdot \frac{N_1}{N_2} \cdot t_D$$

Eftersom $\Delta i = I_o/2$ kan man anta avsluten drift. Alltså $t_D = T - t_T$

$$V_{in} \cdot \delta = V_o \cdot \frac{N_1}{N_2} (1 - \delta) \cdot \delta$$

$$\frac{N_1}{N_2} = \frac{V_{in} \delta}{V_o (1 - \delta)} \quad \left. \begin{array}{l} V_{in} = 50 \\ V_o = 25 \\ \delta = 0,4 \end{array} \right\} \Rightarrow \frac{N_1}{N_2} = \frac{50 \cdot 0,4}{25(1 - 0,4)} = \frac{4}{3}$$

$$\Delta i = \frac{I_o}{2} = \frac{25/5}{2} = 2,5 \text{ A}$$

Räkna på sekundärsidan:

$$L_m'' = \frac{V_o}{\Delta i_m'' / \Delta t} = \frac{V_o}{\Delta i_m''} \cdot t_D = \frac{25}{2,5} \cdot 0,6 \cdot \frac{1}{20 \text{ kHz}} = 0,3 \text{ mH}$$

På primärsidan: $L_m' = \left(\frac{N_1}{N_2}\right)^2 \cdot L_m'' = \left(\frac{4}{3}\right)^2 \cdot 0,3 \text{ mH} = 0,533 \text{ mH}$