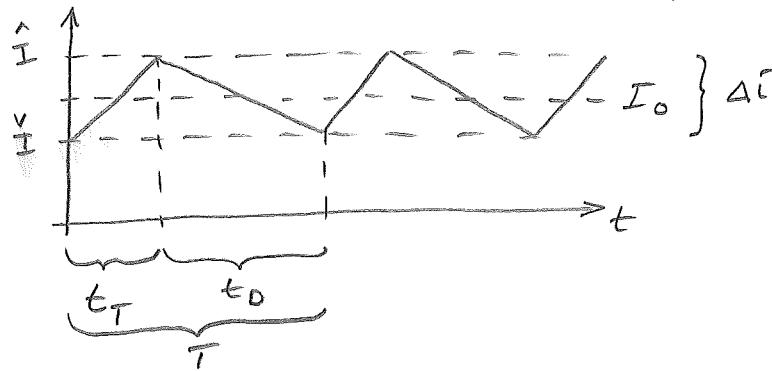


# Uppgift 17.4

I



ANSLUTEN DRIFT (ccm)  
STRÖMMEN NÄR ALDRIG  
NOLL  $\Rightarrow t_T + t_D = T$

$$I_{Rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \frac{1}{T} \left( \int_0^{t_T} i^2(t) dt + \int_{t_T}^{t_T+t_D} i^2(t) dt \right)$$

$$I_{Rms}^2 = \frac{1}{T} \left( \int_0^{t_T} \left( \hat{I} + \frac{\Delta i}{t_T} \cdot t \right)^2 dt + \int_{t_T}^{t_D} \left( \hat{I} - \frac{\Delta i}{t_D} \cdot t \right)^2 dt \right) =$$

$$= \frac{1}{T} \left( \int_0^{t_T} \hat{I}^2 + 2 \hat{I} \frac{\Delta i}{t_T} \cdot t + \left( \frac{\Delta i}{t_T} \right)^2 t^2 dt + \right.$$

$$\left. + \int_{t_T}^{t_D} \hat{I}^2 - 2 \hat{I} \frac{\Delta i}{t_D} \cdot t + \left( \frac{\Delta i}{t_D} \right)^2 t^2 dt \right) =$$

$$= \frac{1}{T} \left( \left[ \hat{I}^2 t + \hat{I} \frac{\Delta i}{t_T} t^2 + \left( \frac{\Delta i}{t_T} \right)^2 \cdot \frac{t^3}{3} \right]_0^{t_T} + \right.$$

$$\left. + \left[ \hat{I}^2 t - \hat{I} \frac{\Delta i}{t_D} t^2 + \frac{\Delta i}{t_D} \cdot \frac{t^3}{3} \right]_0^{t_D} \right) =$$

$$= \frac{1}{T} \left( \hat{I}^2 t_T + \hat{I} \Delta i t_T + \frac{\Delta i^2}{3} t_T^2 + \hat{I}^2 t_D - \hat{I} \Delta i t_D + \frac{\Delta i^2}{3} t_D^2 \right) =$$

$$= \frac{1}{T} \left( \left( I_0 - \frac{\Delta i}{2} \right)^2 t_T + \left( I_0 - \frac{\Delta i}{2} \right) \Delta i t_T + \frac{\Delta i^2}{3} t_T^2 + \right.$$

$$\left. + \left( I_0 + \frac{\Delta i}{2} \right)^2 t_D - \left( I_0 + \frac{\Delta i}{2} \right) \Delta i t_D + \frac{\Delta i^2}{3} t_D^2 \right) =$$

$$= \frac{1}{T} \left( I_0^2 t_T - I_0 \Delta i t_T + \frac{\Delta i^2}{4} t_T^2 + I_0 \Delta i t_T - \frac{\Delta i^2}{2} t_T + \frac{\Delta i^2}{3} t_D + \right.$$

$$\left. + I_0^2 t_D + I_0 \Delta i t_D + \frac{\Delta i^2}{4} t_D - I_0 \Delta i t_D - \frac{\Delta i^2}{2} t_D + \frac{\Delta i^2}{3} t_D \right) =$$

17.4 forts.

$$= \frac{1}{T} \left( I_0^2 (t_r + t_D) + \frac{3-6+4}{12} \Delta i^2 (t_r + t_D) \right) =$$

$$= \frac{t_r + t_D}{T} \left( I_0^2 + \frac{1}{12} \Delta i^2 \right) = \{ \text{CCM} \Rightarrow t_r + t_D = T \}$$

$$= I_0^2 + \left( \frac{\Delta i}{2\sqrt{3}} \right)^2 \Rightarrow$$

$$I_{RMS} = \sqrt{I_0^2 + \left( \frac{\Delta i}{2\sqrt{3}} \right)^2} \quad \Rightarrow$$

$$I_{RMS} = \sqrt{I_{DC, AVG}^2 + I_{AC, RMS}^2} \quad \leftarrow \text{DENNA ÄR BRÅA ATT KUNNA!}$$

$$I_{AC, RMS} = \frac{\Delta i}{2\sqrt{3}}$$