







Grid Connected Power Electronics

L11 - Static VAr compensation

Acronyms

- **APF – Active Power Filter**
- **UPFC – Unified Power Flow Controller**
- **SVC – Static Var Converter**
- **HVDC – High Voltage Direct Current**
- ...

All made to improve "Power Quality"

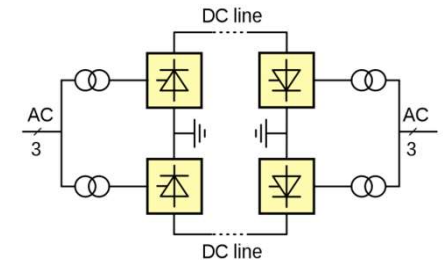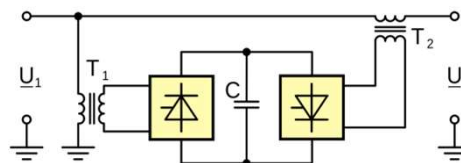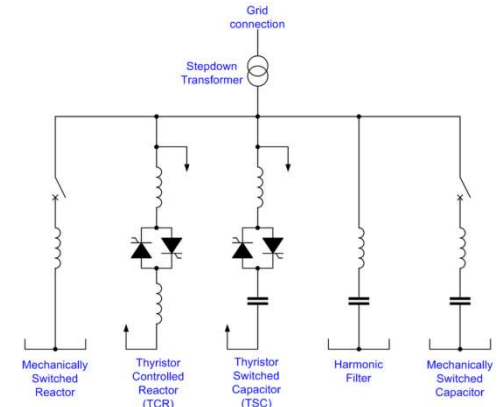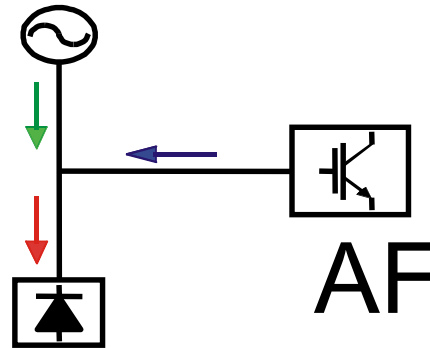



Non ideal loads


- are loads that:
 - *are non-resistive -> consume reactive power*
 - *vary with time or phase -> consume harmonic current components.*
 - *are different in different phases -> consume negative sequence currents*




Ways to improve the loads

- **Self improvement**
 - *Solutions that draw as “ideal” current as possible from the grid*
- **Compensation**
 - *A parallel unit is used to counteract the non ideal currents drawn by the main load*

Load model

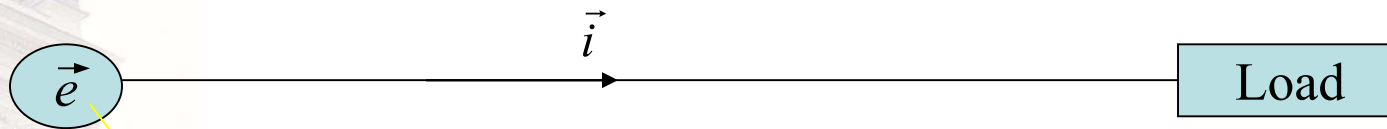
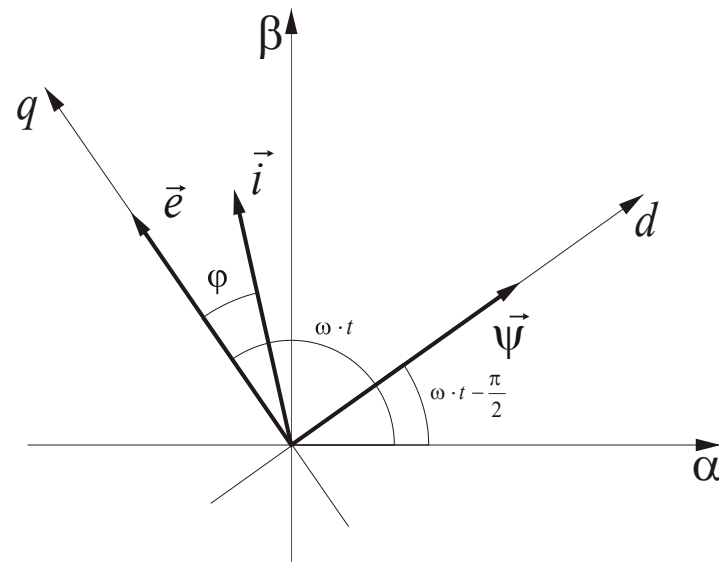
$$\vec{\psi} = \int_0^t \vec{e} \cdot dt = \int_0^t E \cdot e^{j\omega \cdot t} dt = \frac{\vec{e}}{j \cdot \omega} = \frac{E}{\omega} e^{j(\omega \cdot t - \frac{\pi}{2})}$$




Reactive power

- A phase lag between the voltage and the current:

$$\sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\omega t - \phi)}$$


- In flux coordinates:
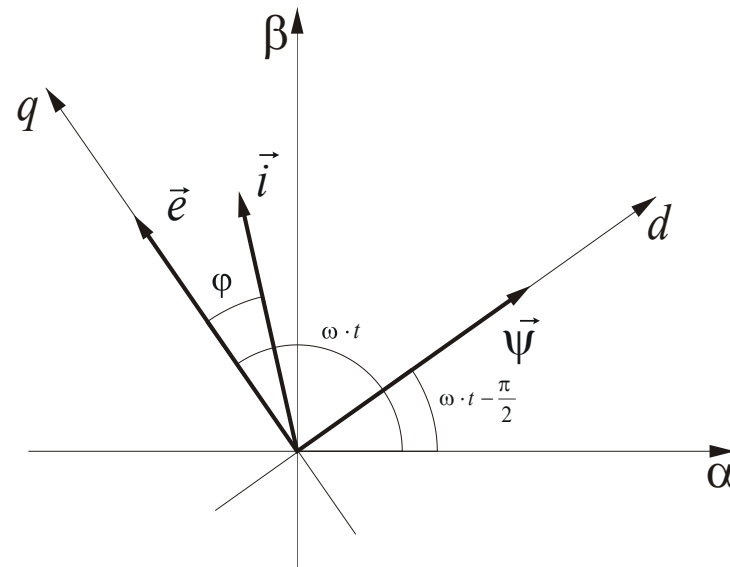
$$\sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\frac{\pi}{2} - \phi)}$$



Assymetric load

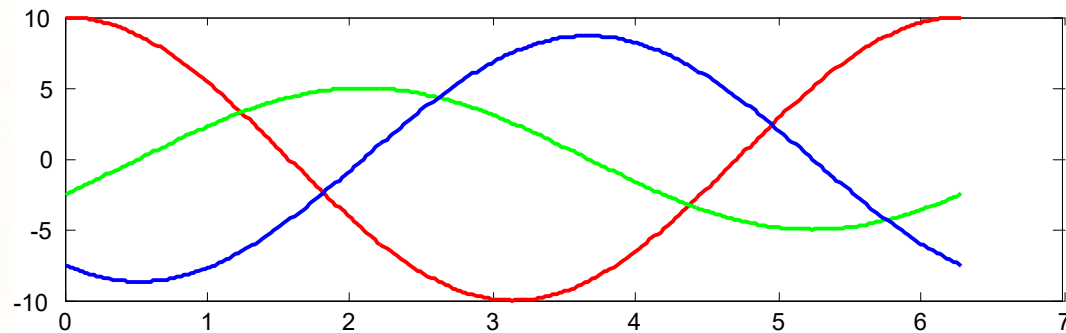- The phase currents are not equal in amplitude or phase lag ...



L11 - Static VAr compensation

An asymmetric load current vector in the (α, β) -frame

$$\vec{i} = \sqrt{\frac{2}{3}} \cdot \left(\hat{i}_a \cdot \frac{e^{j(\omega t - \phi_a)} + e^{-j(\omega t - \phi_a)}}{2} \cdot 1 + \hat{i}_b \cdot \frac{e^{j(\omega t - \phi_b - \frac{2\pi}{3})} + e^{-j(\omega t - \phi_b - \frac{2\pi}{3})}}{2} \cdot e^{j\frac{2\pi}{3}} + \hat{i}_c \cdot \frac{e^{j(\omega t - \phi_c - \frac{4\pi}{3})} + e^{-j(\omega t - \phi_c - \frac{4\pi}{3})}}{2} \cdot e^{j\frac{4\pi}{3}} \right) =$$

$$= \sqrt{\frac{2}{3}} \cdot \left(\hat{i}_a \cdot \frac{e^{j(\omega t - \phi_a)} + e^{-j(\omega t - \phi_a)}}{2} + \hat{i}_b \cdot \frac{e^{j(\omega t - \phi_b)} + e^{-j(\omega t - \phi_b - \frac{4\pi}{3})}}{2} + \hat{i}_c \cdot \frac{e^{j(\omega t - \phi_c)} + e^{-j(\omega t - \phi_c - \frac{2\pi}{3})}}{2} \right) =$$





$$= \begin{cases} \hat{i}_x = \hat{i}, \phi_x = \phi \rightarrow \sqrt{\frac{2}{3}} \cdot \frac{3 \cdot \hat{i}}{2} \cdot e^{j(\omega t - \phi)} + \sqrt{\frac{2}{3}} \cdot \frac{3 \cdot \hat{i}}{2} \cdot \underbrace{\left(e^{-j(\omega t - \phi)} + e^{-j(\omega t - \phi - \frac{4\pi}{3})} + e^{-j(\omega t - \phi - \frac{2\pi}{3})} \right)}_{=0} = \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\omega t - \phi)} \\ \hat{i}_x = \hat{i}, \hat{i}_c \neq \hat{i}, \phi_x = \phi \rightarrow \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\omega t - \phi)} + \sqrt{\frac{2}{3}} \cdot (\hat{i}_c - \hat{i}) \cdot \frac{e^{j(\omega t - \phi_c)} + e^{-j(\omega t - \phi_c - \frac{2\pi}{3})}}{2} \end{cases}$$


An assymmetric load current vector in the (d,q)-frame

$$\begin{aligned} \vec{i}^{dq} &= \vec{i}^{\alpha\beta} \cdot e^{-j(\omega t - \frac{\pi}{2})} = \begin{cases} = \\ = \end{cases} \\ &= \begin{cases} \hat{i}_x = \hat{i}, \phi_x = \phi \rightarrow \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\omega t - \phi)} \cdot e^{-j(\omega t - \frac{\pi}{2})} \\ \hat{i}_x = \hat{i}, \hat{i}_c \neq \hat{i}, \phi_x = \phi \rightarrow \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\omega t - \phi)} \cdot e^{-j(\omega t - \frac{\pi}{2})} + \sqrt{\frac{2}{3}} \cdot (\hat{i}_c - \hat{i}) \cdot \frac{e^{j(\omega t - \phi_c)} + e^{-j(\omega t - \phi_c - \frac{2\pi}{3})}}{2} \cdot e^{-j(\omega t - \frac{\pi}{2})} \end{cases} = \\ &= \begin{cases} \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\frac{\pi}{2} - \phi)} \\ \sqrt{\frac{3}{2}} \cdot \hat{i} \cdot e^{j(\frac{\pi}{2} - \phi)} + \frac{1}{\sqrt{6}} \cdot (\hat{i}_c - \hat{i}) \cdot \left(\underbrace{e^{j(\frac{\pi}{2} - \phi_c)}}_{\text{Not moving!}} + \underbrace{e^{-j(2\omega t - \phi_c - \frac{2\pi}{3} - \frac{\pi}{2})}}_{\text{Rotating backwards with } 2\omega!} \right) \end{cases} \end{aligned}$$

M-file "Load current vectors" - demo


- Symmetric load
- Assymmetric

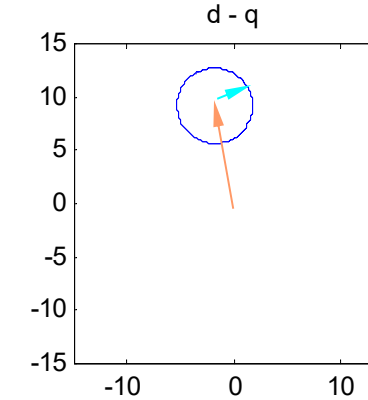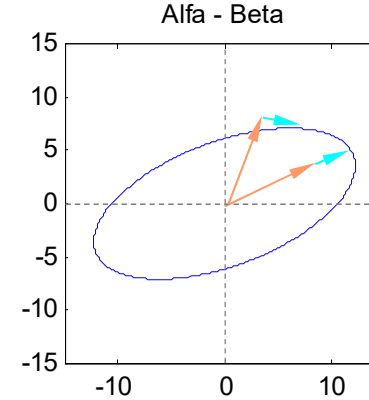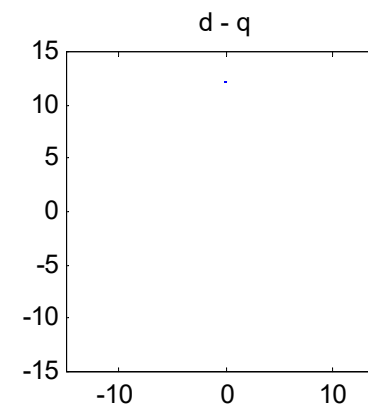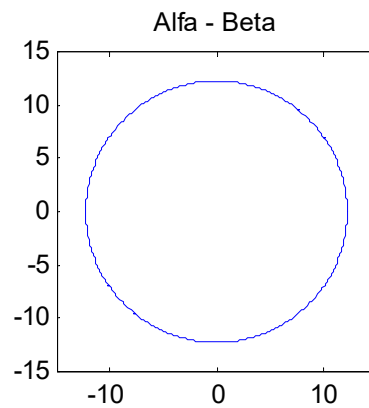

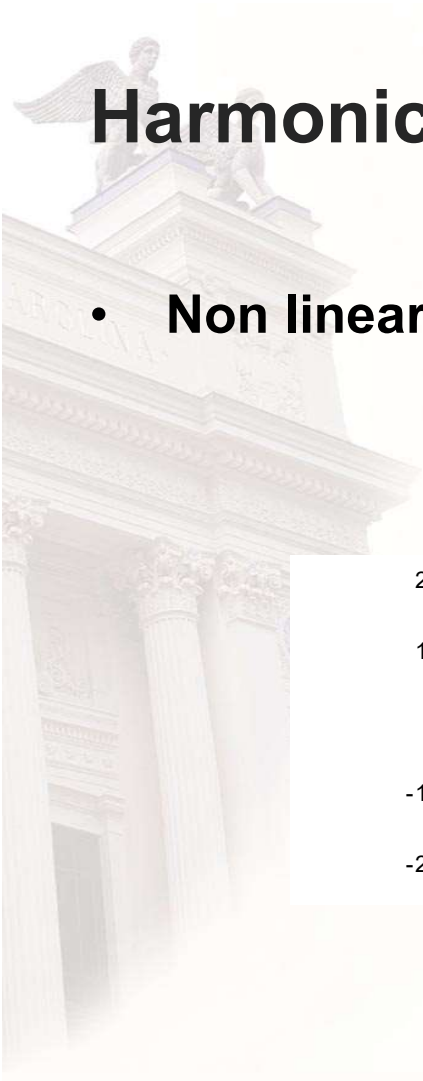

Harmonics

- Non linear load impedance

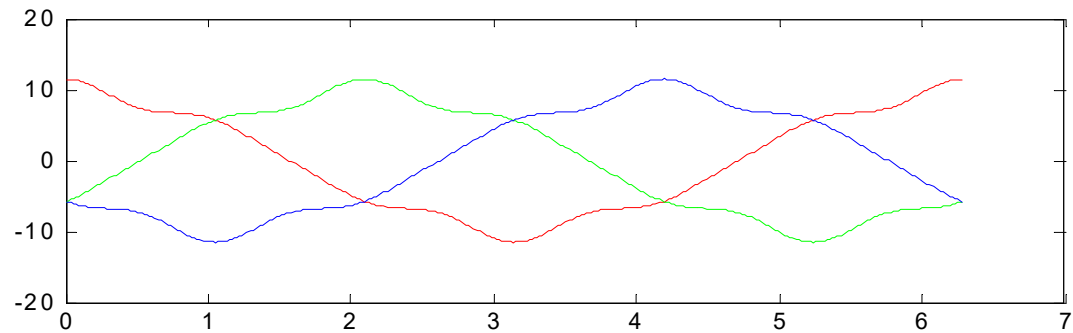


L11 - Static VAr compensation

5'th and 7'th harmonic example with Simulink

$$\vec{i}^{\alpha\beta} = \sqrt{\frac{3}{2}} \cdot \hat{i}_1 \cdot e^{j(\omega t - \phi)} + \sqrt{\frac{3}{2}} \cdot \hat{i}_5 \cdot e^{j(-5\omega t - \phi)} + \sqrt{\frac{3}{2}} \cdot \hat{i}_7 \cdot e^{j(7\omega t - \phi)}$$


$$\vec{i}^{dq} = \sqrt{\frac{3}{2}} \cdot \hat{i}_1 \cdot e^{j(\frac{\pi}{2} - \phi)} + \sqrt{\frac{3}{2}} \cdot \hat{i}_5 \cdot e^{j(-6\omega t - \phi)} + \sqrt{\frac{3}{2}} \cdot \hat{i}_7 \cdot e^{j(6\omega t - \phi)}$$

Active filtering

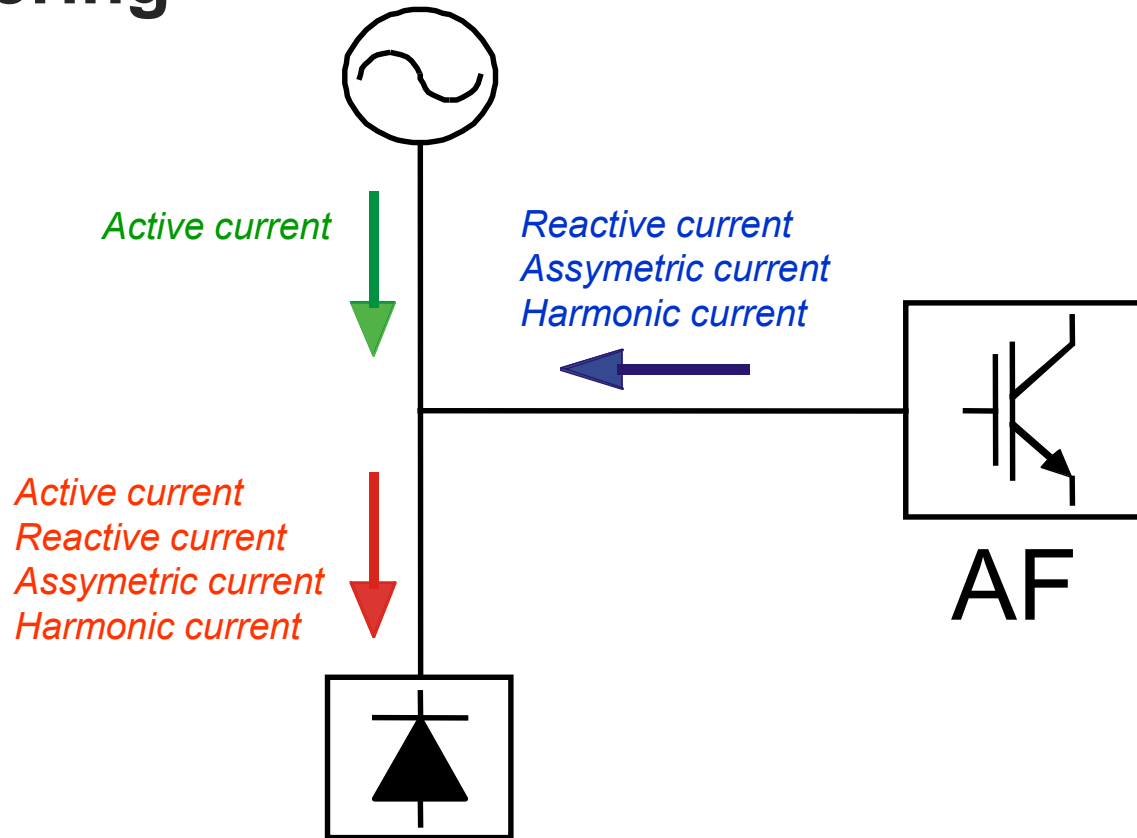

L11 - Static VAr compensation

Shunt Active Filter

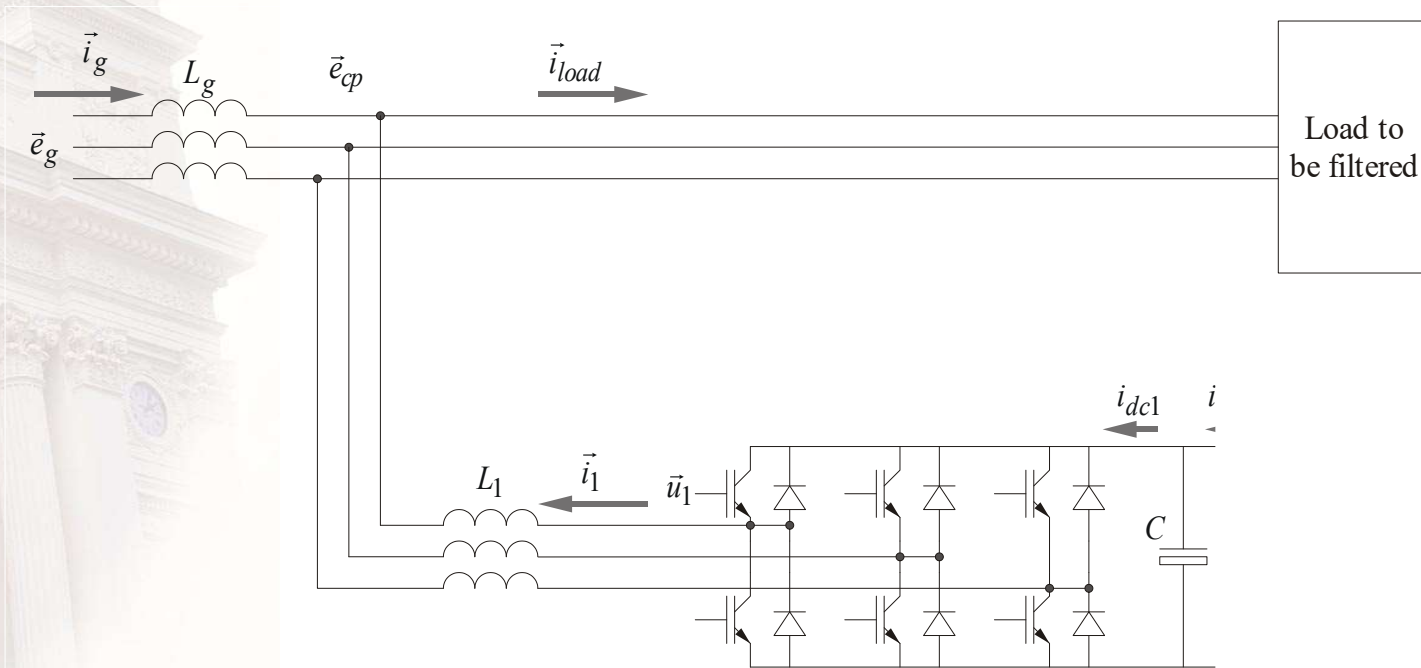



L11 - Static VAr compensation

AC side Current Control

- **Vector Control with Field Orientation**

$$\vec{u}_1^*(k) = \left(\frac{L_1}{T_s} + \frac{R_1}{2} \right) \cdot \left((\vec{i}_1^*(k) - \hat{i}_1(k)) + \frac{T_s}{\left(\frac{L}{R} + \frac{T_s}{2} \right)} \cdot \sum_{n=0}^{n=k-1} (\vec{i}_1^*(n) - \hat{i}_1(n)) \right) + \hat{e}_{cp}(k)$$

DC link Voltage Control System

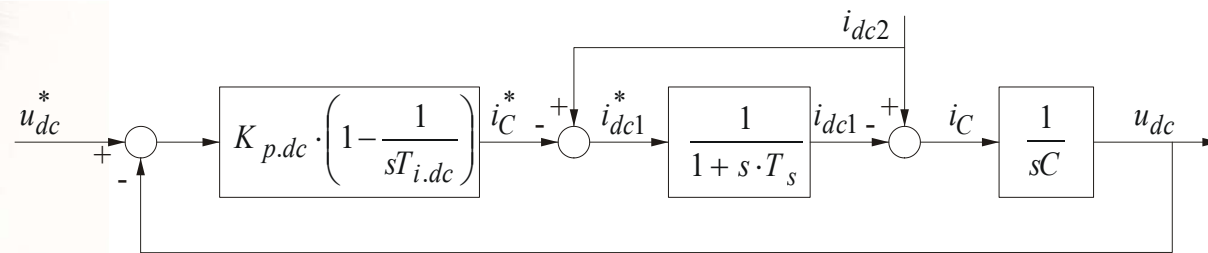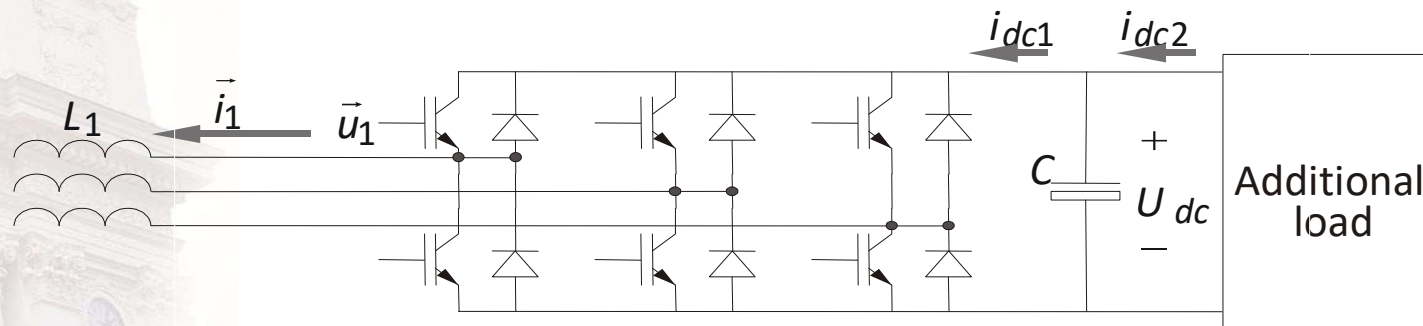

L11 - Static VAr compensation



Controller Parameters ...

- Use Symmetric Optimum

$$\zeta = \frac{a - 1}{2}$$

$$T_{i.dc} = a^2 \cdot T_s, \text{ where } a > 1$$

$$K_{p.dc} = \frac{a \cdot C}{T_{i.dc}}$$


Convert DC to AC current references

$$p(t) = Ri_{1d}^2 + Ri_{1q}^2 + L \frac{di_{1d}}{dt} i_{1d} + L \frac{di_{1q}}{dt} i_{1q} + e_{cp.q} i_{1q} = u_{dc} \cdot i_{dc1} \approx e_{cp.q} i_{1q}$$

↓


$$i_{dc1} = \frac{e_{cp.q}}{u_{dc}} \cdot i_{1q}$$

DC link voltage controller

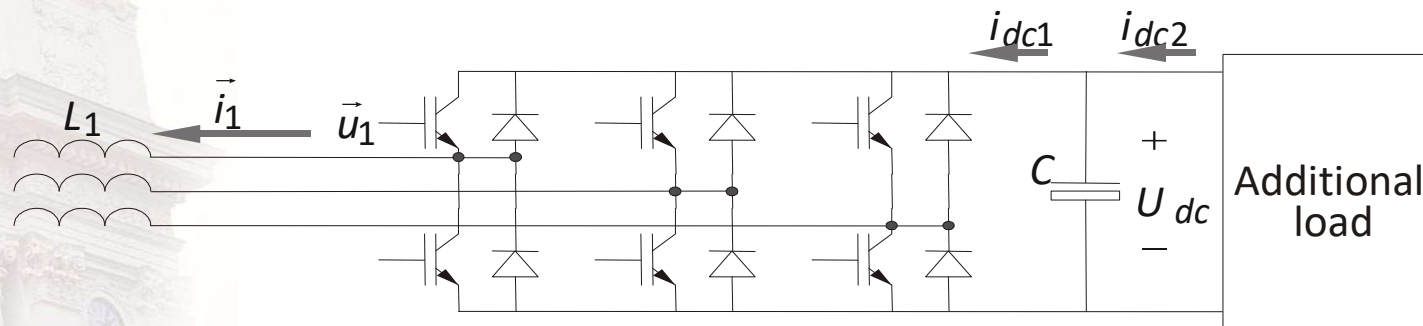

$$i_{1q}^* = \frac{u_{dc}}{e_{cp}} \left(i_{dc2} - K_{p.dc} \cdot \left(1 - \frac{1}{sT_{i.dc}} \right) \cdot (u_{dc}^* - u_{dc}) \right)$$

DC Link Voltage Control vs Speed Control

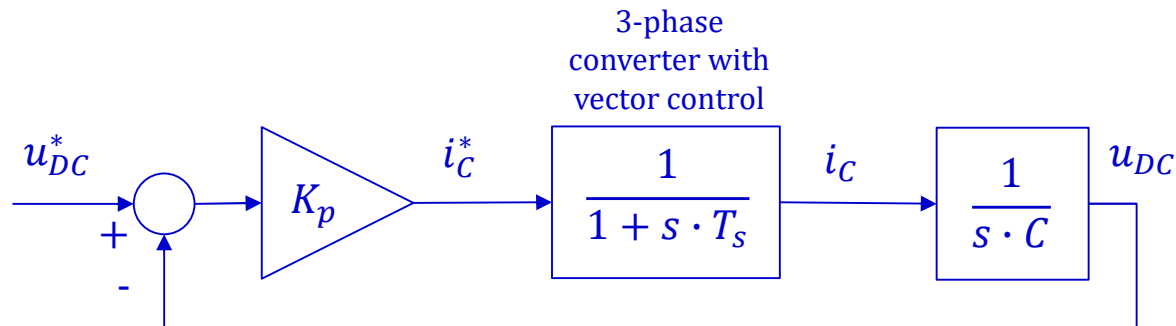

$$\frac{u_{DC}}{u_{DC}^*} = \frac{K_p \cdot \frac{1}{1+s \cdot T_s} \cdot \frac{1}{s \cdot C}}{1 + K_p \cdot \frac{1}{1+s \cdot T_s} \cdot \frac{1}{s \cdot C}}$$

$$= \frac{\frac{K_p}{C \cdot T_s}}{s^2 + s \cdot \frac{1}{T_s} + \frac{K_p}{C \cdot T_s}}$$

$$s^2 + s \cdot \frac{1}{T_s} + \frac{K_p}{C \cdot T_s} = 0 \rightarrow K_p = \frac{C}{4 \cdot T_s}$$

Speed Control

Torque dynamics as first order low pass filter

Closed system:

$$\frac{\omega^*}{\omega} = \frac{\frac{k_\omega}{J \cdot T_{ic}}}{s^2 + s \cdot \frac{1}{T_{ic}} + \frac{k_\omega}{J \cdot T_{ic}}}$$

Roots:

$$-\frac{1}{2T_{ic}} \pm \sqrt{\frac{1}{4 \cdot T_{ic}^2} - \frac{k_\omega}{J \cdot T_{ic}}}$$


Non osc. roots ->

$$k_\omega = \frac{J}{4 \cdot T_{ic}}$$


Limited k_ω gives stationary error with P-control!!!

© Mats Alakula
Power Electronics / Speed & Position Control

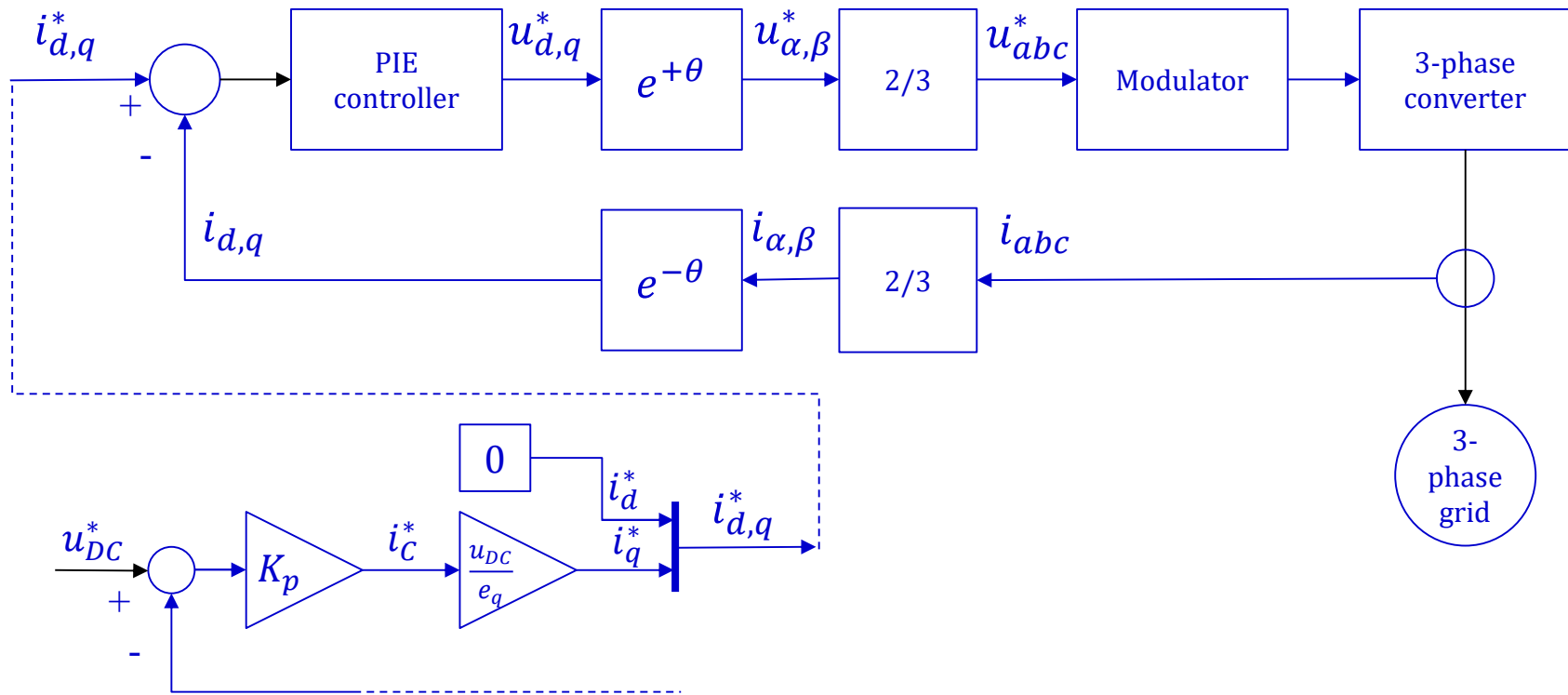
The 3phase Grid connected converter is the DC link current source



The full control system

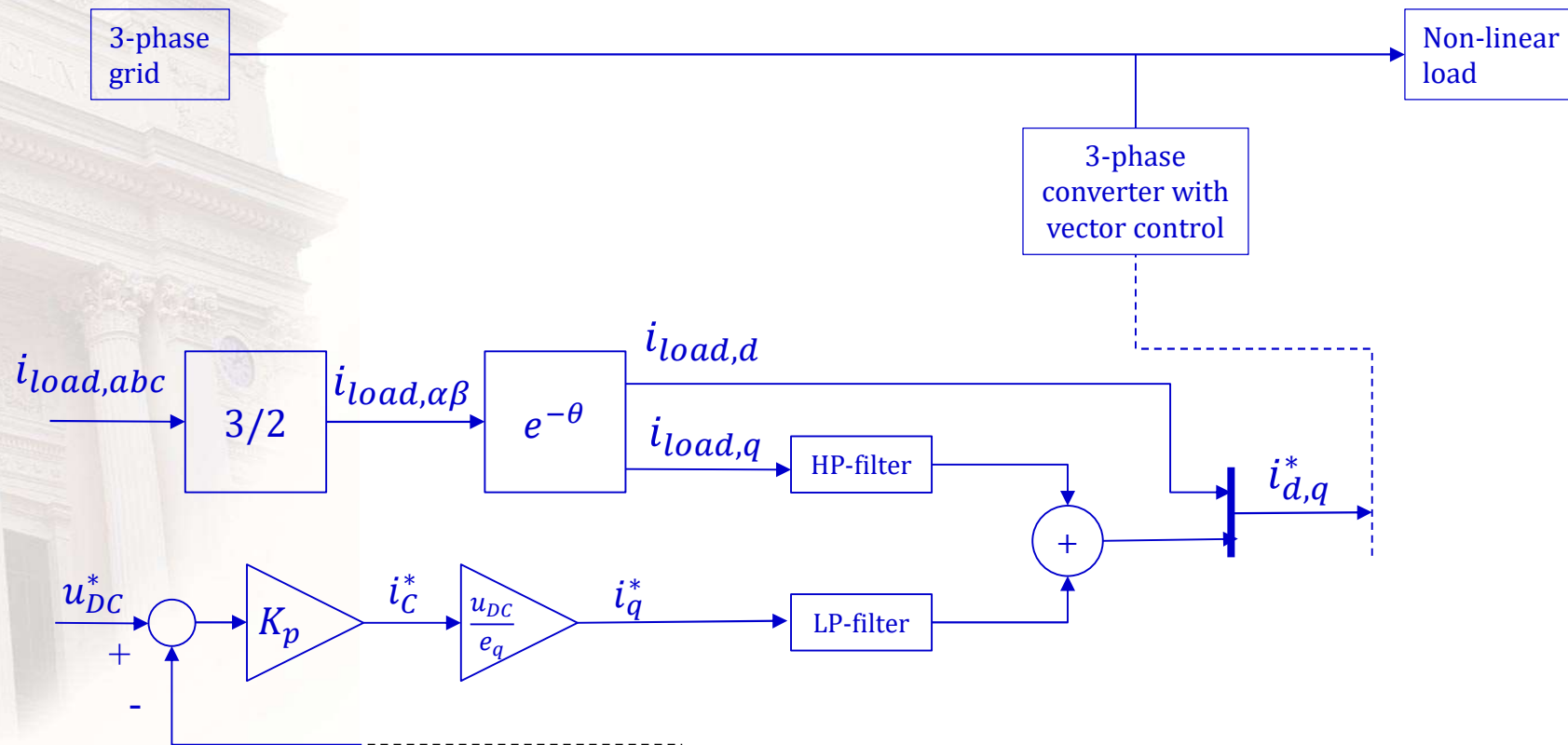


Active filter control

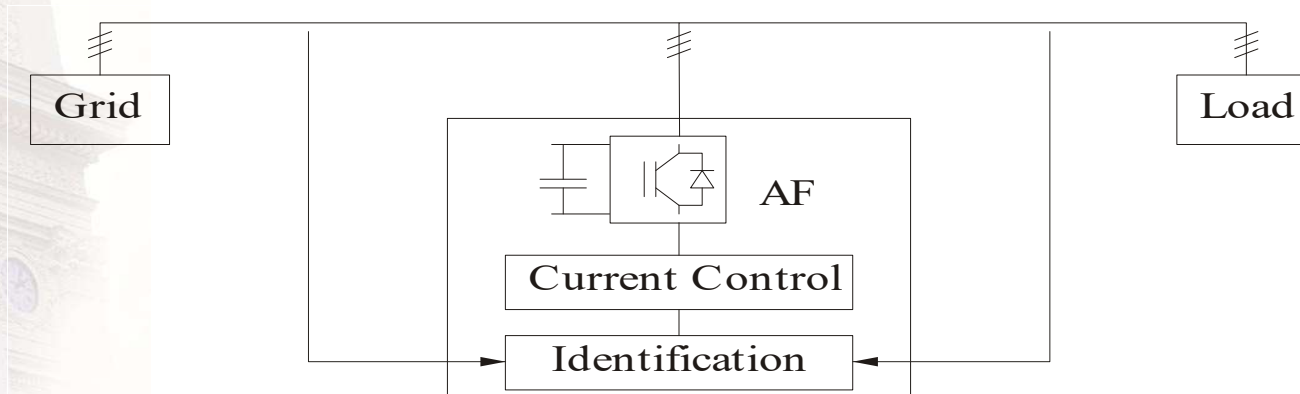


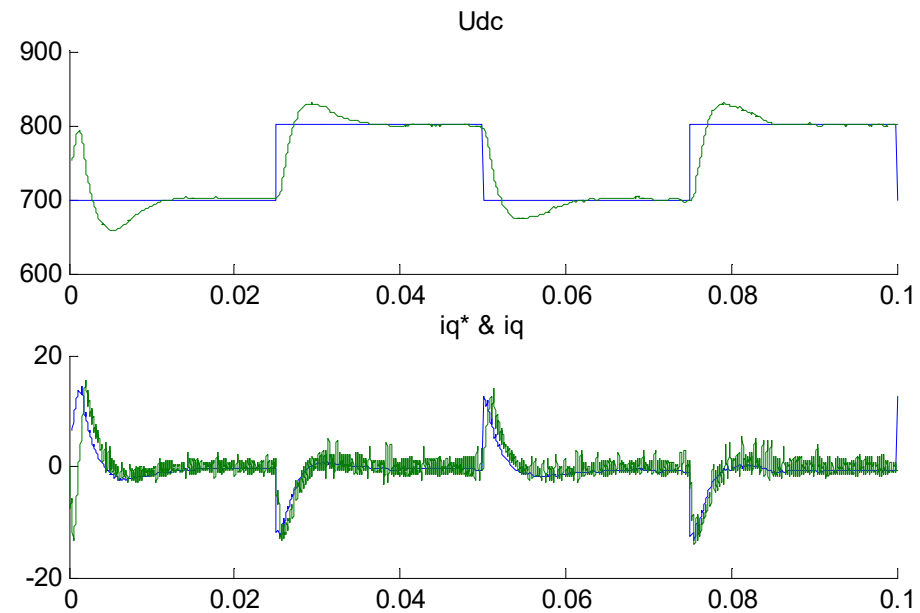
Example of DC voltage control

```
>> L=0.01;  
>> R=1;  
>> Ts=0.0005;  
>> Tdc=9*Ts;  
>> Kpdc=3*Cdc/Tdc;  
>> Cdc=1e-4;
```



L11 - Static VAr compensation

Example with active filtering

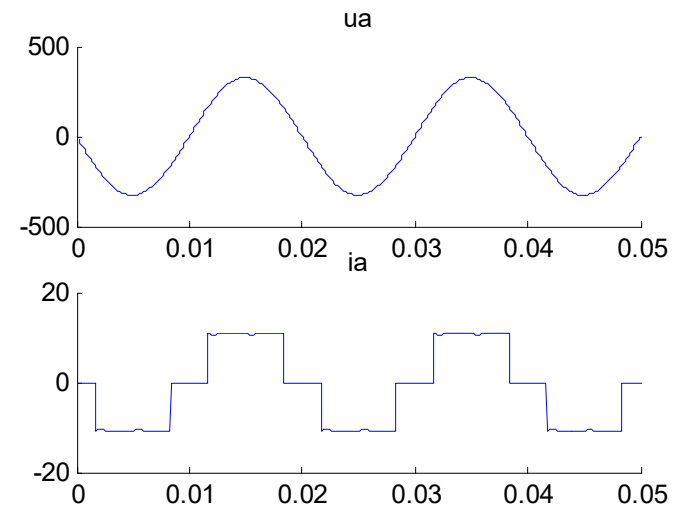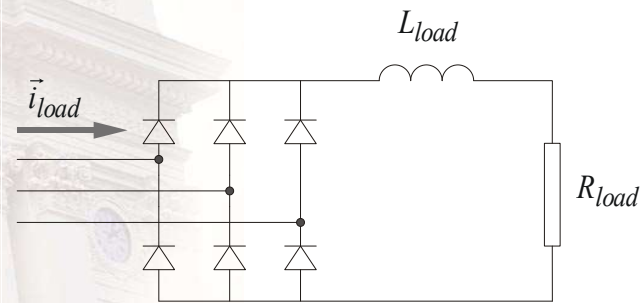




Filter Current References

$$i_{d,ActiveFilter}^* = i_{d,load}$$

$$i_{q,ActiveFilter}^* = i_{q,load} \cdot \frac{s \cdot T_f}{1 + s \cdot T_f} + \frac{u_{dc}}{e_{cp}} \left(i_{dc2} - K_{p.dc} \cdot \left(1 - \frac{1}{sT_{i.dc}} \right) \cdot (u_{dc}^* - u_{dc}) \right) \cdot \frac{1}{1 + s \cdot T_f}$$

Filter Currents

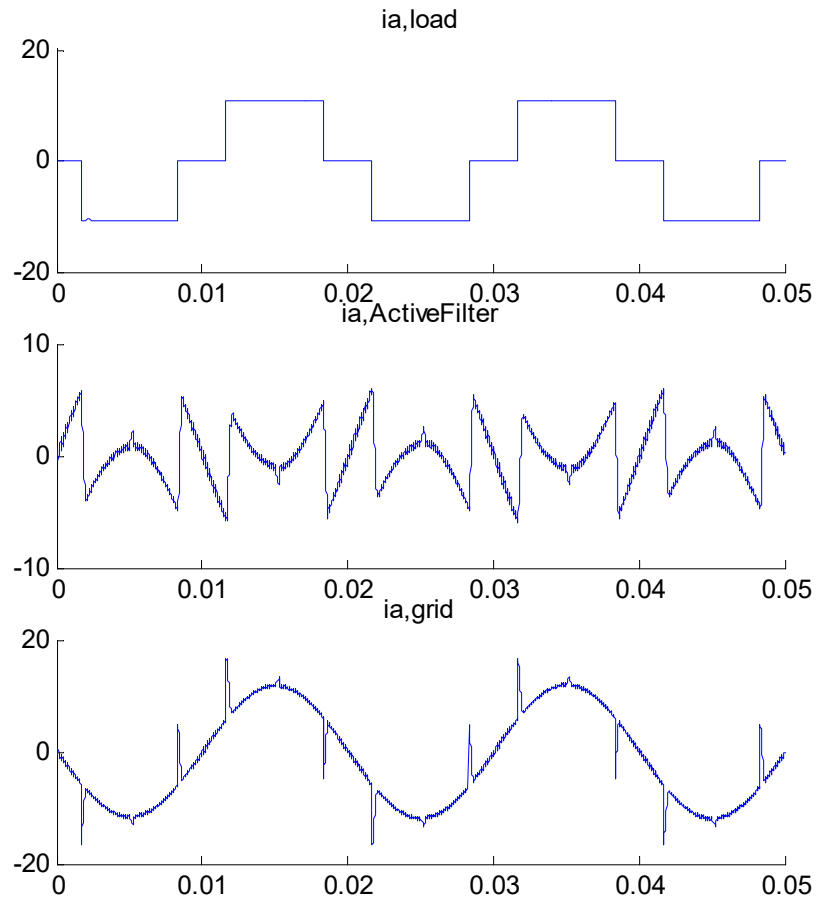
```
>> L=0.01;  
>> R=1;  
>> Ts=0.00005;  
>> Rload=50;  
>> Lload=0.1;  
>> Tf=10e-3;  
>> Tdc=9*Tf;  
>> Kpdc=3*Cdc/Tdc;
```




L11 - Static VAr compensation

Spectra

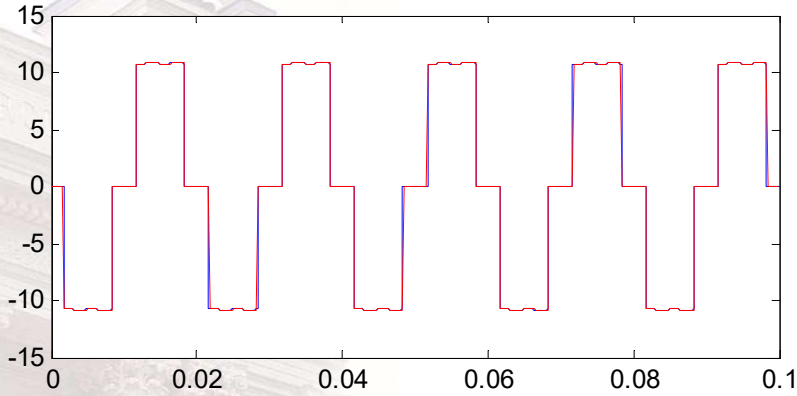
Original signal (Blue) and resampled signal (Red)



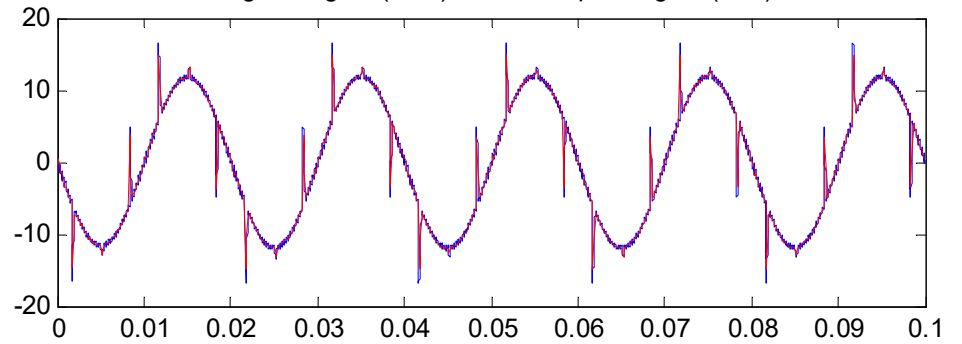
Original signal (Blue) and resampled signal (Red)




Frequency spectra with 10 Hz resolution

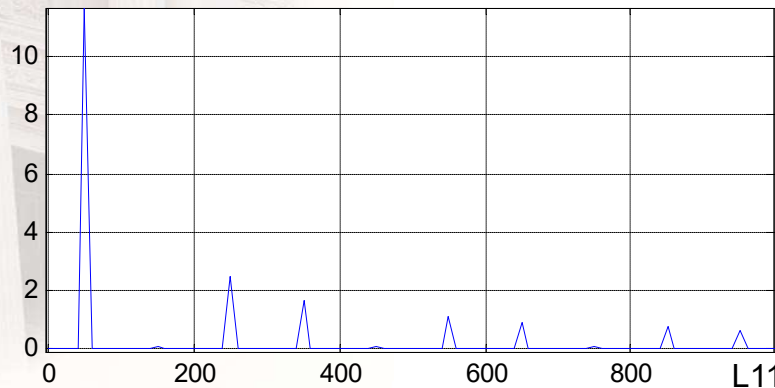

Frequency spectra with 10 Hz resolution

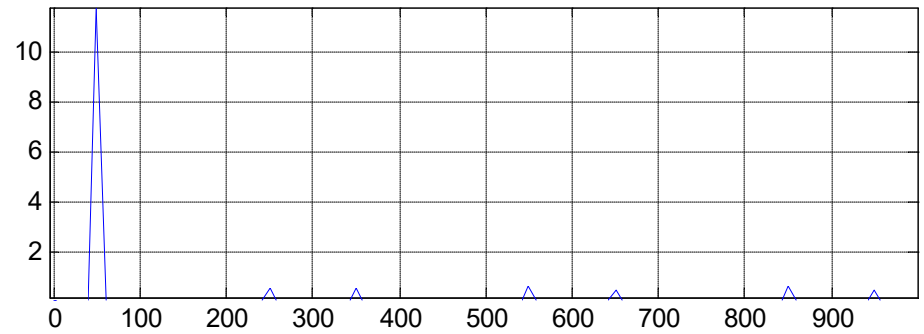

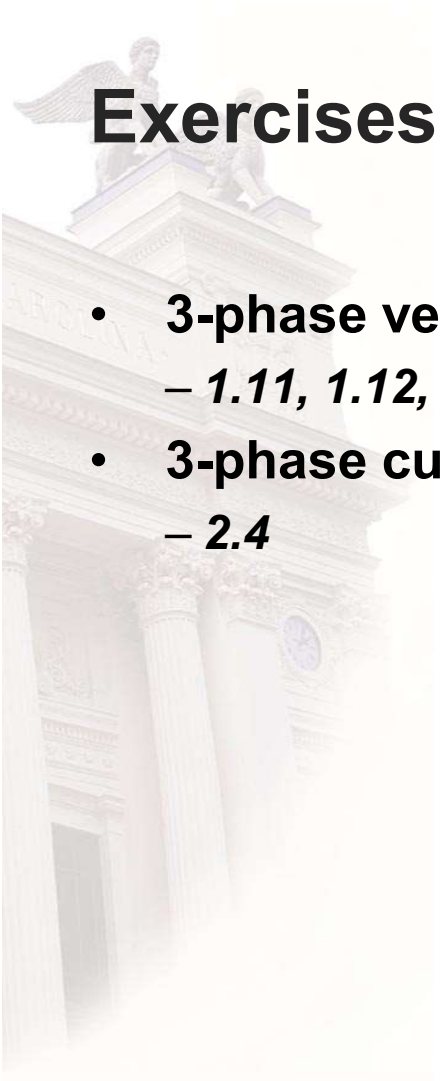

Exercises

- **3-phase vectors**
 - *1.11, 1.12, 1.13, 1,14*
- **3-phase current control**
 - *2.4*