
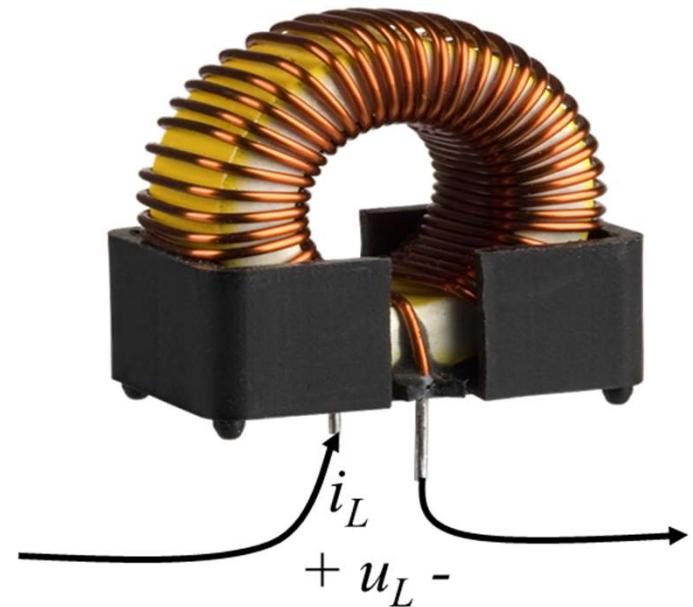


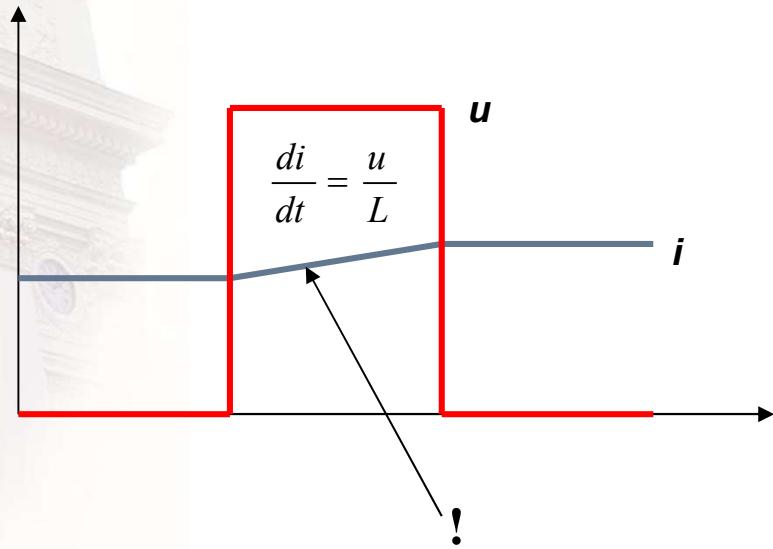Lecture 2 – Bridges, switches and snubbers





Summary

An inductance keeps a current "constant"



Summary


A capacitance keeps a voltage "constant"

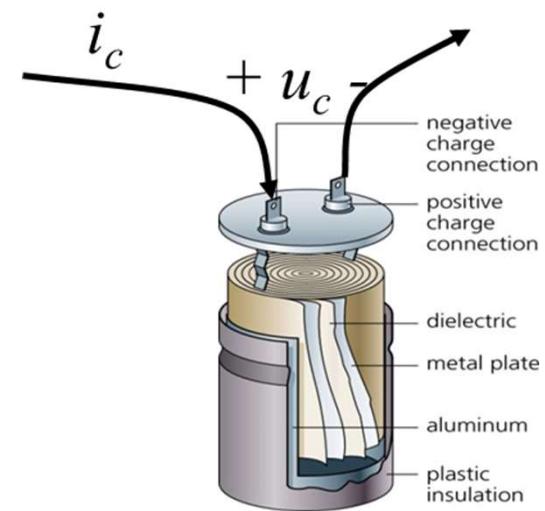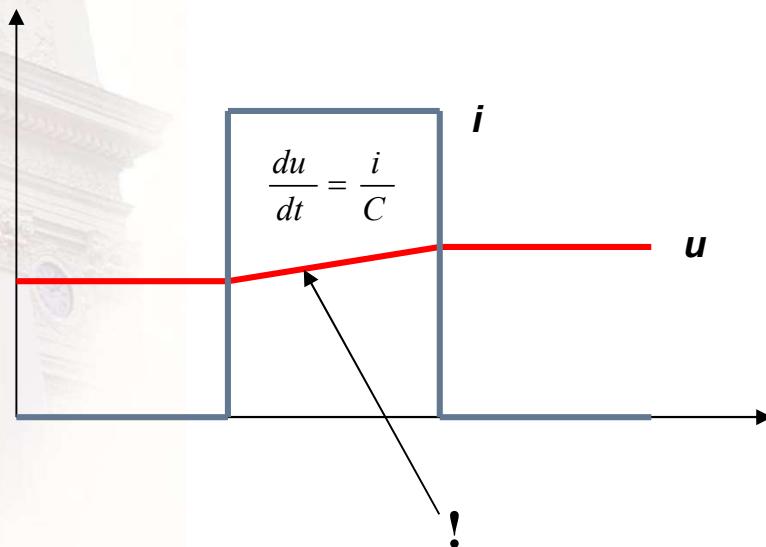



Some fundamental topologies

Quadrants

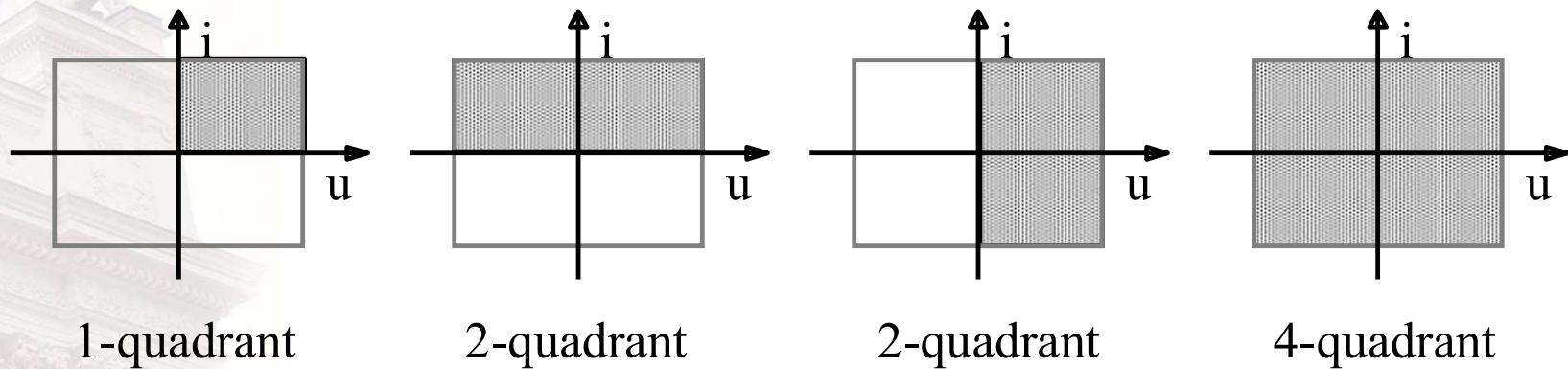


1-quadrant


2-quadrant

2-quadrant


4-quadrant

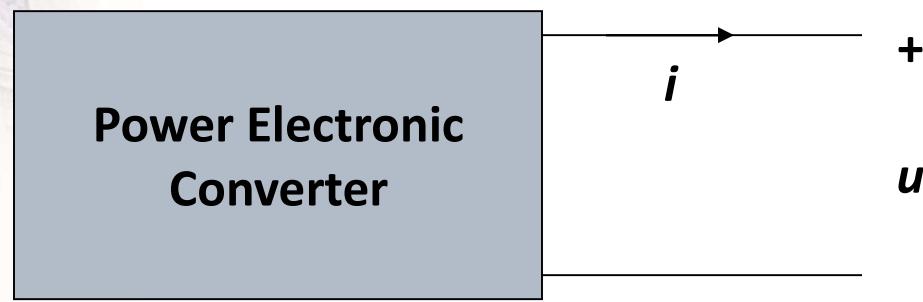

Classification

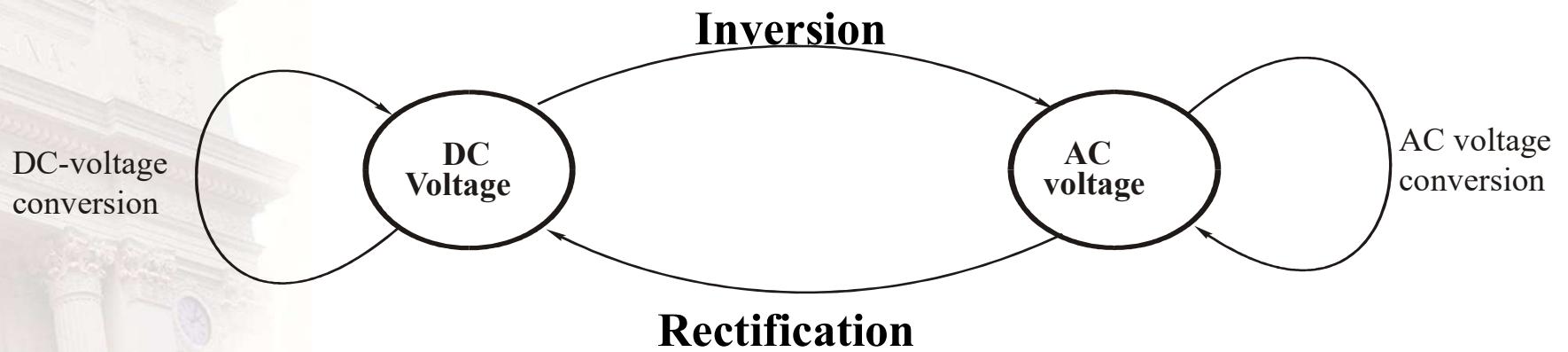


Single phase diode rectifier ideal

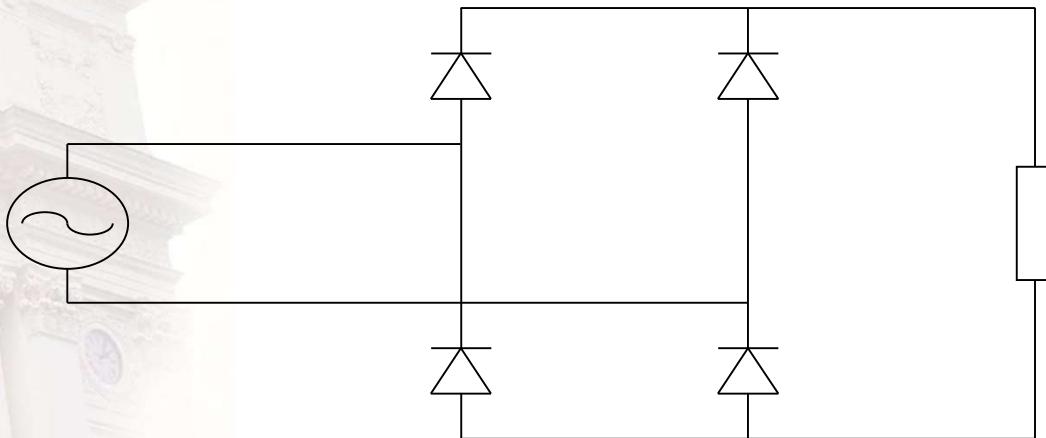


Single phase diode rectifier ideal



Positive

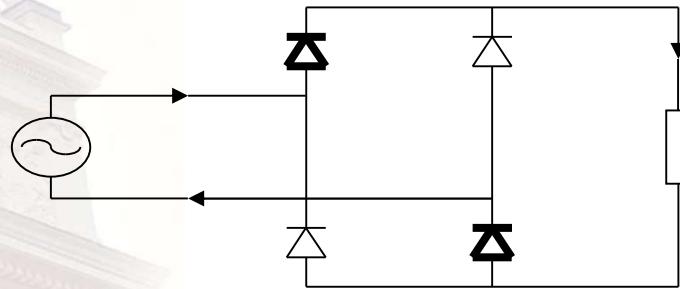

Negative

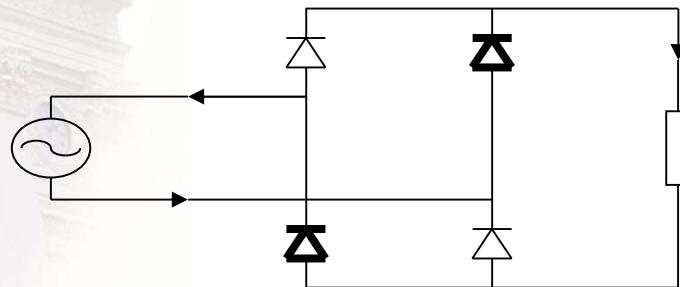
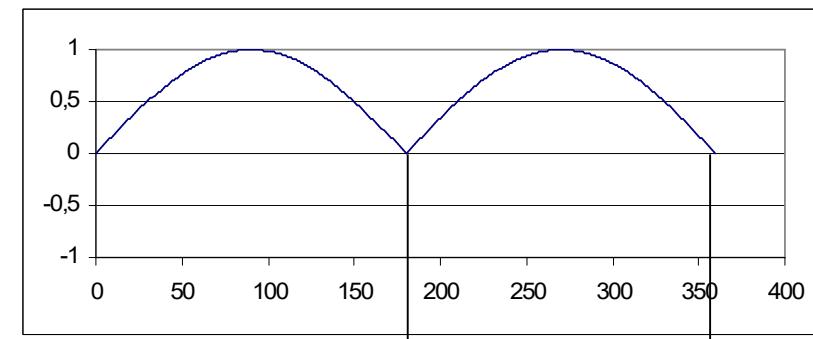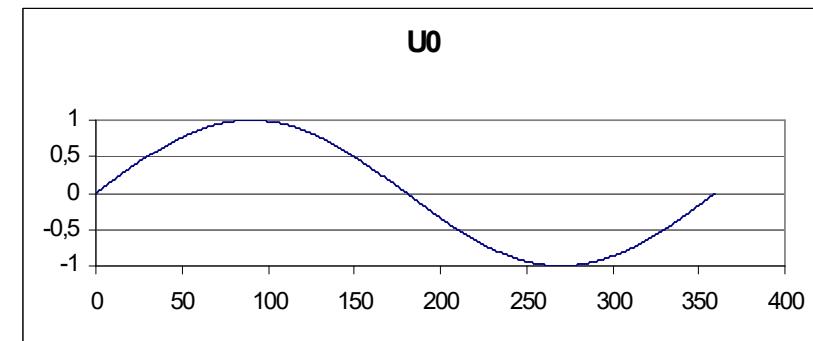
$$V_{dc} = \frac{1}{T/2} \int_{T/2}^{\infty} \hat{e}_{LN} \cos(\omega t) dt = 2 \frac{\hat{e}_{LN}}{2\pi} \int_{-\pi/2}^{\pi/2} \cos(\omega t) d(\omega t) = \frac{2}{\pi} \hat{e}_{LN} = \frac{2\sqrt{2}}{\pi} E_{LN}$$



$T/2$

Diode rectifier with capacitive DC link

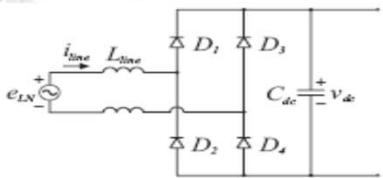


Figure 1.1: A single-phase diode rectifier with a capacitive DC link.

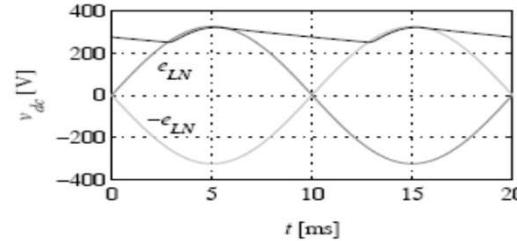


Figure 1.2: Line-to-neutral voltage and DC side voltage for a single-phase diode rectifier with a capacitive DC link.

$$V_{dc} = \frac{1}{T/2} \int_{T/2}^0 \hat{e}_{LN} \cos(\omega t) dt = 2 \frac{\hat{e}_{LN}}{2\pi} \int_{-\pi/2}^{\pi/2} \cos(\omega t) d(\omega t) = \frac{2}{\pi} \hat{e}_{LN} = \frac{2\sqrt{2}}{\pi} E_{LN}$$

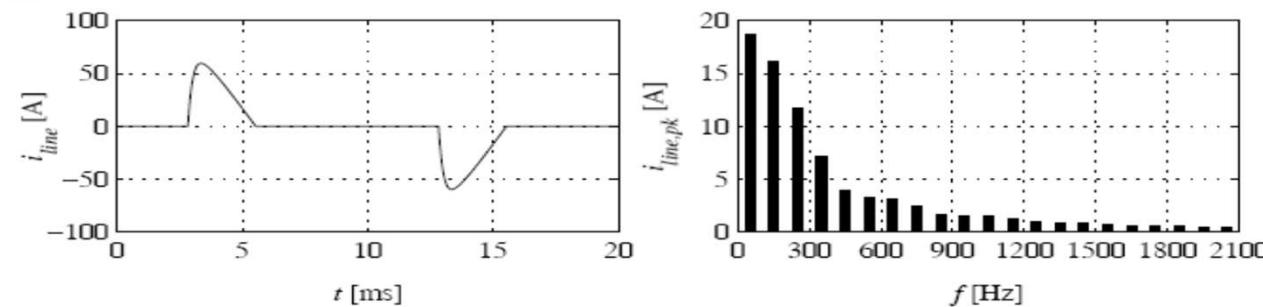


Figure 1.3: Line current (left) and its frequency spectrum (right), for a single-phase diode rectifier with a capacitive DC link.

The Buck Converter (Step-Down Converter)

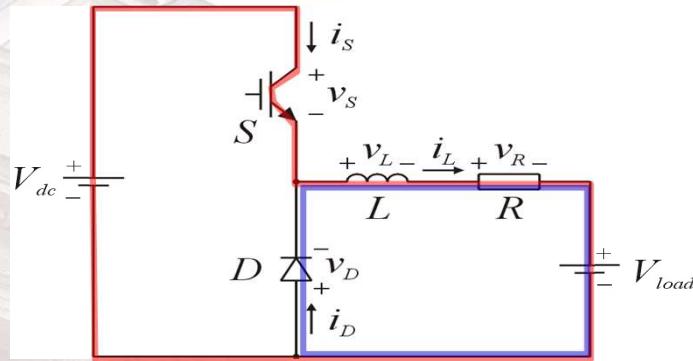


Figure 1.16: Buck converter.

S "on"

$$V_{dc} - V_{load} = v_L = L \frac{di_L}{dt} \Rightarrow \Delta i_L = \frac{V_{dc} - V_{load}}{L} \cdot DT_{sw}$$

S "off"

$$-V_{load} = v_L = L \frac{di_L}{dt} \Rightarrow \Delta i_L = -\frac{V_{load}}{L} \cdot (1 - D)T_{sw}$$

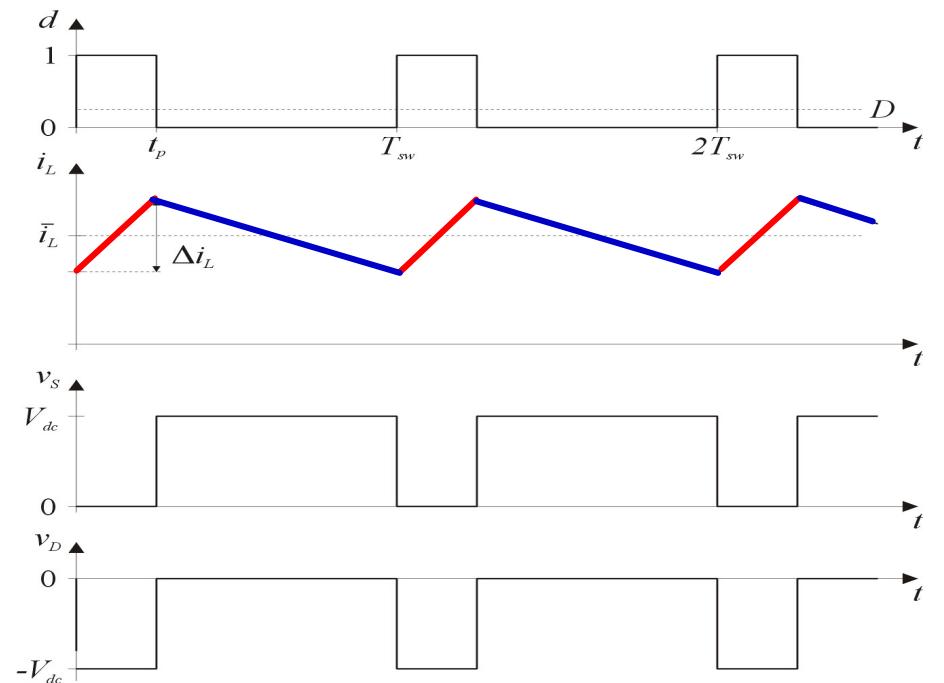


Figure 1.17: Ideal waveforms of the Buck converter.

The Boost Converter (Step-Up Converter)

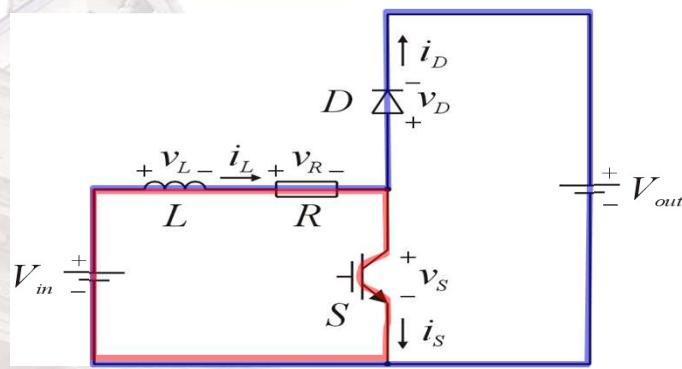


Figure 1.18: Boost converter.

S "on"

$$L \frac{di_L}{dt} = v_L = V_{in} - v_S \approx V_{in} \Rightarrow \Delta i_L = \frac{V_{in}}{L} \cdot DT_{sw}$$

S "off"

$$L \frac{di_L}{dt} = v_L = V_{in} - v_D - V_{out} \approx V_{in} - V_{out} \Rightarrow \Delta i_L = \frac{V_{in} - V_{out}}{L} \cdot (1 - D) T_{sw}$$

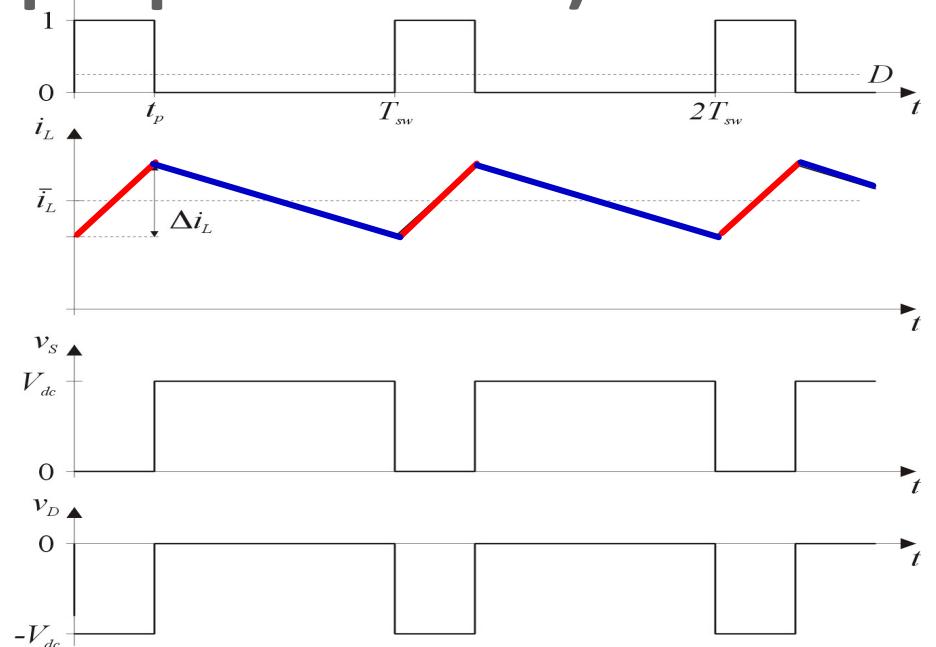


Figure 1.17: Ideal waveforms of the Boost converter.
Replace V_{dc} and V_{load} of the Buck converter with V_{out} and V_{in}

The Buck-Boost Converter (Half-Bridge)

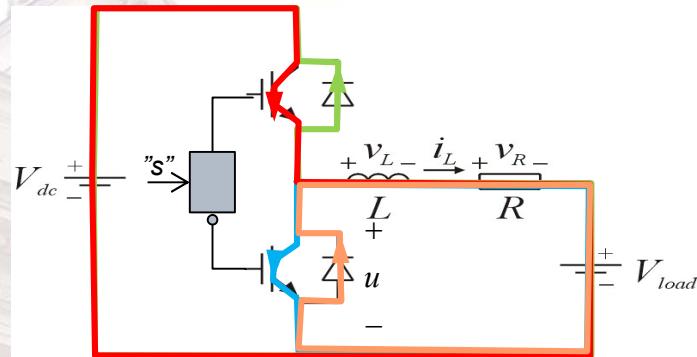



Figure 1.19: Buck-boost converter.

s "on"

$$V_{dc} - V_{load} = v_L = L \frac{di_L}{dt} \Rightarrow \Delta i_L = \frac{V_{dc} - V_{load}}{L} \cdot DT_{sw}$$

s "off"
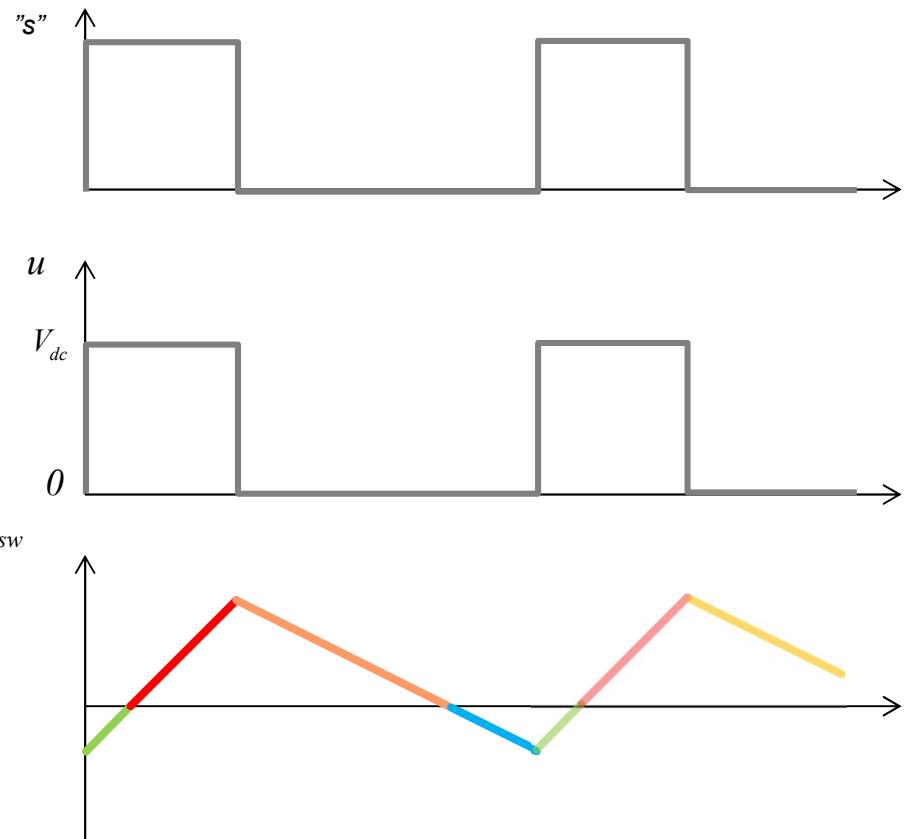
$$-V_{load} = v_L = L \frac{di_L}{dt} \Rightarrow \Delta i_L = -\frac{V_{load}}{L} \cdot (1 - D)T_{sw}$$



The Flyback Converter


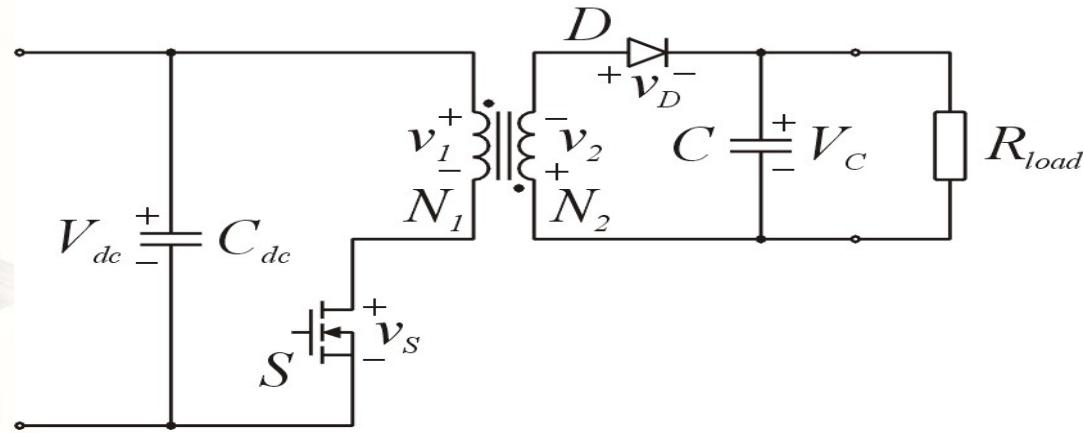


Figure 1.23: Principal schematic of a flyback converter. Only the devices needed to understand the operation are included.

The Laboratory Flyback Converter

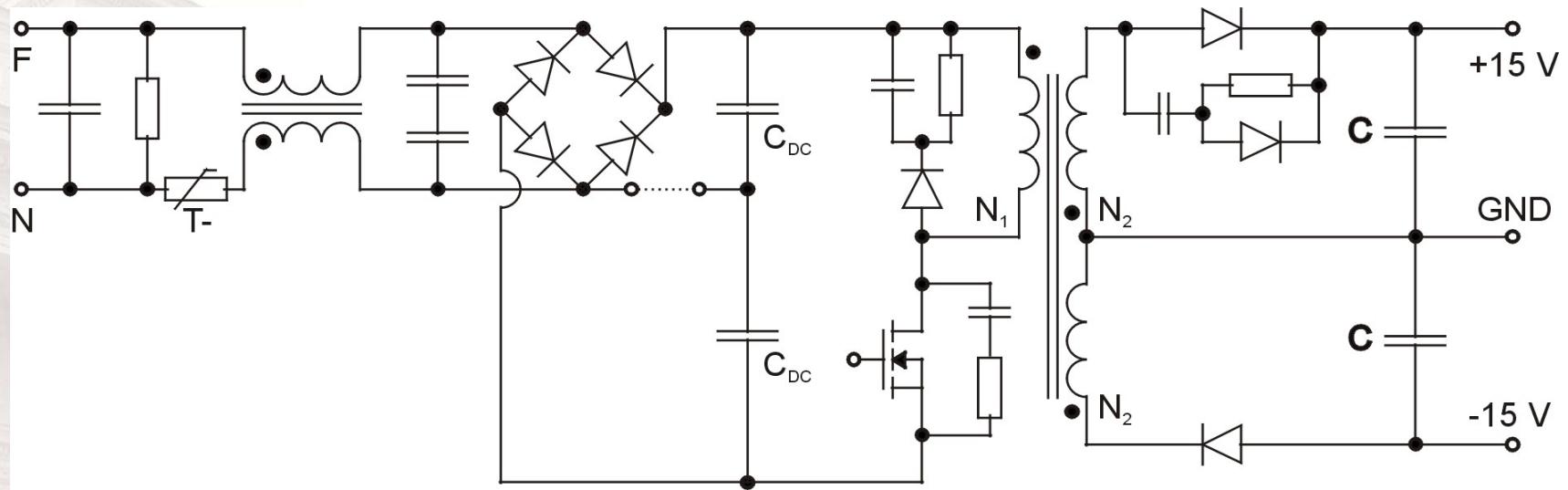


Flyback converter with input filter, inrush current limitation, diode rectifier, dc link capacitors, power MOSFET, transformer, output filter and three snubber circuits. The controller circuits are not included in the circuit.


Switching dynamics 1

- Note:

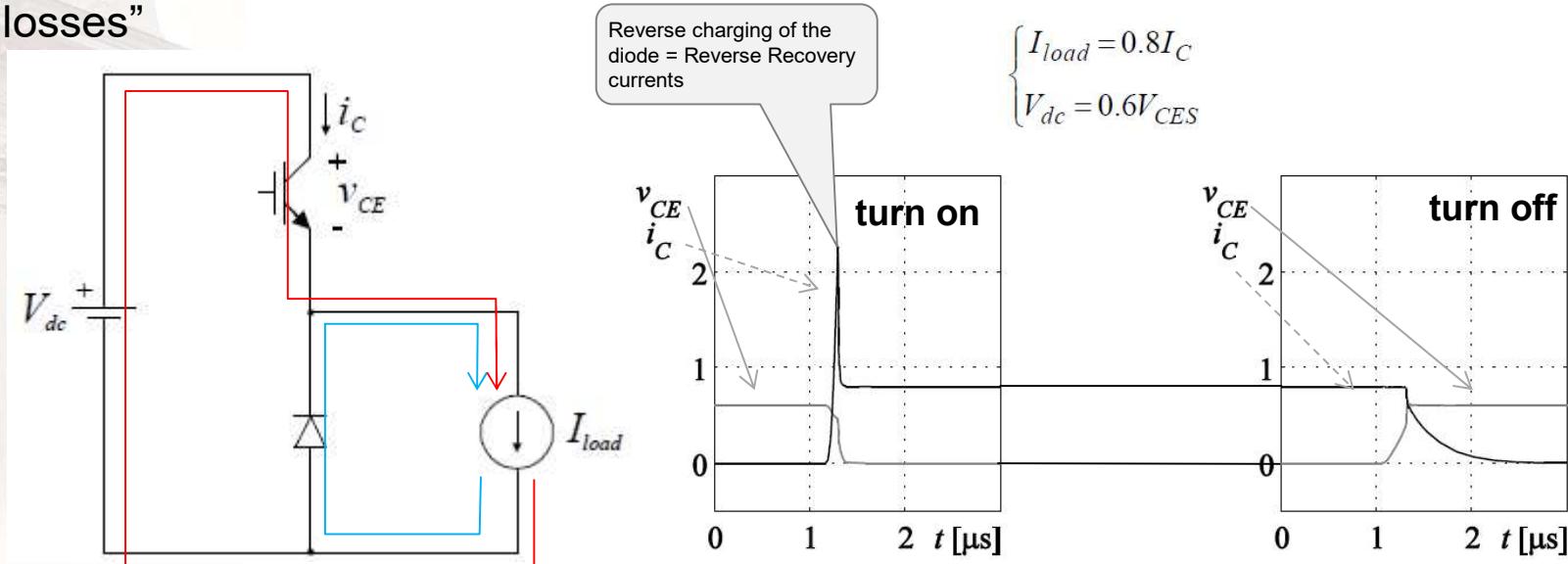
- the "reverse recovery currents" in the diode at turn on
- the simultaneous voltage and current when switching – high "switching losses"



RC charge-discharge snubber



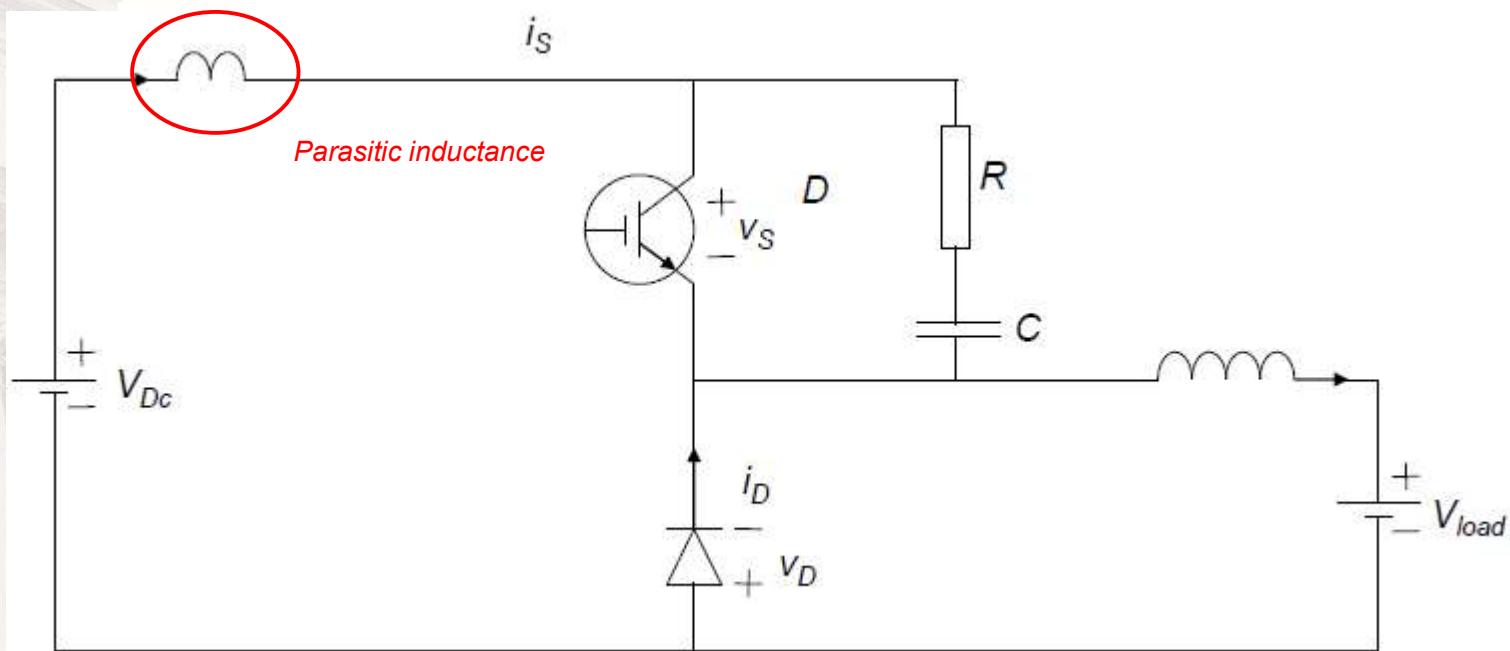


RCD charge-discharge snubber

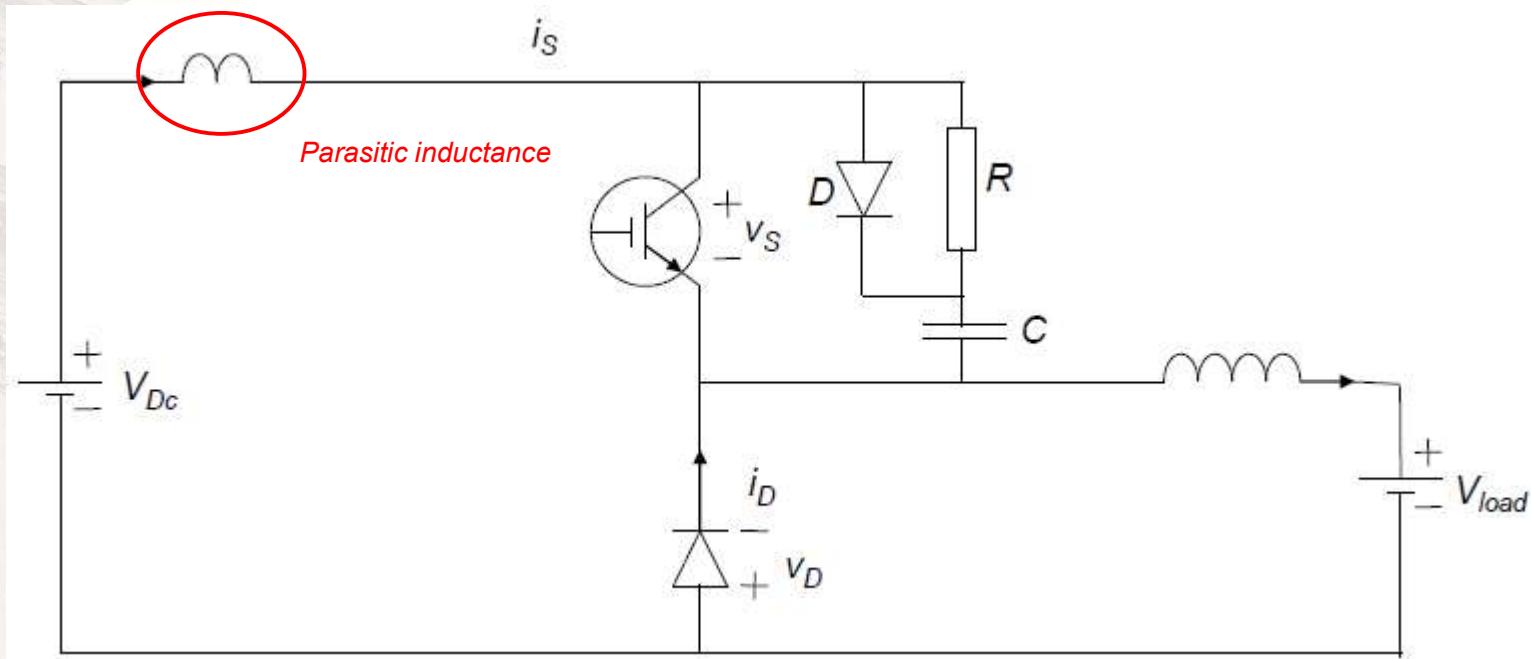


Switching dynamics

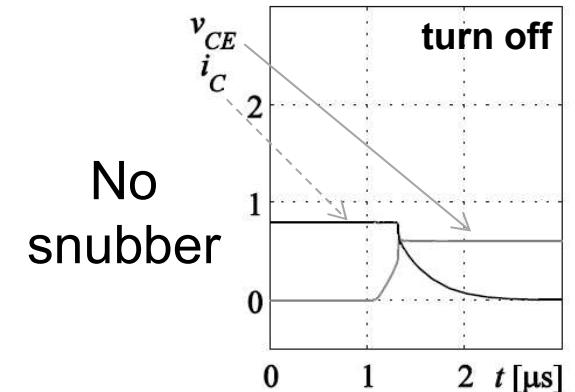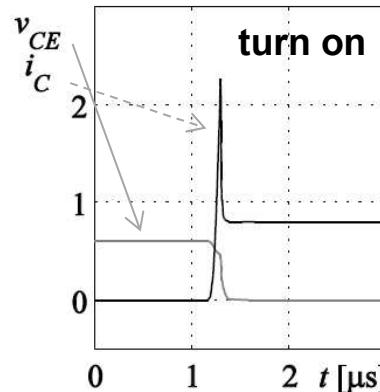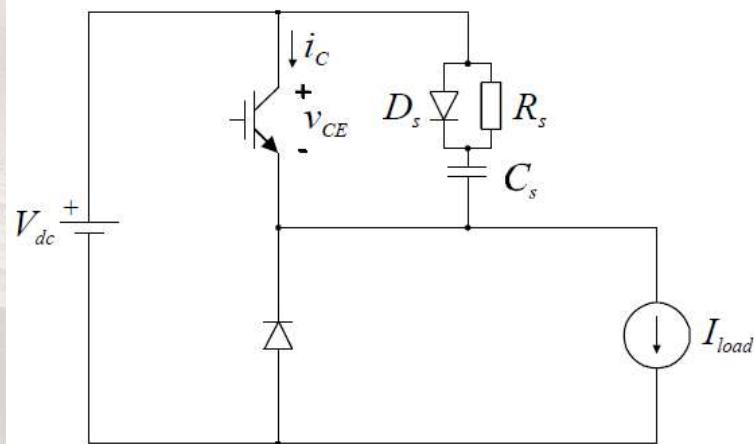
$$\begin{cases} I_{load} = 0.8I_C \\ V_{dc} = 0.6V_{CES} \end{cases}$$



No
snubber

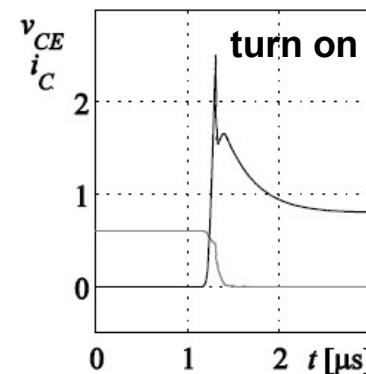

RCD
snubber:

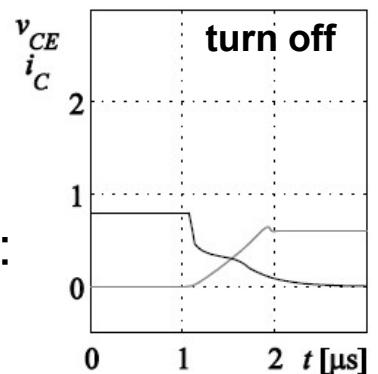



That's all folks...

