
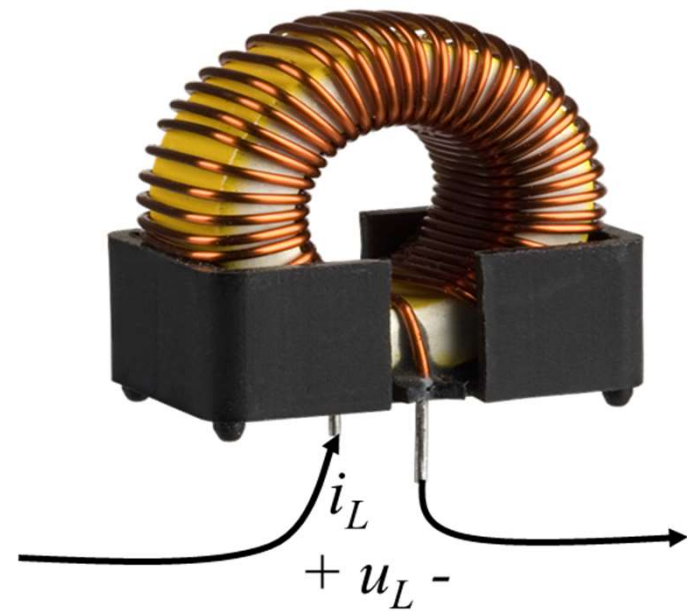


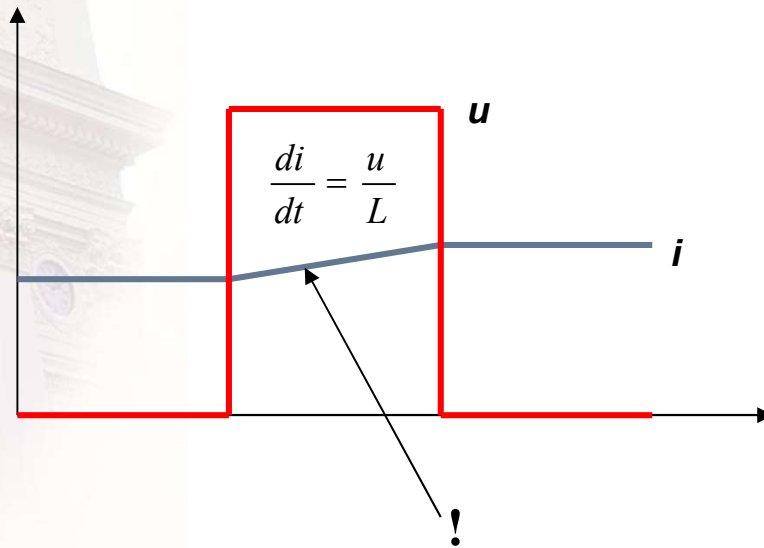

Lecture 3 – Modulation



Summary


An inductance keeps a current "constant"



Summary


A capacitance keeps a voltage "constant"

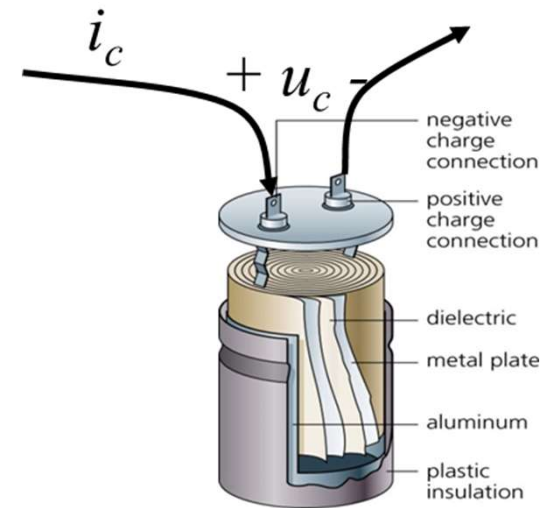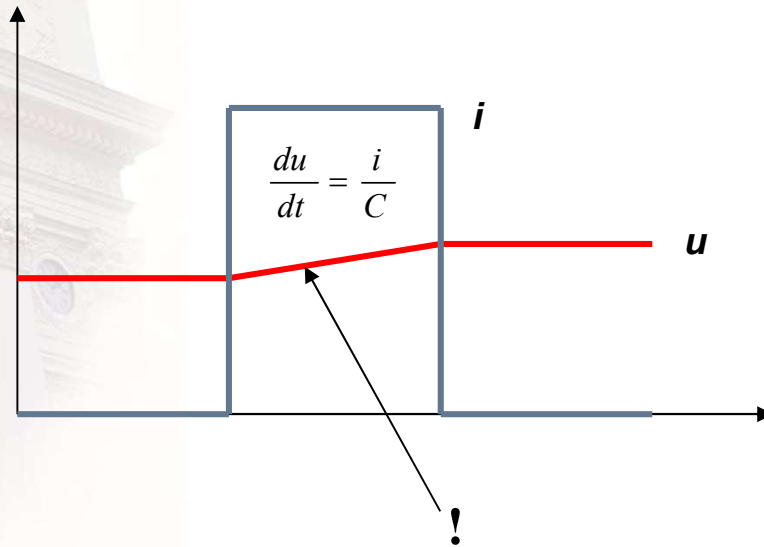

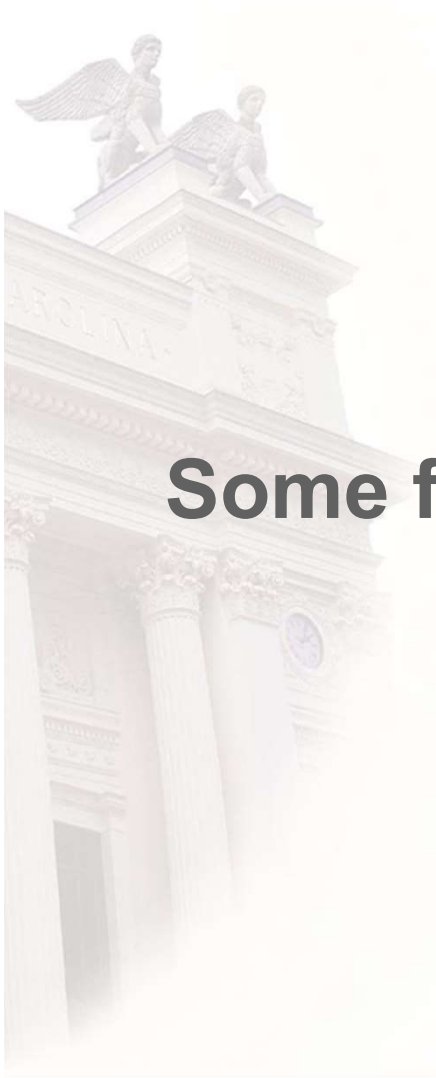


Some fundamental topologies


Quadrants

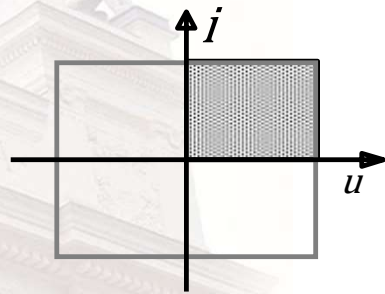


1-quadrant

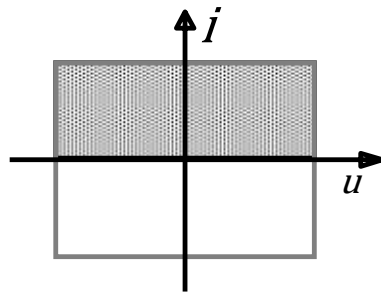


2-quadrant

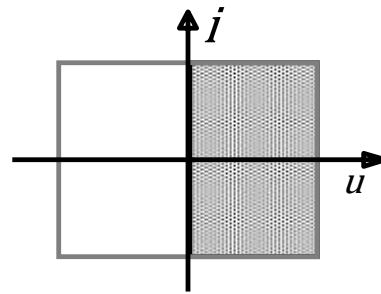

2-quadrant

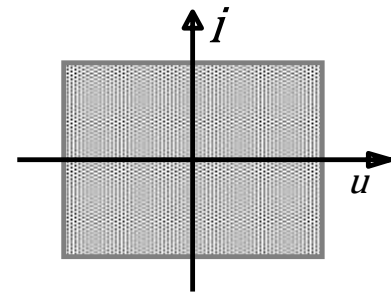


4-quadrant

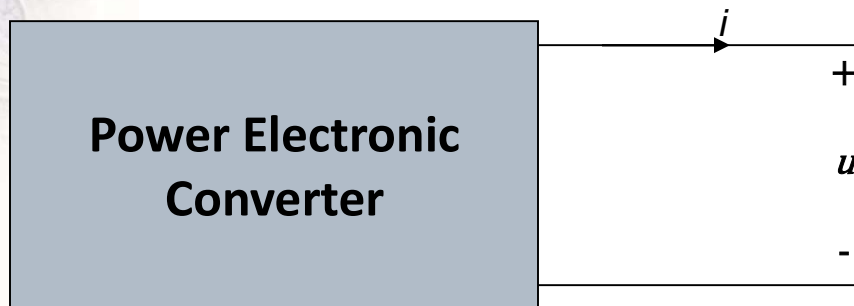

Classification

DC-voltage conversion

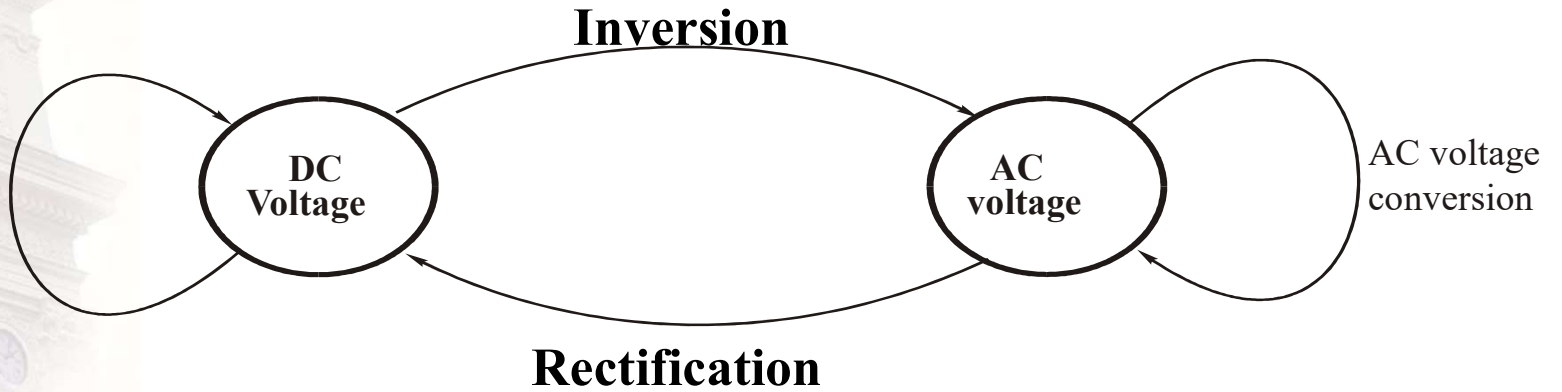


Converter topologies


Remember:

- 1 side capacitive
- 1 side inductive
- ALWAYS!



DC in

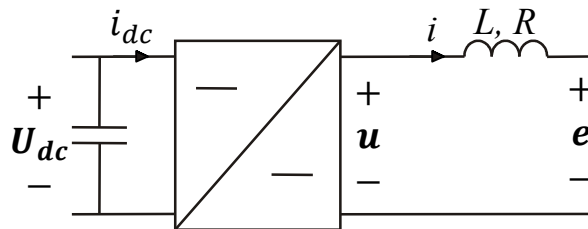

AC out

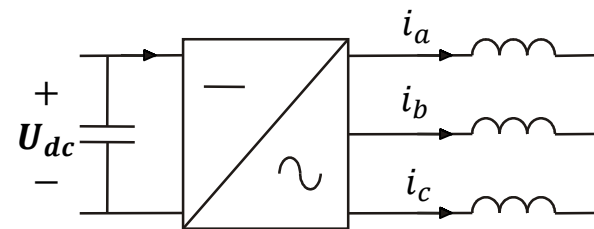


AC in

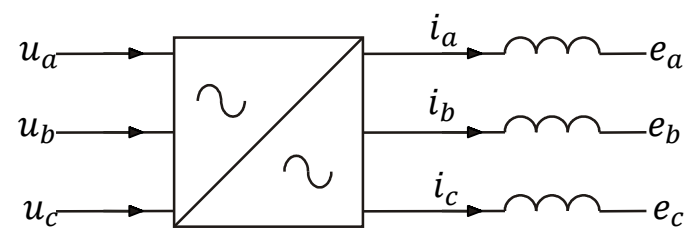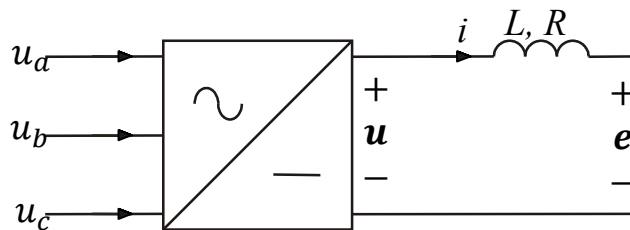



Modulation - Control of voltage time area

$$v_c = \begin{cases} v_a & \text{when } s = 1 \\ v_b & \text{when } s = 0 \end{cases}$$
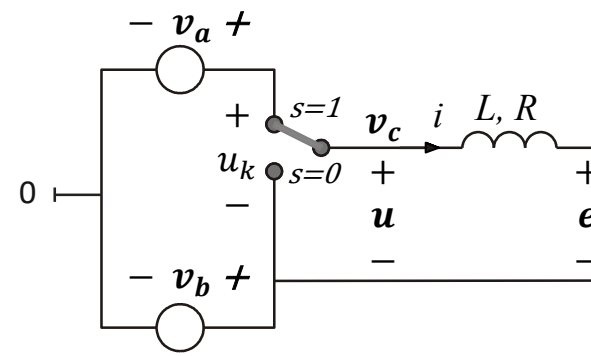
$$u = s \cdot (v_a - v_b) = s \cdot u_k = \begin{cases} u_k & \text{when } s = 1 \\ 0 & \text{when } s = 0 \end{cases}$$



Output voltage

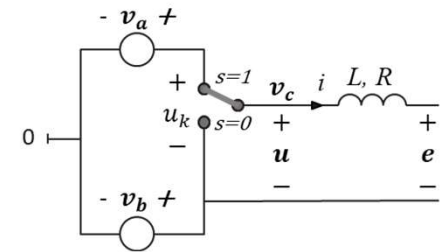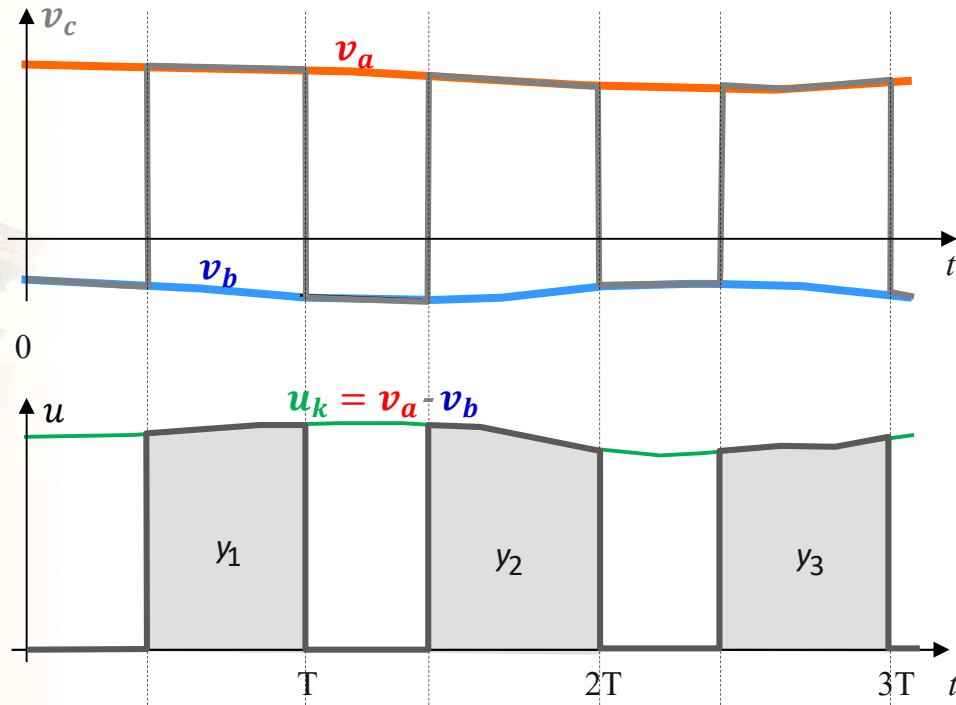






Voltage control options

Assume a limited pulse interval T and a slowly varying switching voltage u_k

$$Y_0 = \int_0^T u_k \cdot dt$$


$$u_k(\tau_+) = -\frac{dy(\tau_+)}{d\tau_+}$$
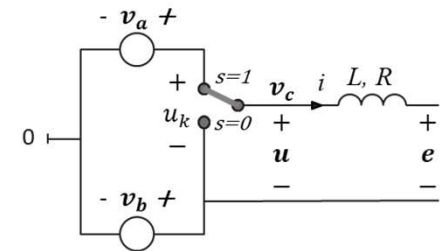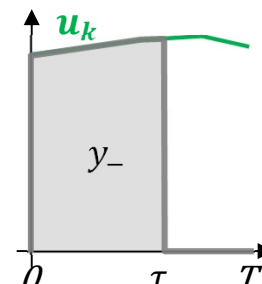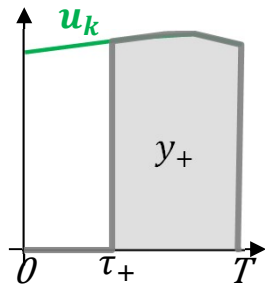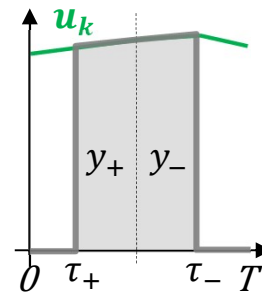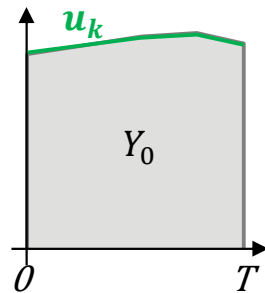
$$u_k(\tau_-) = \frac{dy(\tau_-)}{d\tau_-}$$




Control with positive flank
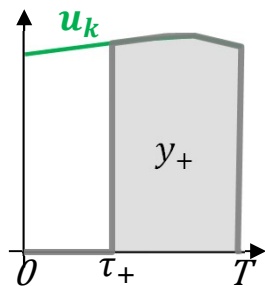
$$y(\tau_+) = \int_{\tau_+}^T u_k \cdot dt = Y_0 - \int_0^{\tau_+} u_k \cdot dt$$



Control with negative flank
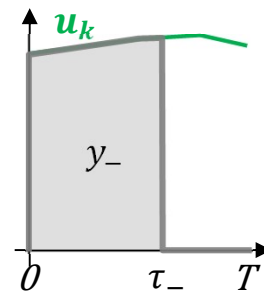
$$y(\tau_-) = \int_0^{\tau_-} u_k \cdot dt$$




Control with both flanks

$$Y_0 = \int_0^{T/2} u_k \cdot dt$$

$$y(\tau_+, \tau_-) = y_+ + y_-$$




$$y_+ = \int_{\tau_+}^{T/2} u_k \cdot dt = Y_0 - \int_0^{\tau_+} u_k \cdot dt$$
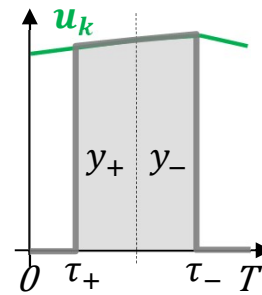
$$y_- = \int_{T/2}^{T/2+\tau_-} u_k \cdot dt$$



Carrier wave modulation

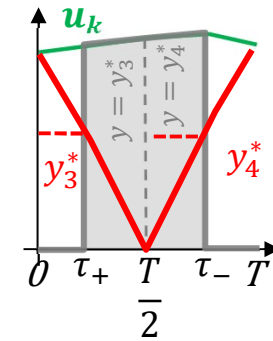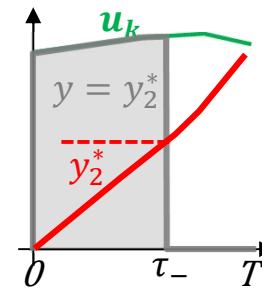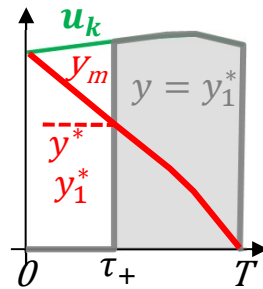- A reference value y^* for the desired average voltage over one switching period is calculated by an external control system
- A modulation signal y_m is generated, such that $y(t)=y_m(t)$
- The reference is compared to the modulation signal to determine the switching instants.




Voltage time area vs. average voltage

- This far the modulation has been described with **voltage time areas**, both regarding the estimate of the output voltage time area as a function of the switching time instant, i.e. the modulating wave y_m , and the references for the output voltage time areas y^* .
- In the following sections and chapters, voltage time area is replaced with average voltages.

$$u_m = \frac{y_m}{T_s}$$
$$u^* = \frac{y^*}{T_s}$$











The modulator


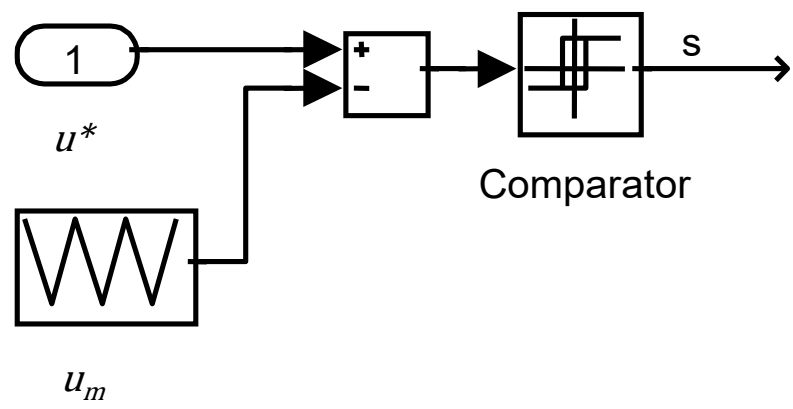






PWM-controlled dc converters

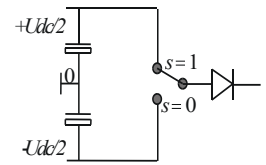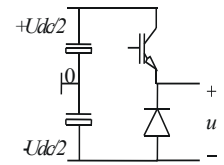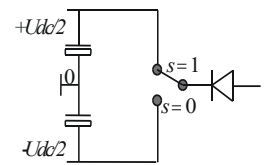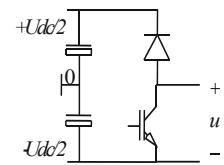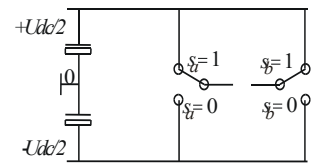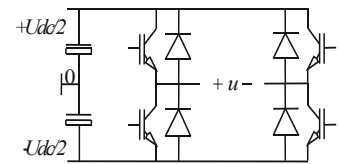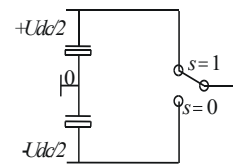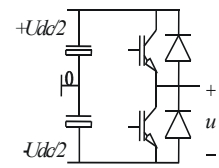

Two quadrant DC converters : I

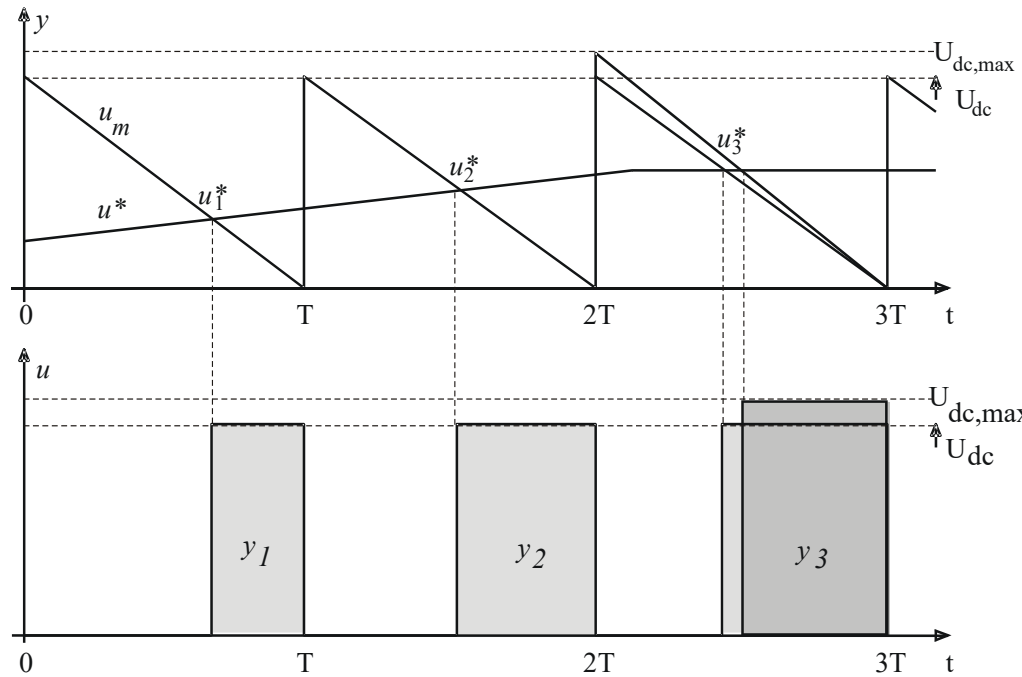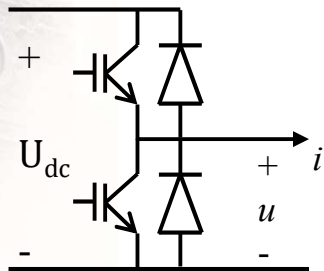


Two quadrant DC converters : II

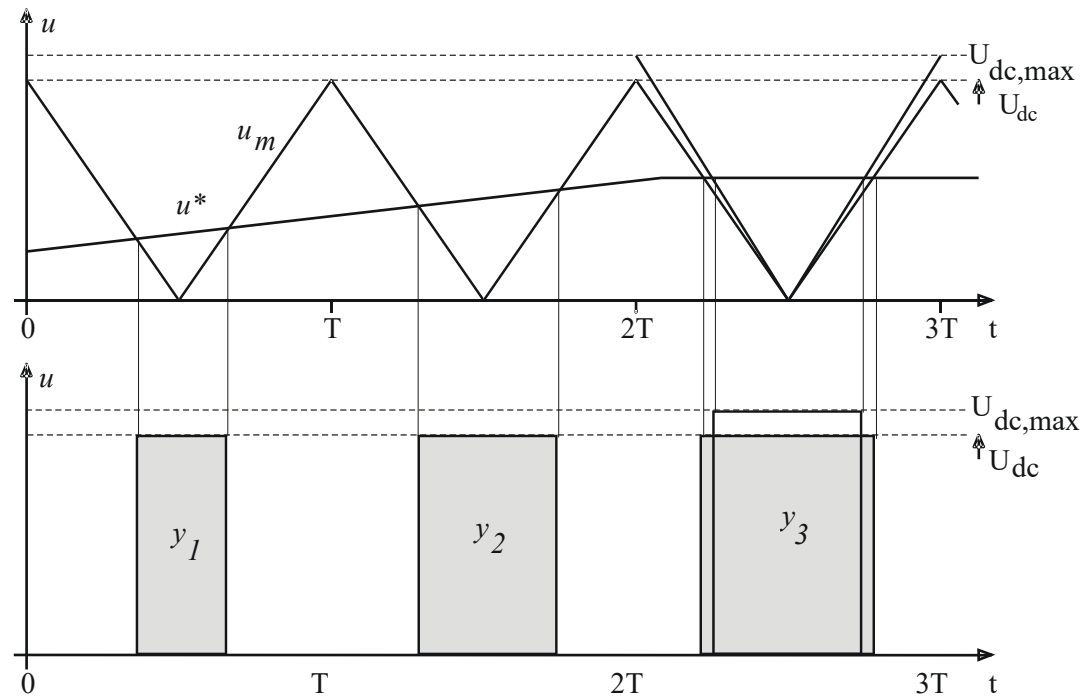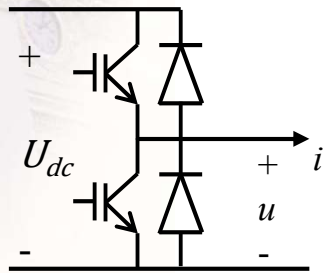


2-quadrant DC converters : III

Current sampling – how often?


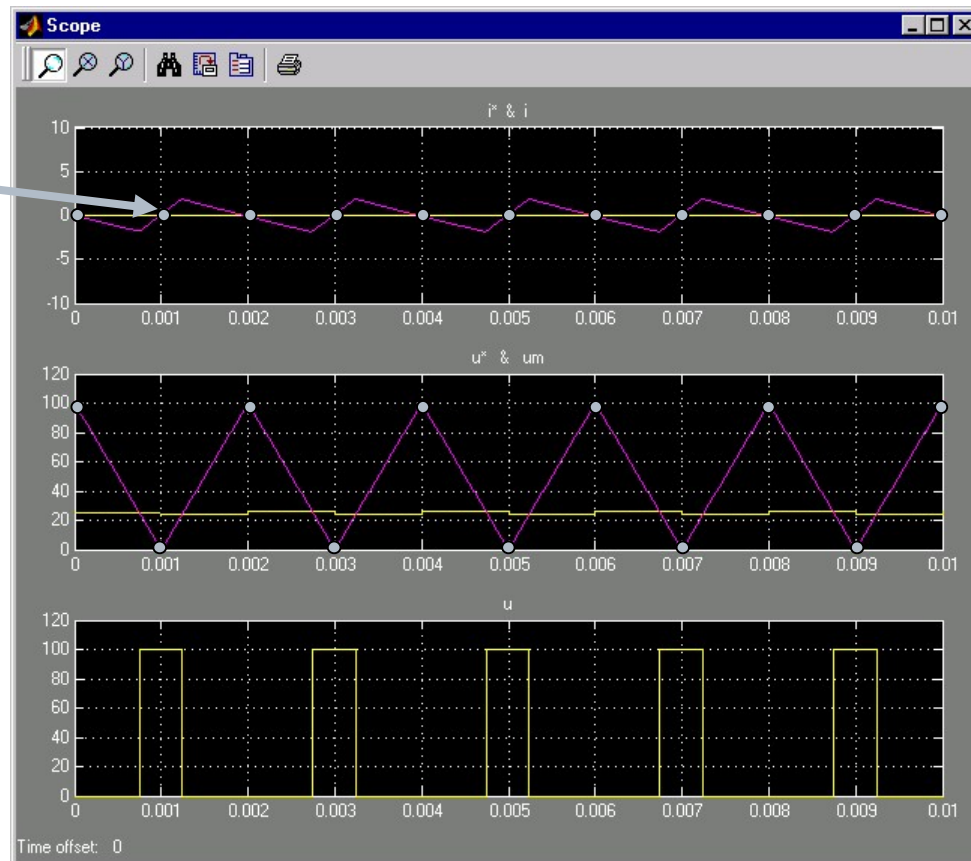
- When the carrier turns, i.e.
With twice the switching
frequency!



Example

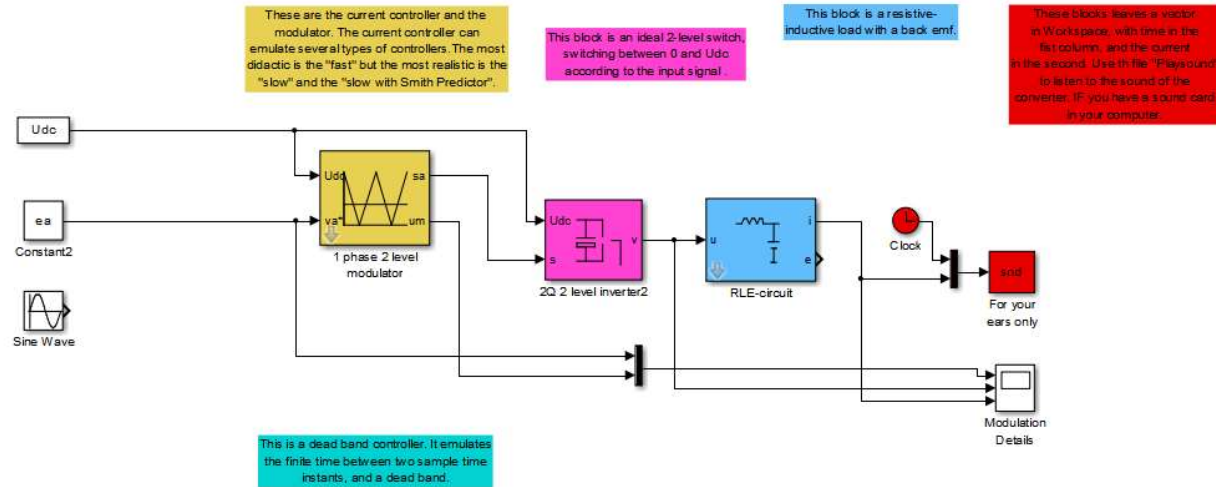


Blanking Time

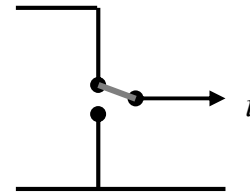
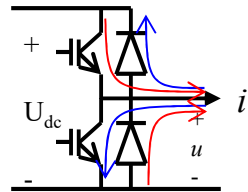


$i < 0$

$i > 0$


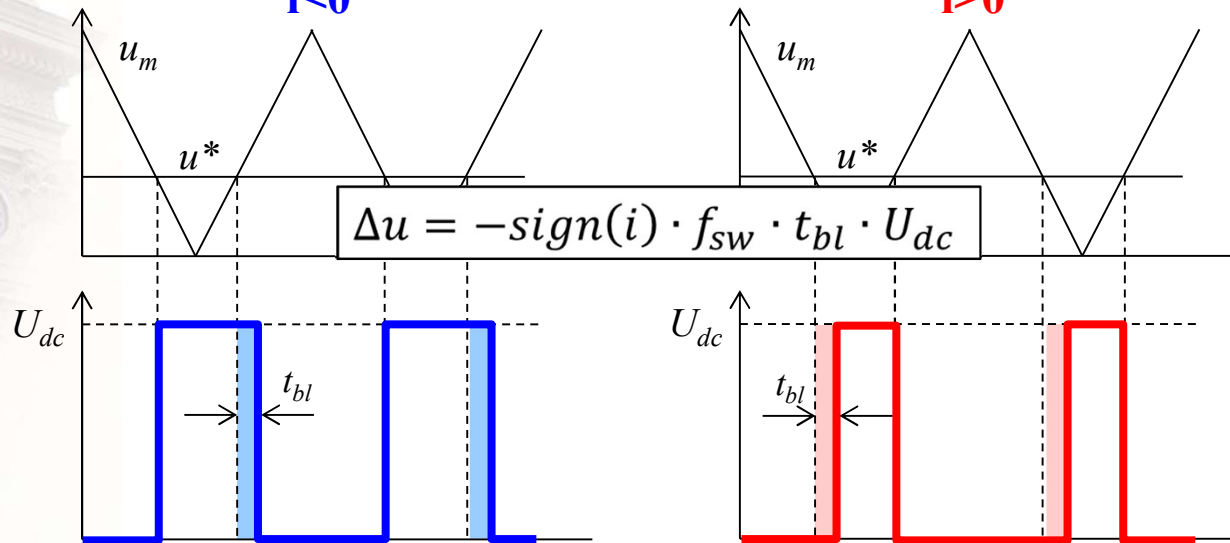


Blanking Time + Voltage Drops

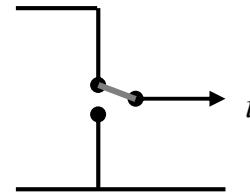
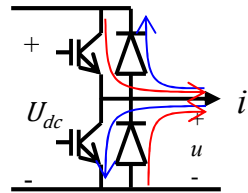


$i < 0$

$i > 0$

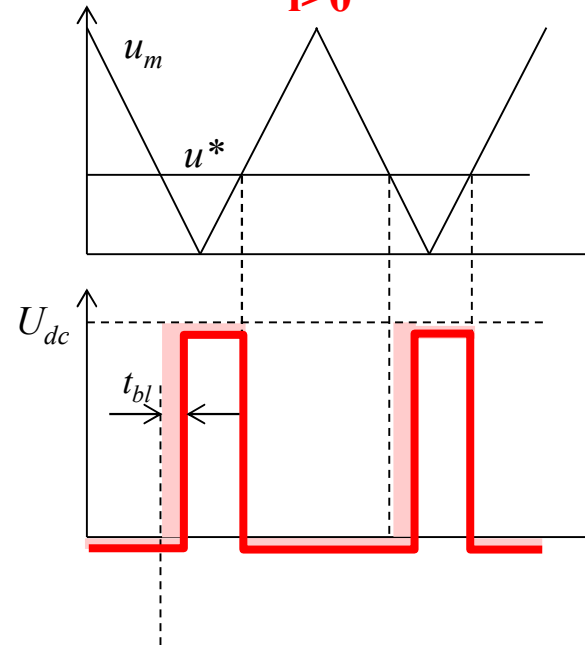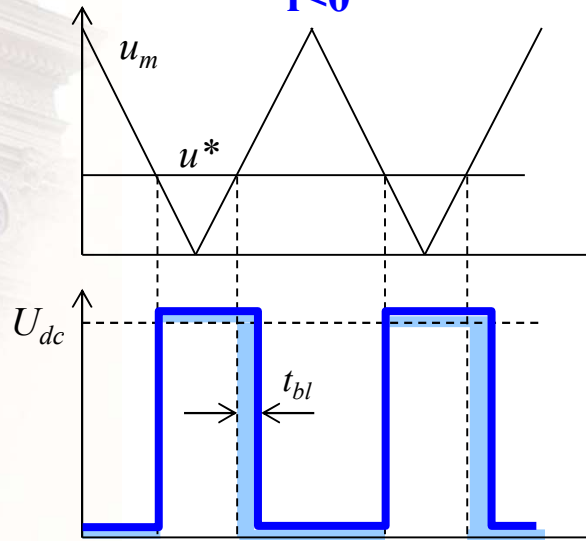

4 – quadrant DC converters

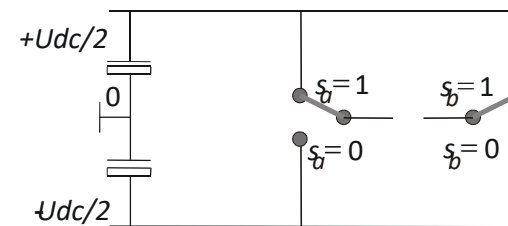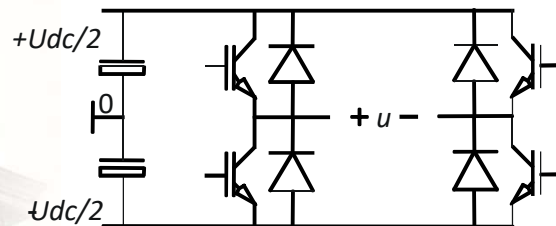

- Bridge connected
- 2 phase potentials:
 - *Only 1 output voltage = 1 degree of freedom to be used for other purposes.*

4-quadrant DC converters


$$u^* = v_a^* - v_b^*$$

$$\text{alt1: } v_a^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} \Rightarrow v_b^* = v_a^* - u^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} - u^*$$

$$\text{alt2: } v_a^* = -v_b^* \Rightarrow v_a^* - v_b^* = 2 \cdot v_a^* \Rightarrow \begin{cases} v_a^* = \frac{u^*}{2} \\ v_b^* = -\frac{u^*}{2} \end{cases}$$




4-quadrant DC converters – alt 1

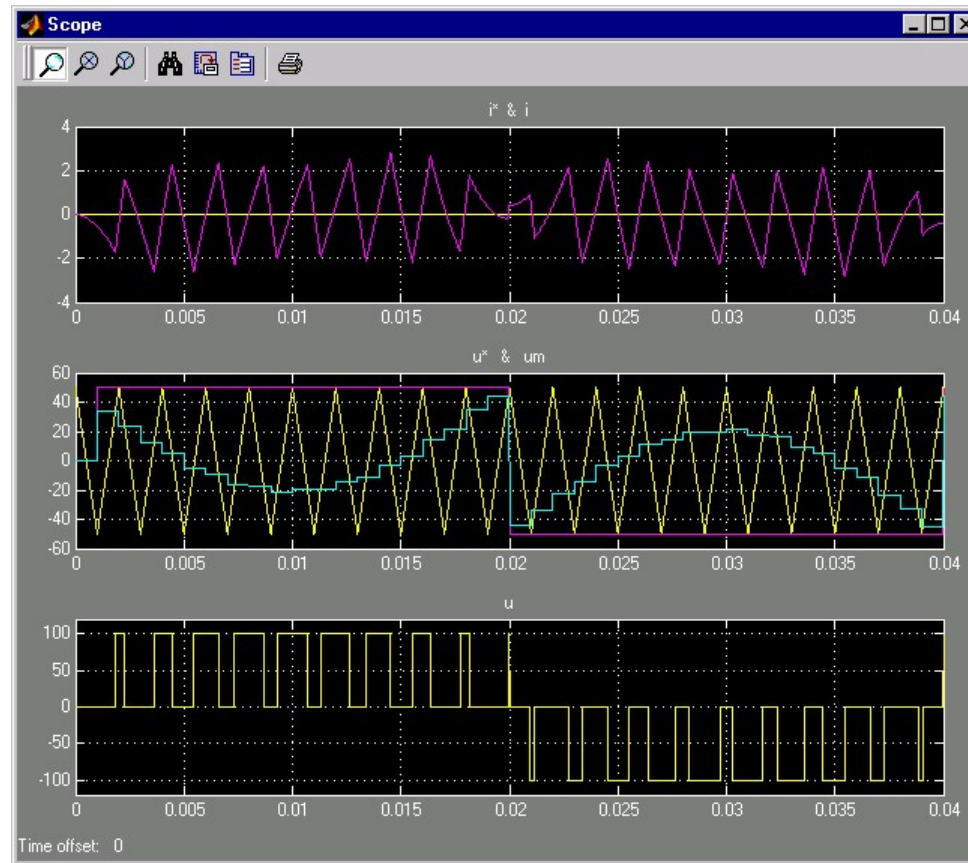




4-quadrant DC converters – alt 2

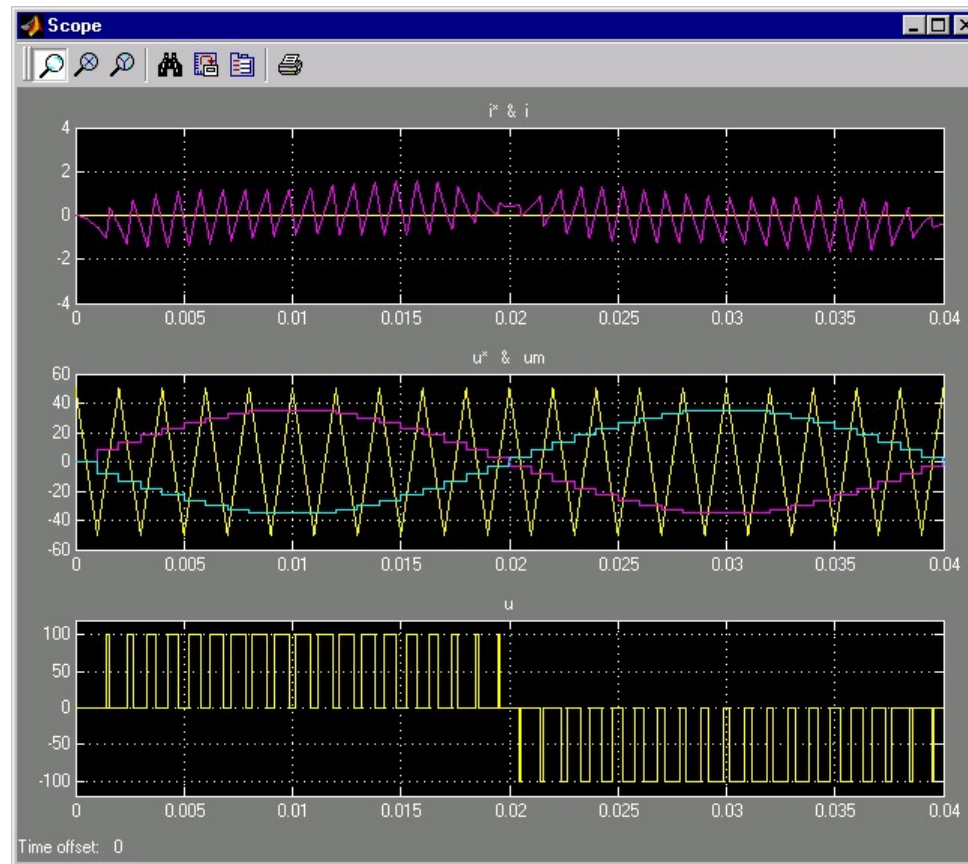



Example

- Sampling and symmetry ...

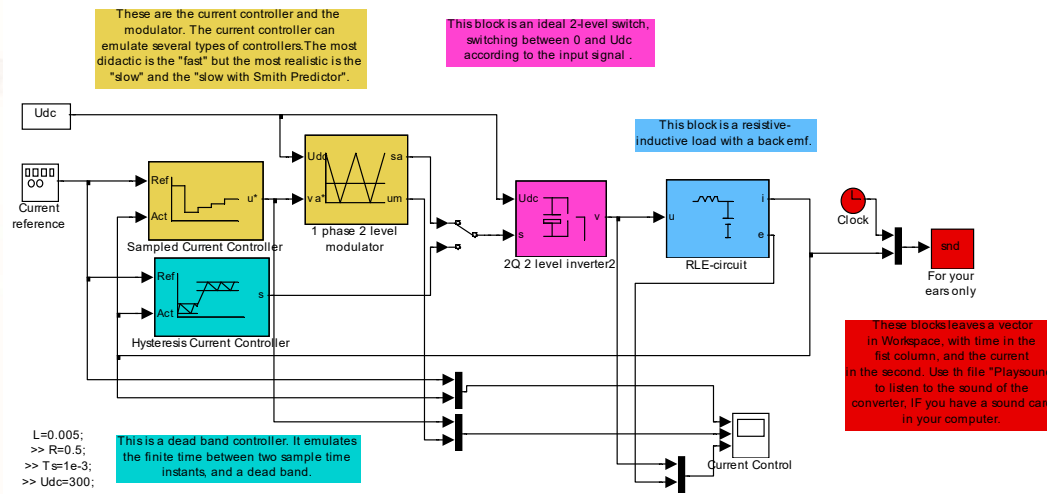

2-Q DC converters

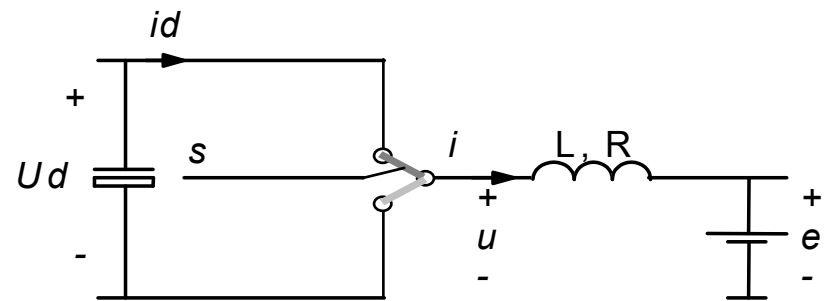
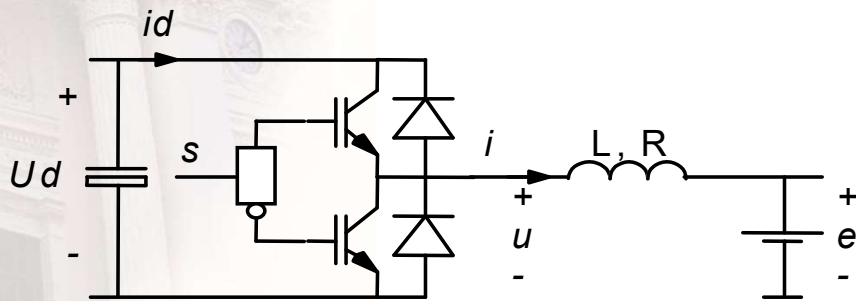
- Bidirectional power
 - $u > 0$, i bidirectional
- Equivalent switch:




Modulation of a 2Q DC converter

- Only positive output voltages
- Currents both positive and negative
- Example:
 - $U_{dc}=600$;
 - $L_a=1e-3$;
 - $R_a=0.1$;
 - $e_a=400$;
 - $T_s=100e-6$
 - $u^* = 400 + R_a \cdot 10$
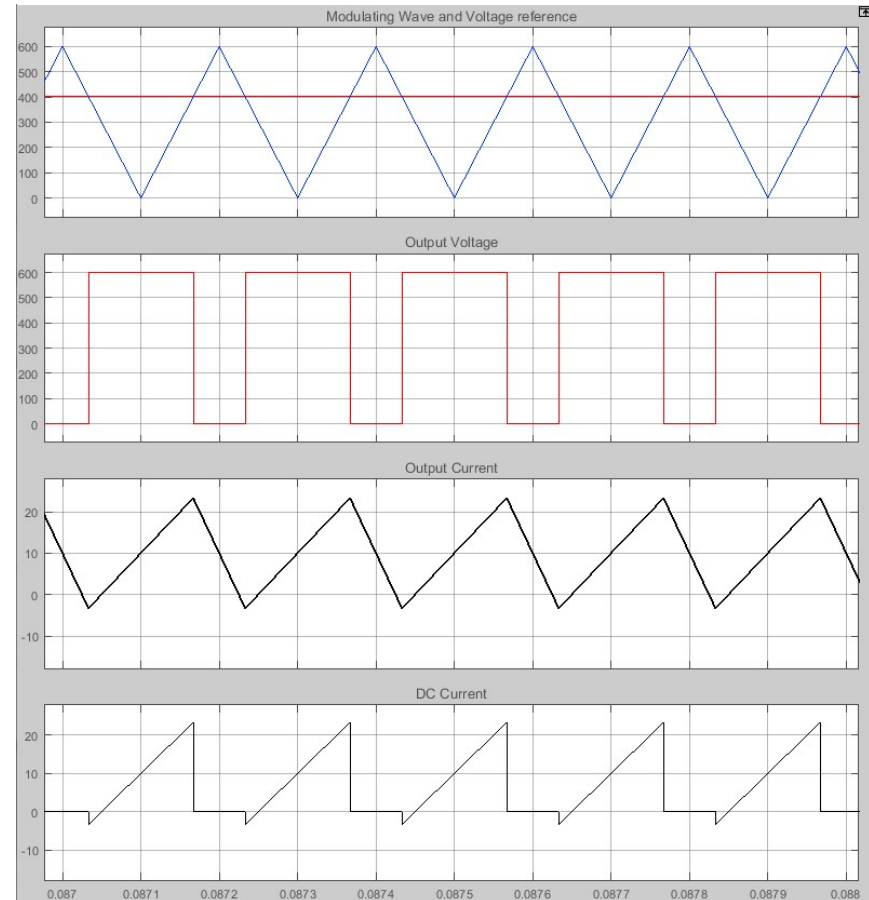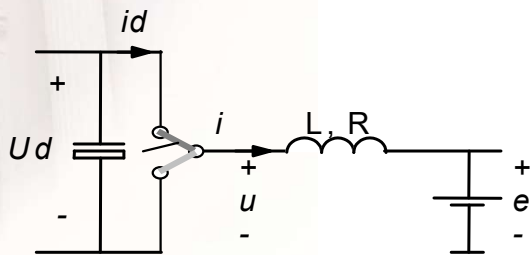
$$\frac{di}{dt} = \frac{(u - e - R \cdot i)}{L}$$



To Simulink

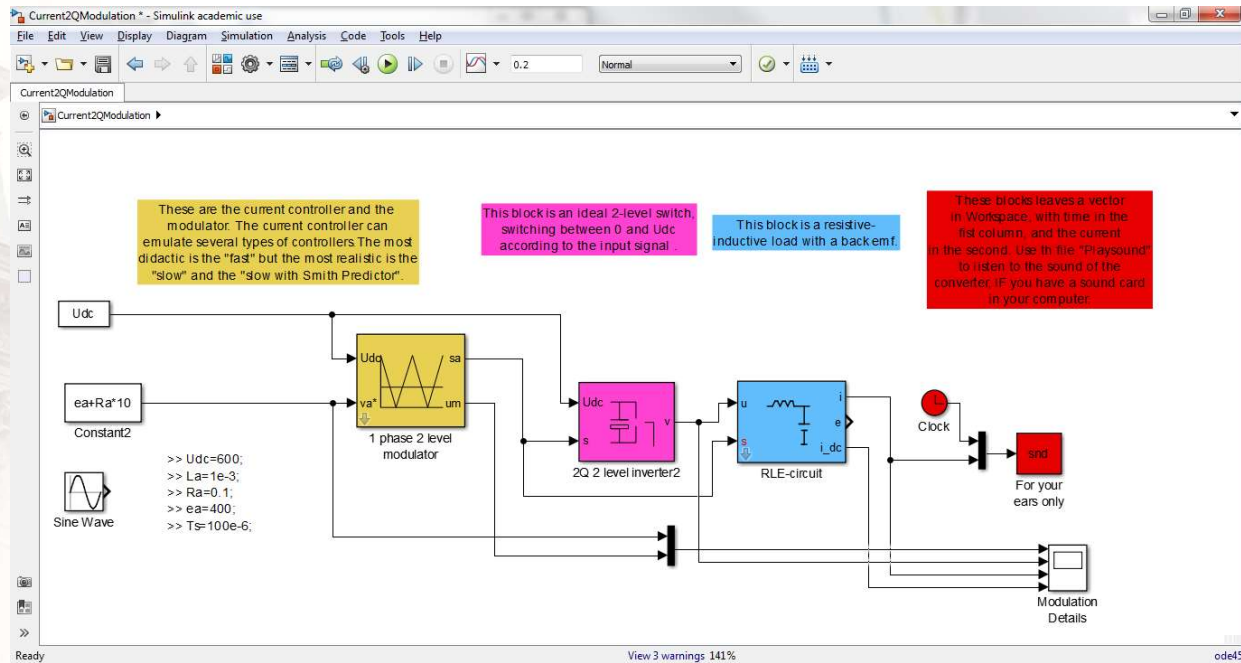

One more 2Q example

- To reduce current ripple
- Example:
 - $U_{dc}=600$;
 - $L_a=1e-3$;
 - $R_a=0.1$;
 - $e_a=400$;
 - $T_s=25e-6$ (much higher switching frequency)
 - $u^* = 400 + R_a \cdot i$
- DC side: PWM current
- AC side: PWM voltage

