

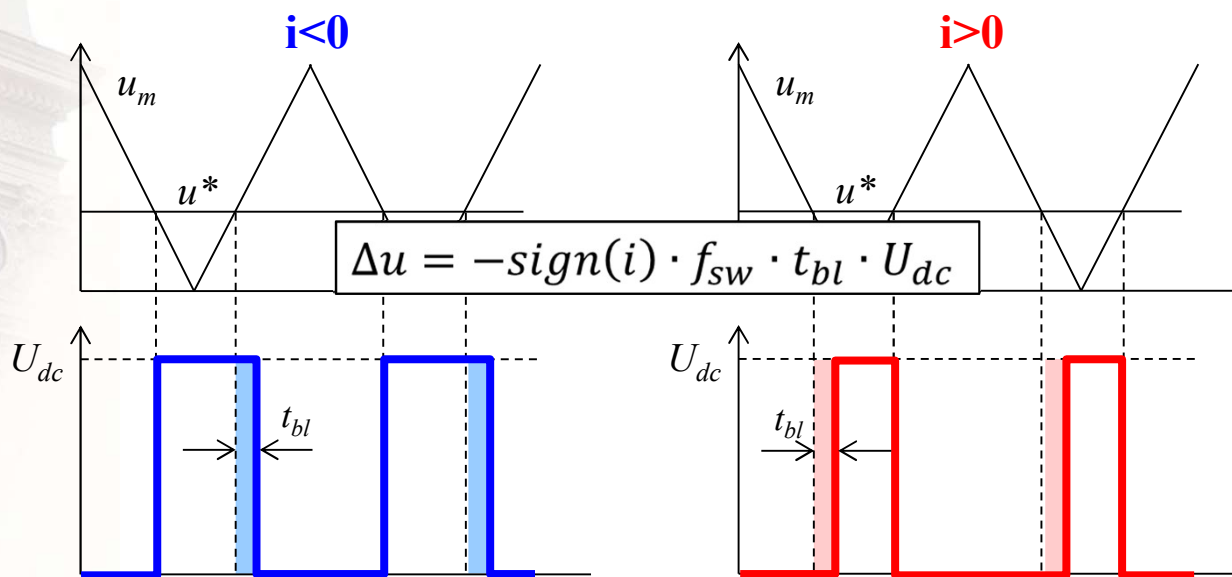


Lecture 4 – 4Q converter and modulation




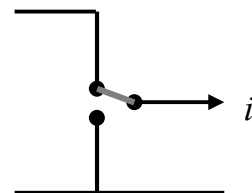


Electric Drives Control

Blanking Time

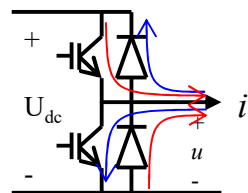

Blanking Time + Voltage Drops

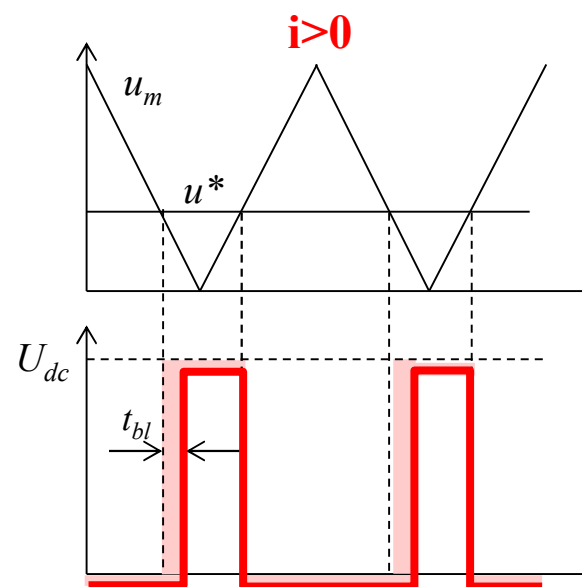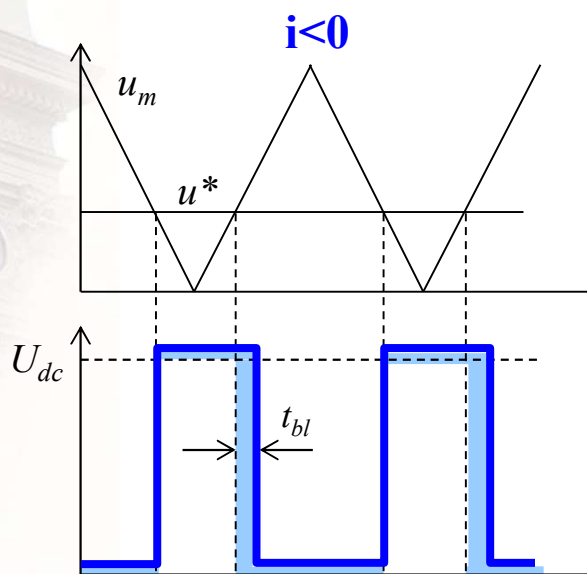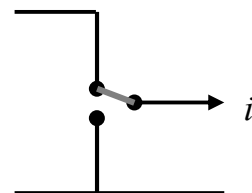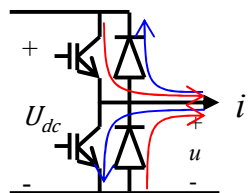


Modulation of a 4Q converter

- 1 output voltage, 2 phase potentials
->infinite number of combinations of v_a^* och v_b^* gives $u = v_a - v_b$.
- 2 clear alternatives:

$$u^* = v_a^* - v_b^*$$


$$\text{alt1: } v_a^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} \Rightarrow v_b^* = v_a^* - u^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} - u^*$$
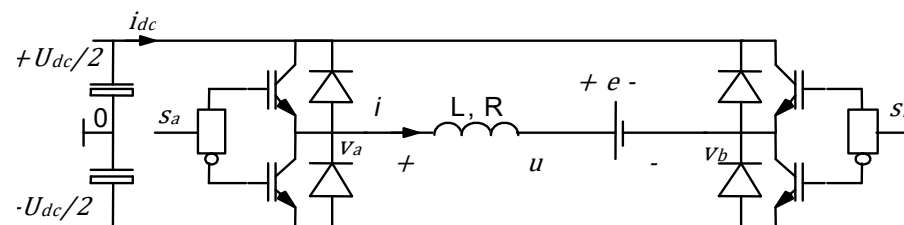
$$\text{alt2: } v_a^* = -v_b^* \Rightarrow v_a^* - v_b^* = 2 \cdot v_a^* \Rightarrow \begin{cases} v_a^* = \frac{u^*}{2} \\ v_b^* = -\frac{u^*}{2} \end{cases}$$




$$\frac{di}{dt} = \frac{(u - e)}{L}$$

4-quadrant DC converters – alt 1

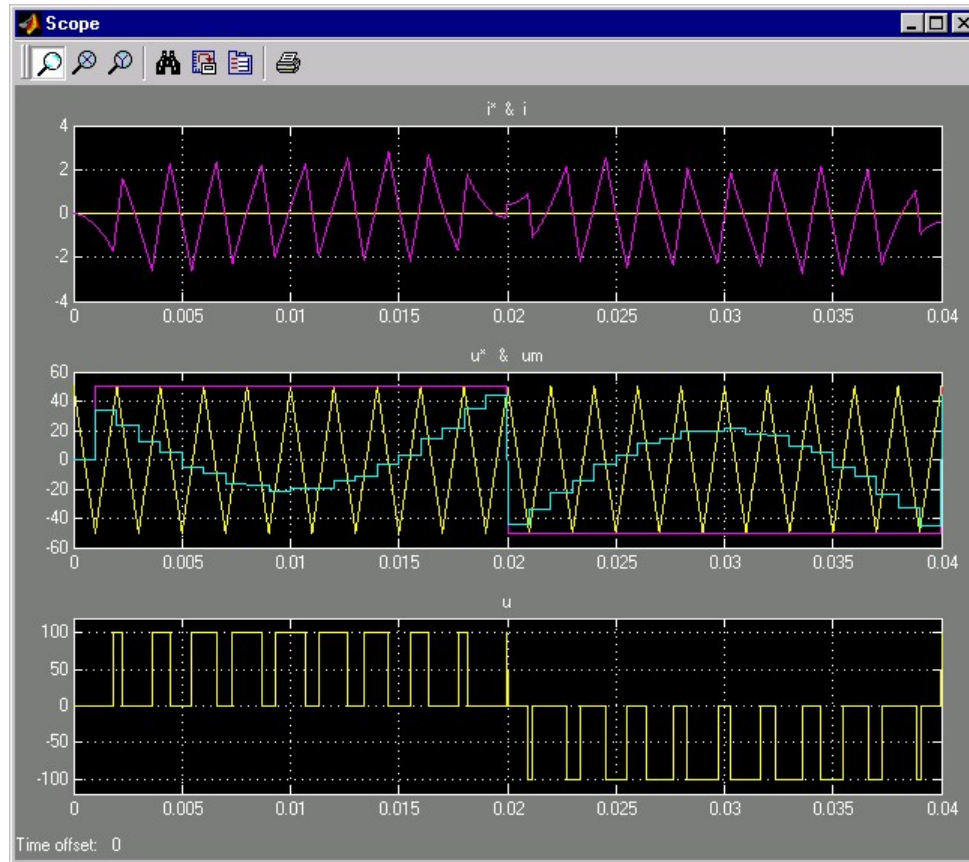

4-quadrant DC converters – alt 2

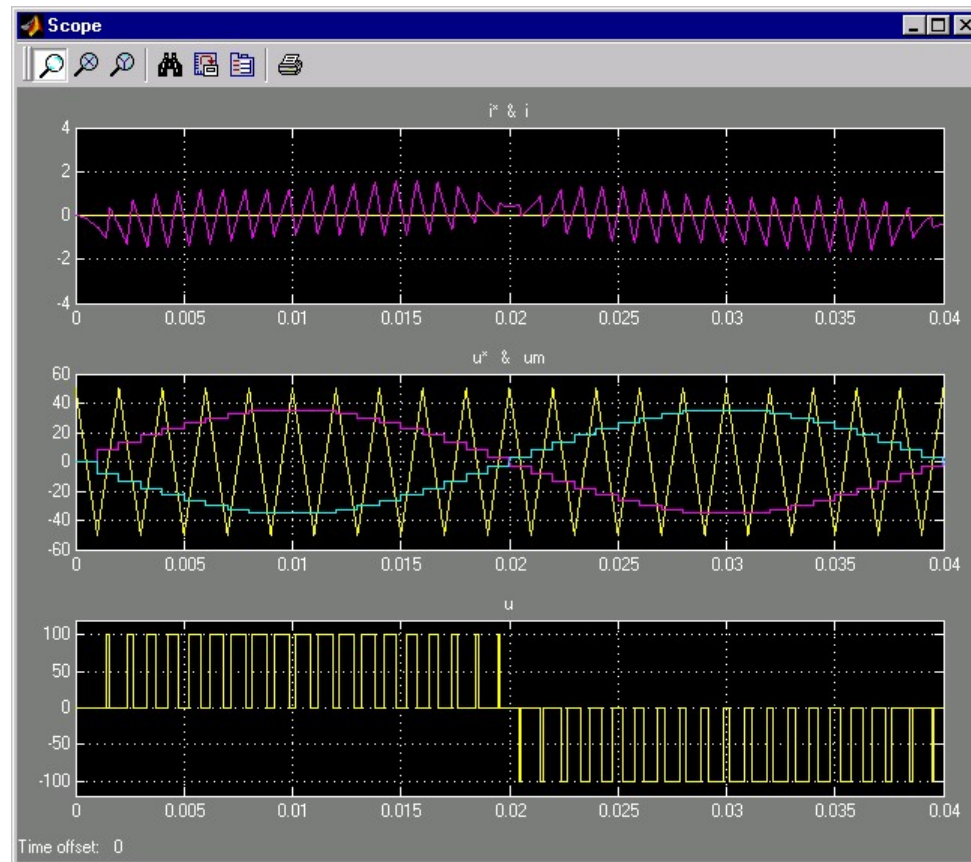

Electric Drives Control


Modulation of a 4Q converter

- 1 output voltage, 2 potentials -
 >infinite number of combinations of v_a^* och v_b^* gives $u = v_a - v_b$.
- 2 clear alternatives:

$$u^* = v_a^* - v_b^*$$

$$\text{alt1: } v_a^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} \Rightarrow v_b^* = v_a^* - u^* = \text{sign}(u^*) \cdot \frac{U_{dc}}{2} - u^*$$
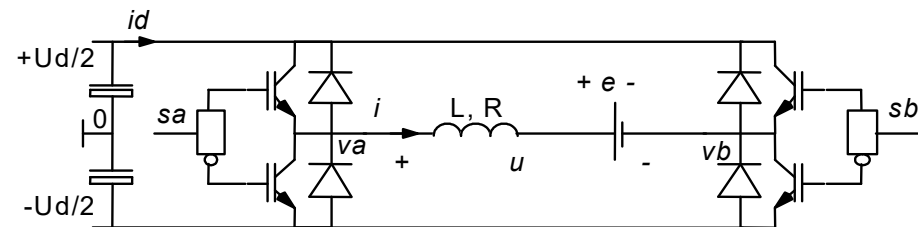
$$\text{alt2: } v_a^* = -v_b^* \Rightarrow v_a^* - v_b^* = 2 \cdot v_a^* \Rightarrow \begin{cases} v_a^* = \frac{u^*}{2} \\ v_b^* = -\frac{u^*}{2} \end{cases}$$




$$\frac{di}{dt} = \frac{(u - e)}{L}$$

Modulation of a 4Q DC converter: DC voltage

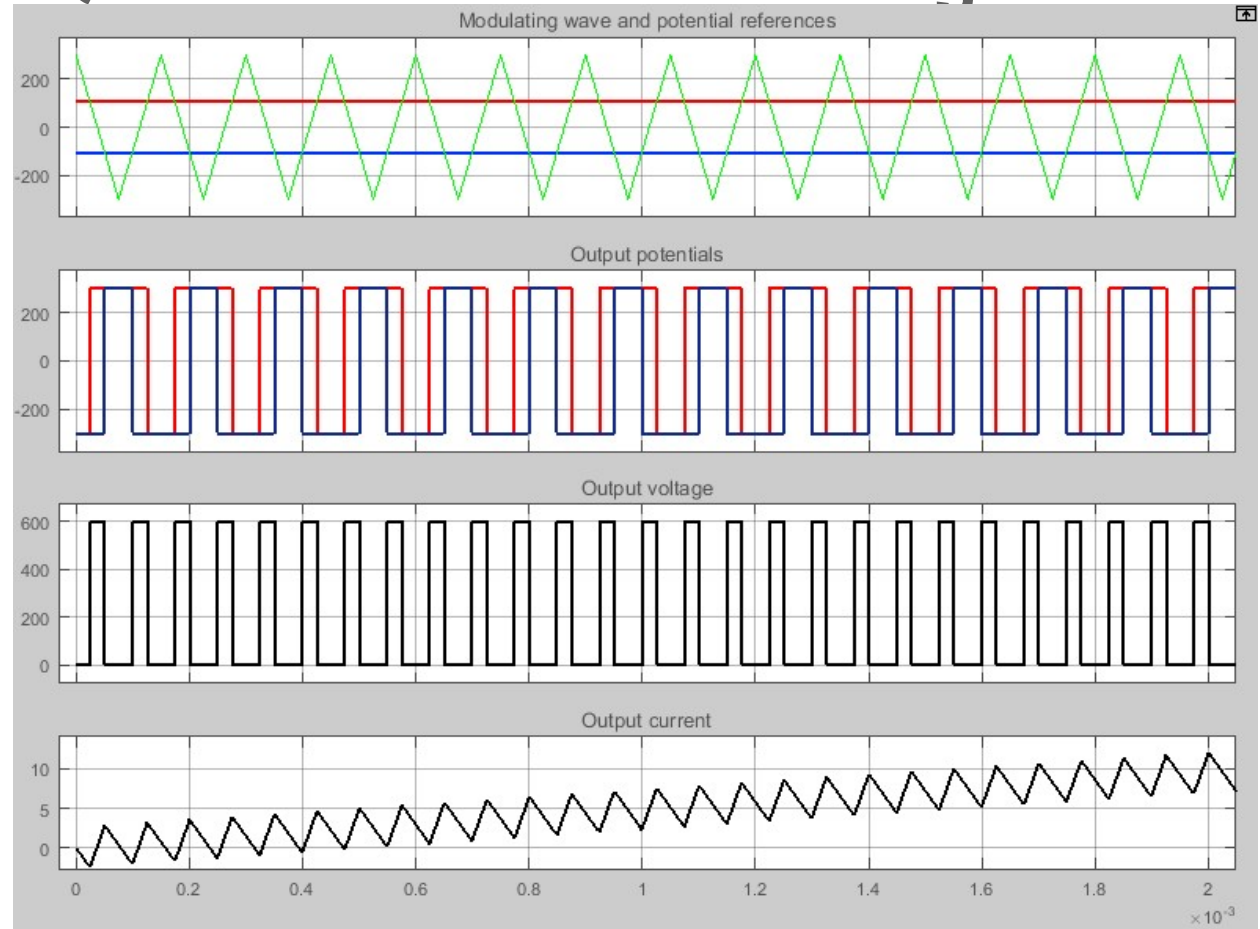- **Example:**

- $U_{dc} = 600 [V]$
- $R_a = 0.1 [Ohm]$
- $e_a = 200 [V]$
- $L = 2 [mH]$
- **Switchfrequency: 6.67 [kHz]**
- **Assume 100 A (20 kW)**
- $u^* = e_a + R_a \cdot 100$
- **First two milliseconds:**



Modulation of a 4Q DC converter: DC voltage


- **Example:**

- $U_{dc} = 600$ [V]
- $R_a = 0.1$ [Ohm]
- $e_a = 200$ [V]
- $L = 2$ [mH]
- Switchfrequency: 6.67 [kHz]
- Assume 100 A (20 kW)
- $u^* = e_a + R_a \cdot 100$

- **First two milliseconds:**

- **Notice:**

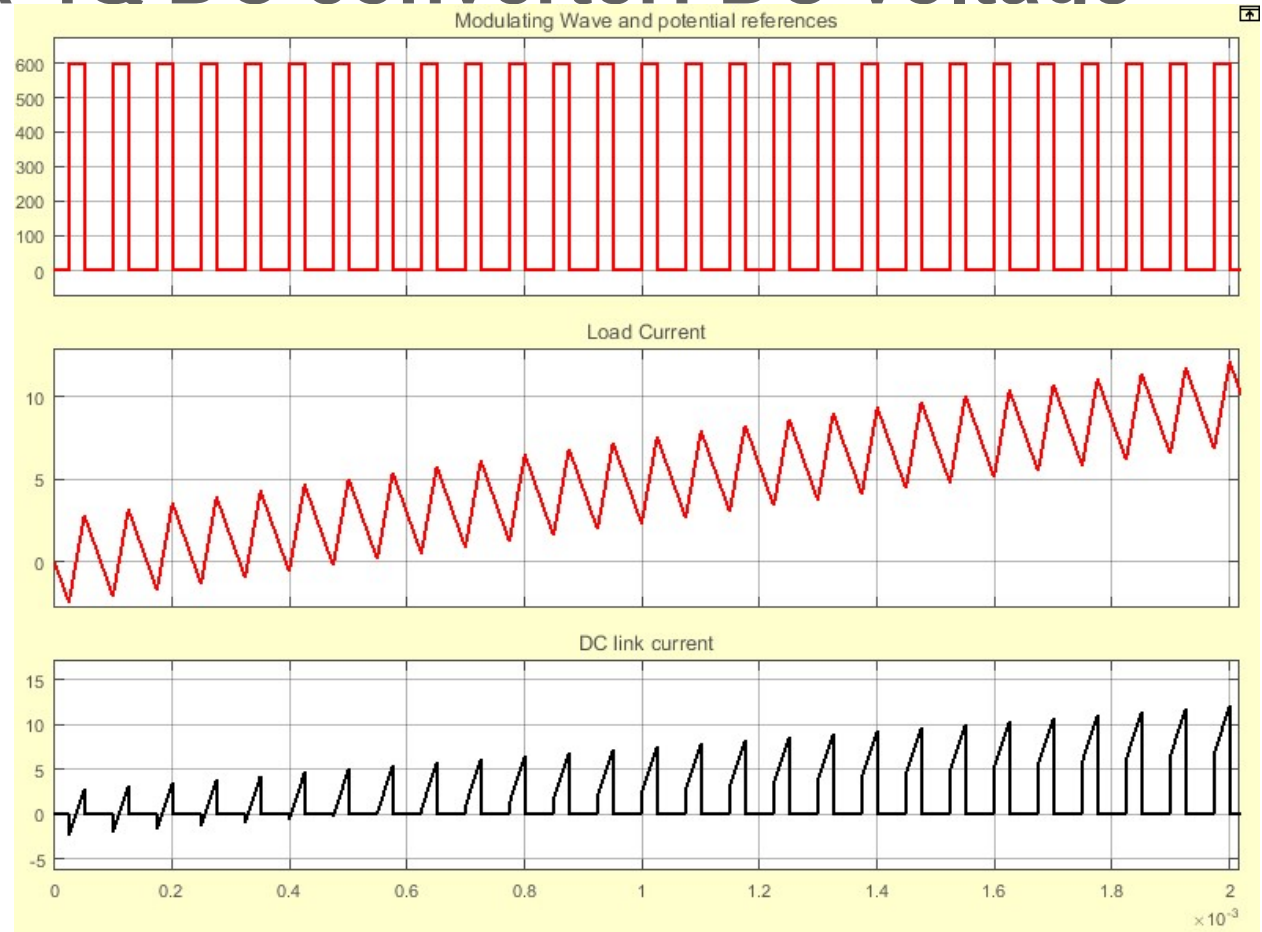- DC-side: PWM current
- AC side: PWM voltage
- DC side: instantaneous power, but average (almost) zero, due to *mainly reactive load*.
- **DC side current negative if load current is negative**



Exercise: Modulation of a 4Q converter

- Given:

- $U_{dc} = 600\text{ V}$
- $e = 200\text{ V}$
- $i(t=0) = 0$
- Voltage reference given

- Parameters:

- $L = 2\text{ [mH]}$
- Switchfrekvens: 6.67 [kHz]

- Draw:



- Potentials v_a and v_b
- Load voltage u

- Calculate

- Positive current derivative
- Negative current derivative



- Draw

- Load current i

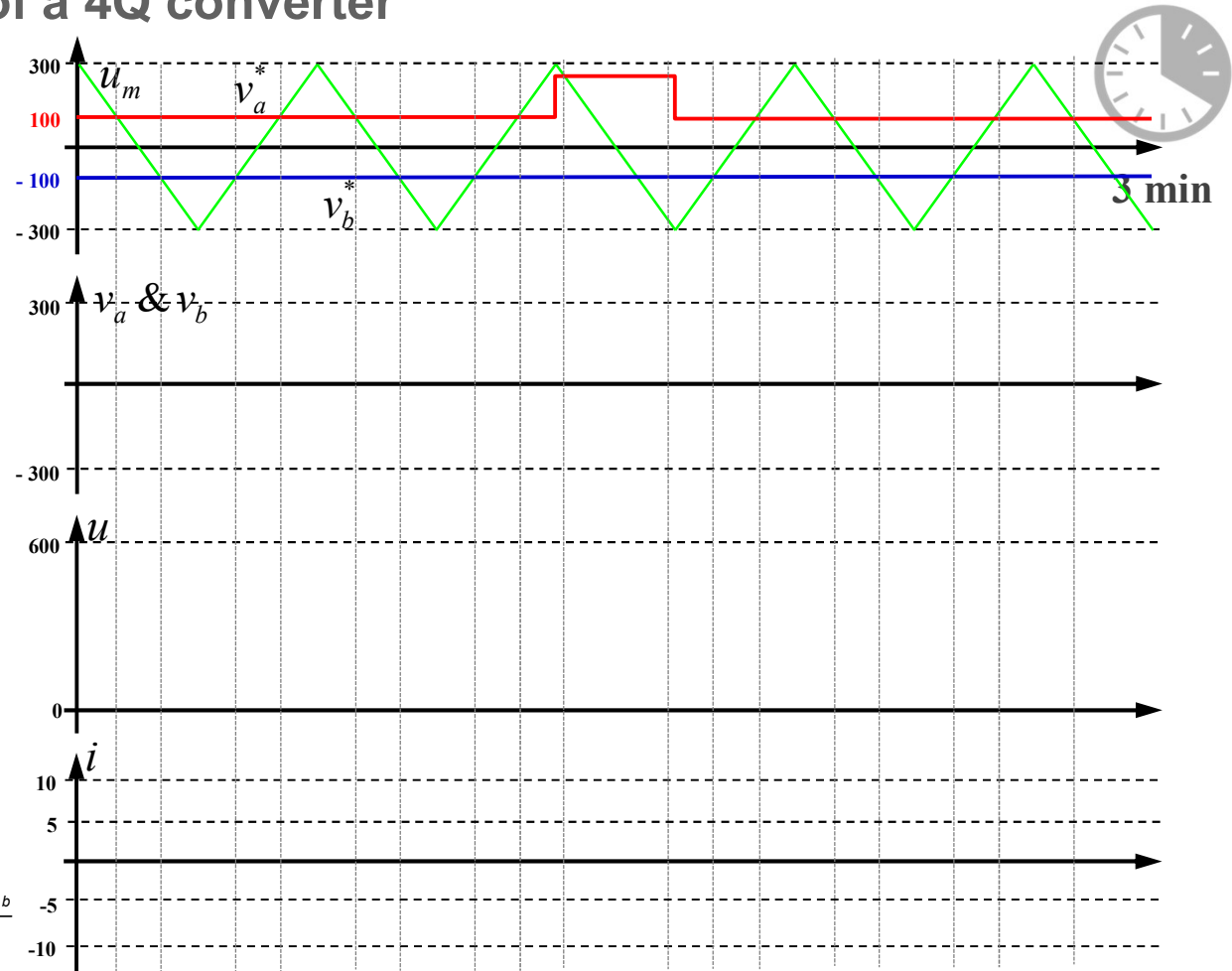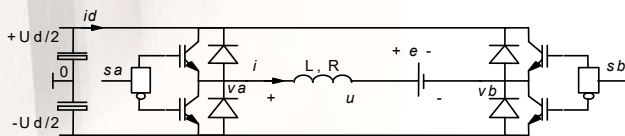

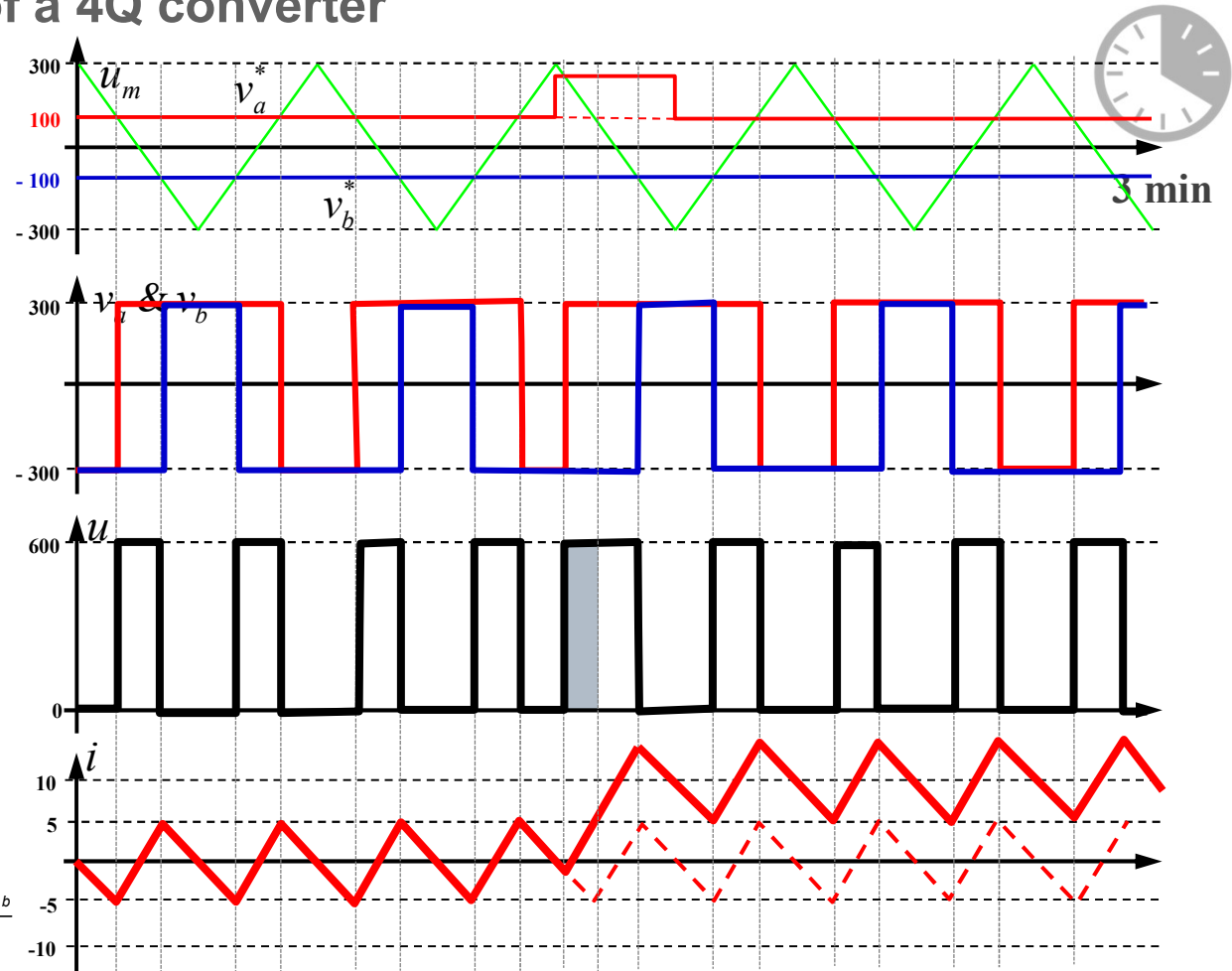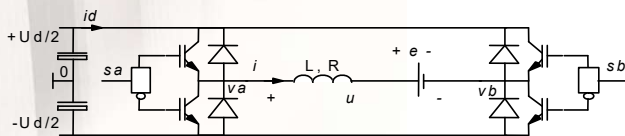Exercise: Modulation of a 4Q converter

- **Given:**
 - $U_{dc} = 600\text{ V}$
 - $e = 200\text{ V}$
 - $i(t=0) = 0$
 - Voltage reference given
- **Parameters:**
 - $L = 2\text{ [mH]}$
 - Switchfrekvens: 6.67 [kHz]
- **Draw:**
 - Potentials v_a and v_b
 - Load voltage u
- **Calculate**
 - Positive current derivative
 - Negative current derivative
- **Draw**
 - Load current i




Modulation of a 4Q DC converter: AC voltage

- **Example:**

- $U_{dc} = 600 [V]$
- $e_a = 0 [V]$
- $L_a = 2 [mH]$
- $R_a = 0.1 [Ohm]$
- Switchfrekvens: 6.67 [kHz]
- $U_{ref} = 400 [V]; 500 [Hz]$

- **First 5 milliseconds:**

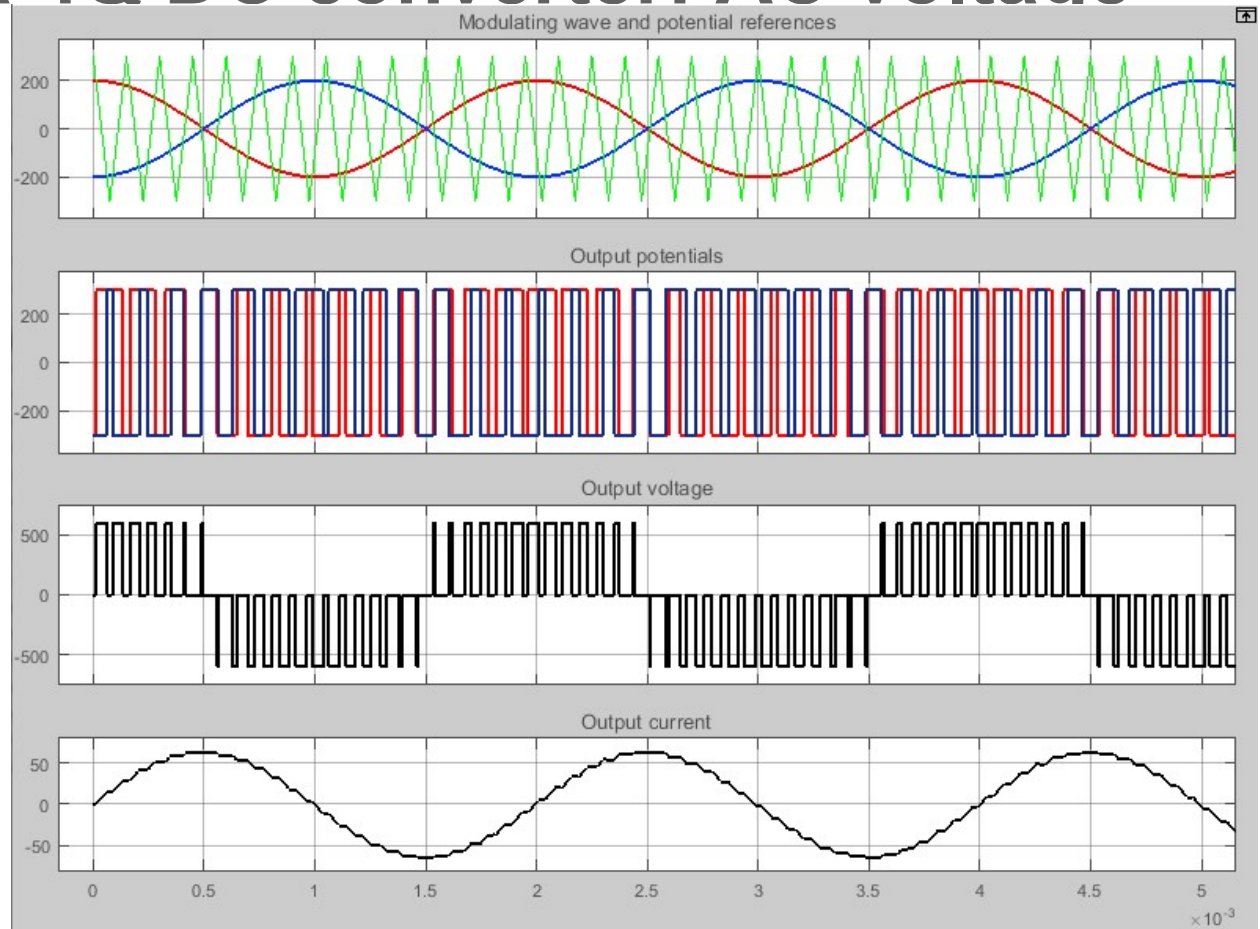

Modulation of a 4Q DC converter: AC voltage


- **Example:**

- $U_{dc} = 600 [V]$
- $e_a = 0 [V]$
- $L_a = 2 [mH]$
- $R_a = 0.1 [Ohm]$
- Switchfrekvens: $6.67 [kHz]$
- $U_{ref} = 400 [V]; 500 [Hz]$

- **First 5 milliseconds:**

- **Notice:**

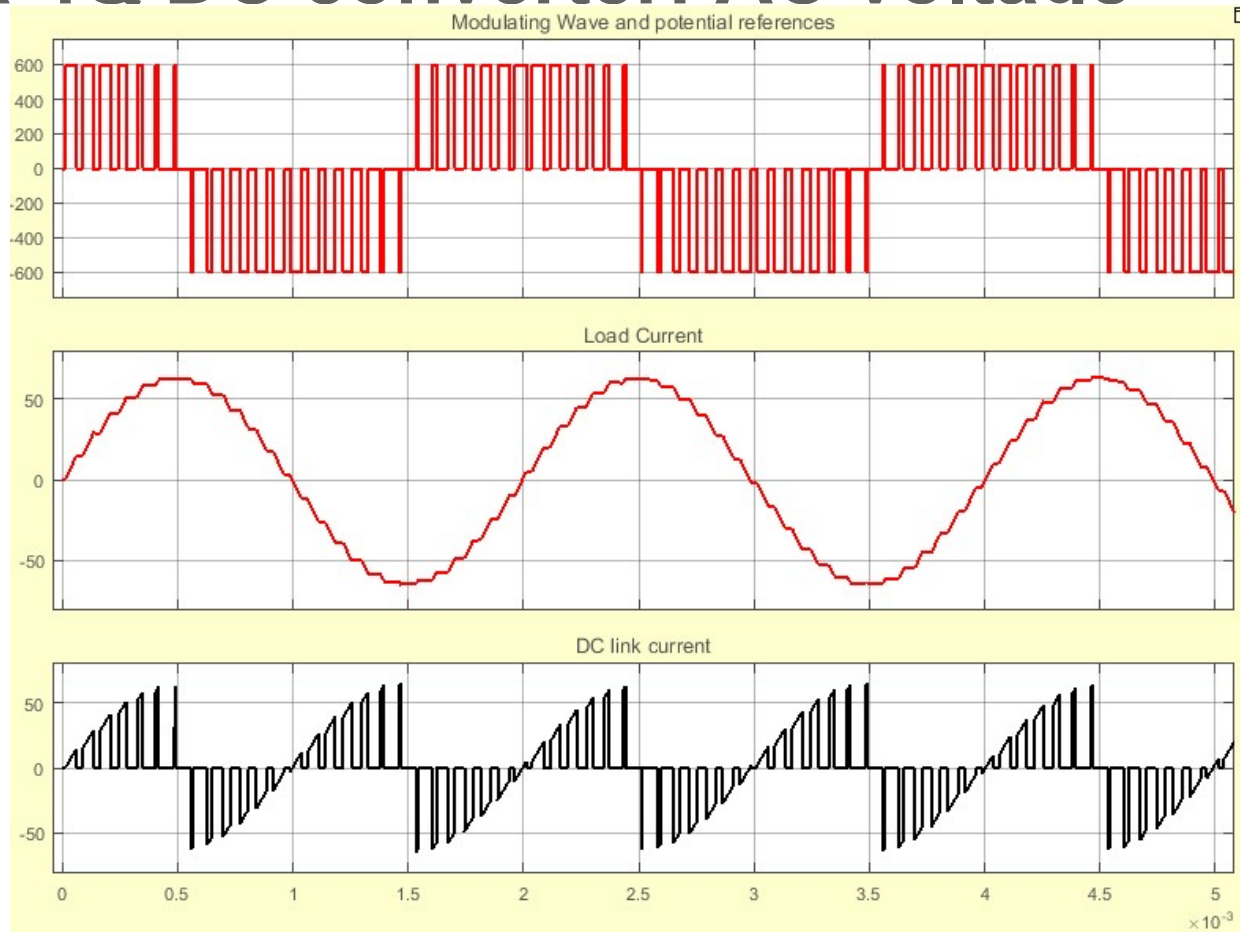- DC-side: PWM current
- AC side: PWM voltage
- DC side: instantaneous power, but average (almost) zero, due to *maily reactive load*.




Modulation of a 4Q DC converter: AC voltage

- **Example:**

- $U_{dc} = 600$ [V]
- $e_a = 0$ [V]
- $L_a = 2$ [mH]
- $R_a = 2 \cdot \pi \cdot 500 \cdot L_a$ [Ohm]
- Switchfrekvens: 6.67 [kHz]
- $U_{ref} = 400$ [V]; 500 [Hz]

- **First 5 milliseconds:**

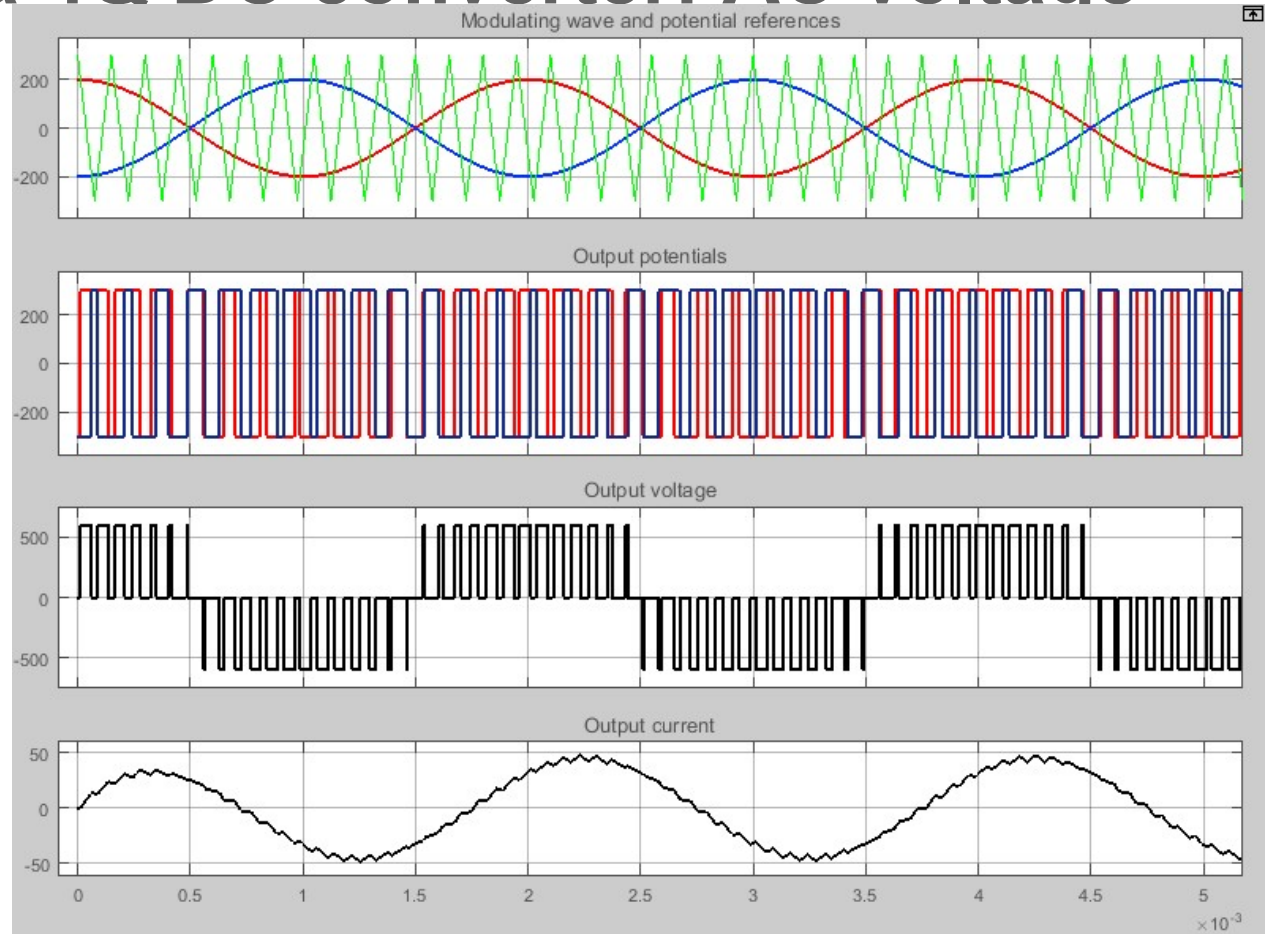

Modulation of a 4Q DC converter: AC voltage


- **Example:**

- $U_{dc} = 600$ [V]
- $e_a = 0$ [V]
- $L_a = 2$ [mH]
- $R_a = 2 * \pi * 500 * L_a$ [Ohm]
- Switchfrekvens: 6.67 [kHz]
- $U_{ref} = 400$ [V]; 500 [Hz]


- **First 5 milliseconds:**

- **Notice:**

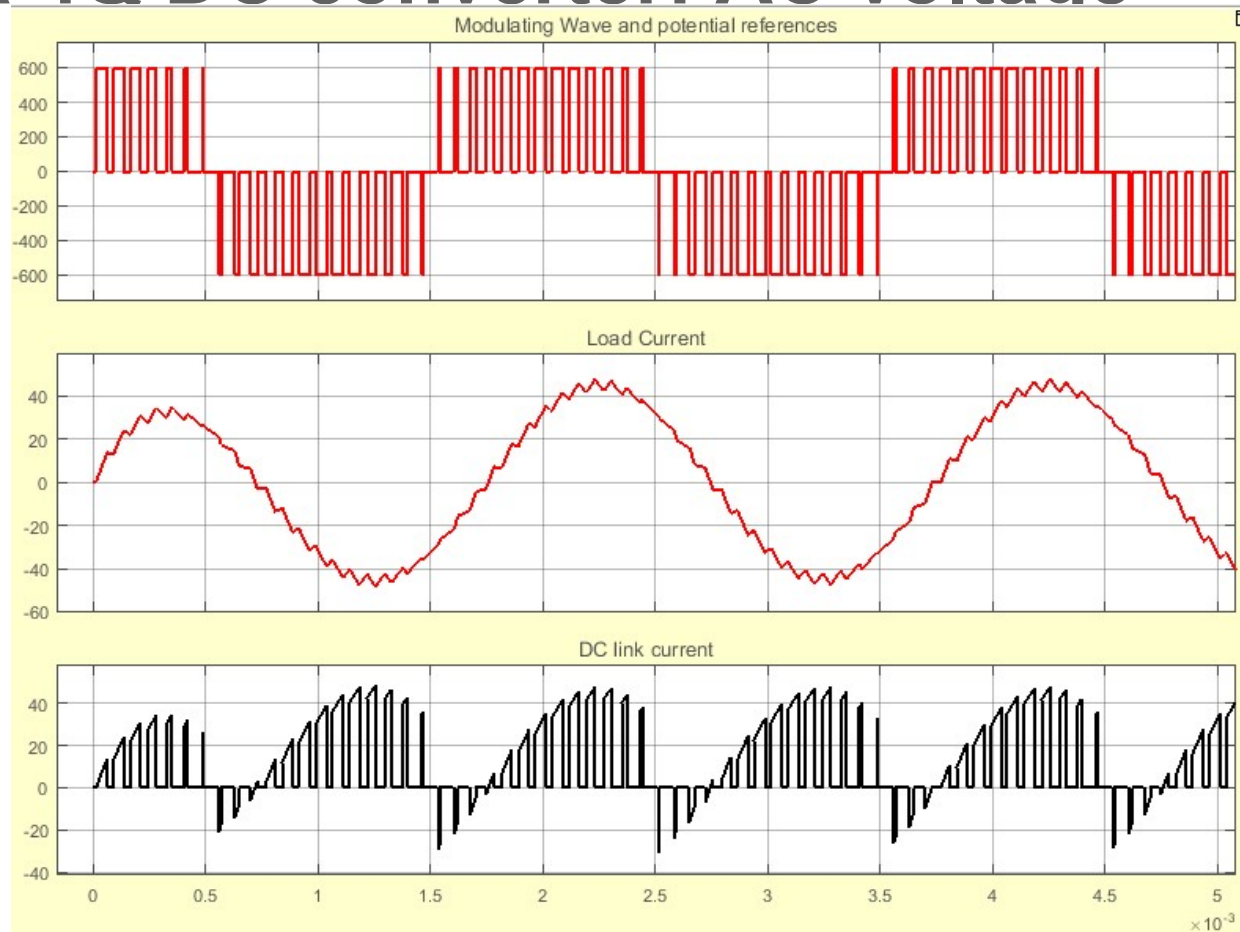
- DC-side: PWM current
- AC side: PWM voltage
- DC side: *Average power positive due to high R_a . $p/4$ phase shift due to $R_a = \omega L_a$*



To Simulink

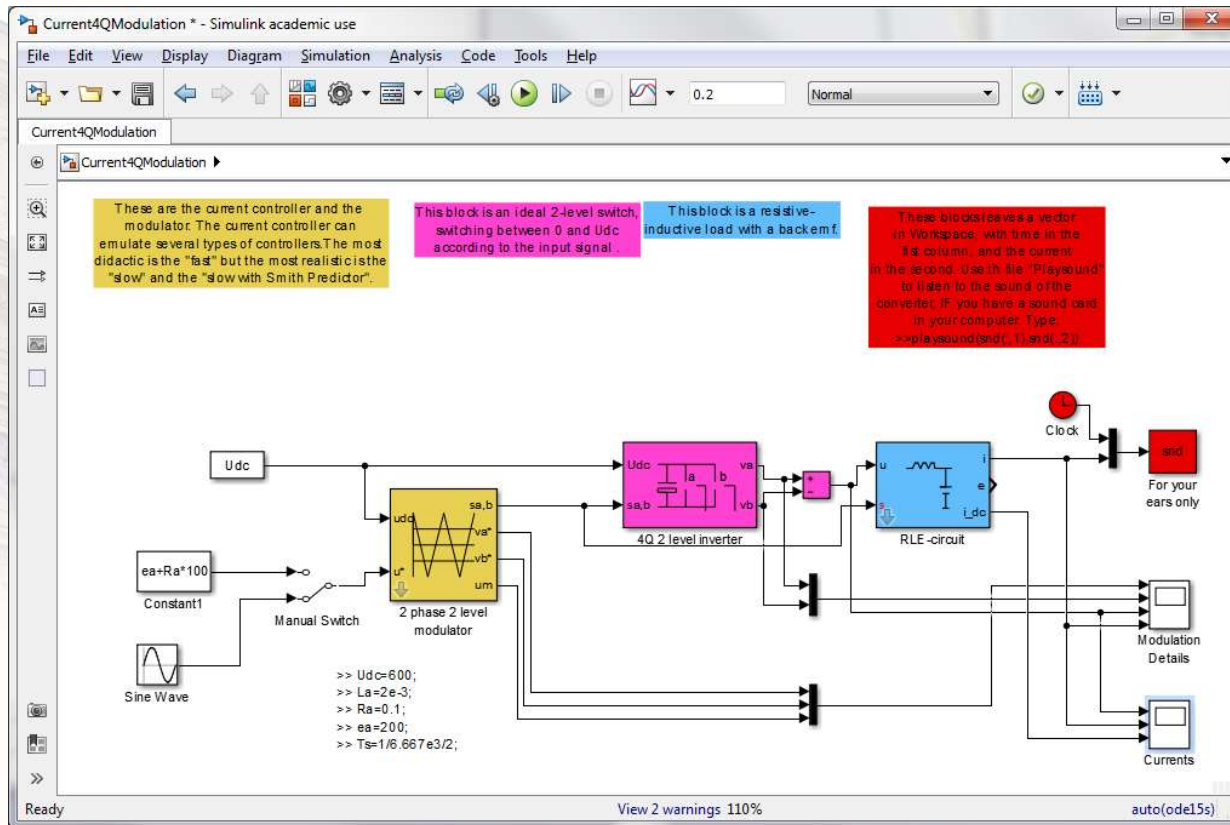

Thermal circuit

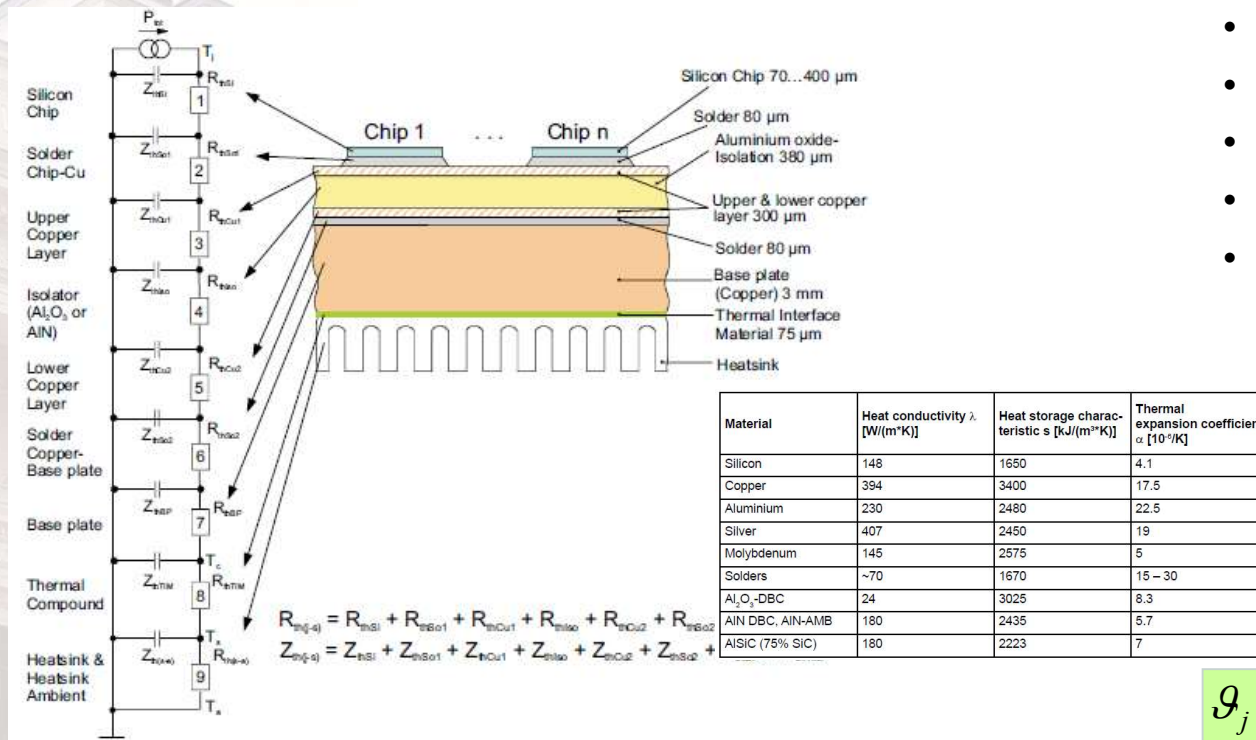

- Chip temperature ϑ_j
- Heat sink temperature ϑ_s
- Power losses P
- Thermal resistance R_{th}
- Thermal capacitance C_{th}

$$R_{th(j-s)} = \sum R_{th(layers)} \quad R_{th} = \frac{l}{\lambda A} \left[\frac{K}{W} \right]$$

$$C_{th(j-s)} = \sum C_{th(layers)} \quad C_{th} = mc \left[\frac{J}{K} \right]$$

$$R_{conv} = \frac{1}{A_{cool} h}$$

$$\vartheta_j = P_j (R_{th} + R_{conv}) + \vartheta_{amb}$$

Thermal circuit

- **Heat flow**


- **Heat sources:** losses in diodes and transistors
- **Heat sink:** natural or forced convection
- **Thermal resistance:** components and thermal connections between them

- **Thermal nodes**

- Junction
- Case
- Heat sink
- Ambient

- **Solutions**


- Steady state
- Transient

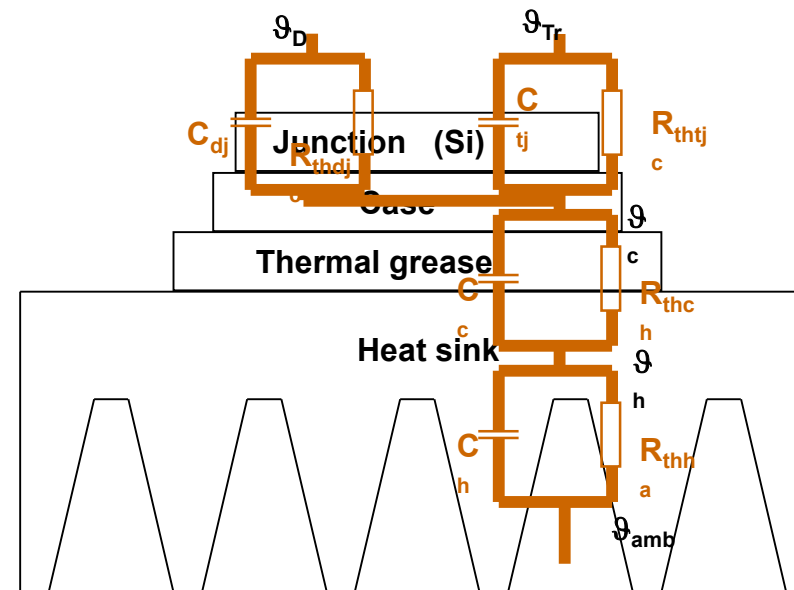

$$g_{A,end} = (R_{th} \cdot P + g_{amb}) \cdot (1 - e^{-\frac{t}{\tau}}) + g_{A,start} \cdot e^{-\frac{t}{\tau}}$$

Simple converter loss model

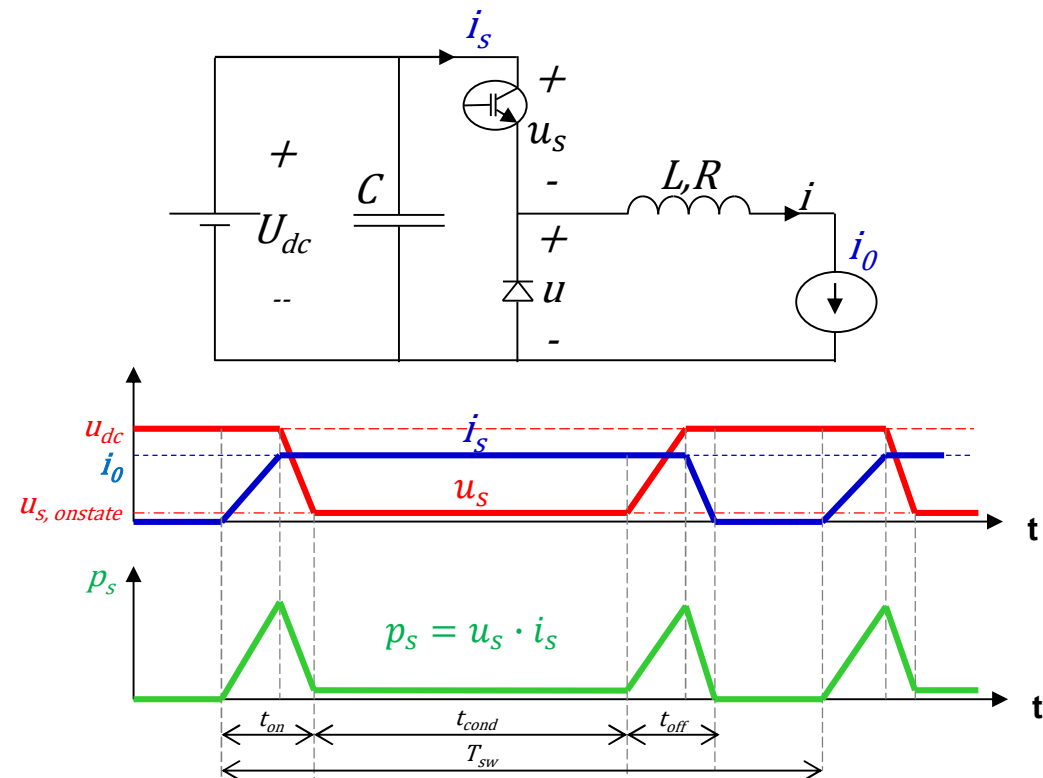- Switching waveforms, looking at turn-on, on-state and turn-off energy losses over switching sequence
- Considering temperature dependence
- Recalculate datasheet values to actual working point
- Pay attention if losses can be separated by components or they are provided as per integrated switch



Switching and conducting losses

Energy losses: $E_S(T_{sw}) = \int_{T_{sw}} p_S(\tau) d\tau = E_{S,on}(T_{sw}) + E_{S,cond}(T_{sw}) + E_{S,off}(T_{sw})$

$$E_{S,on}(T_{sw}) = \int_{t_{on}} p_S(\tau) d\tau = V_{DC} \cdot I_0 \cdot \frac{t_{on}}{2}$$

$$E_{S,cond}(T_{sw}) = \int_{t_{cond}} p_S(\tau) d\tau = V_{S(on)} \cdot I_0 \cdot t_{cond} \quad \text{Note} \quad V_{S(on)} = V_{S0} + R_S \cdot I_0$$

$$E_{S,off}(T_{sw}) = \int_{t_{off}} p_S(\tau) d\tau = V_{DC} \cdot I_0 \cdot \frac{t_{off}}{2}$$

Power losses: $P_S(T_{sw}) = \frac{E_S(T_{sw})}{T_{sw}} = P_{S,on}(T_{sw}) + P_{S,cond}(T_{sw}) + P_{S,off}(T_{sw})$

$$P_{S,on}(T_{sw}) = \frac{E_{S,on}(T_{sw})}{T_{sw}} = E_{S,on}(T_{sw}) \cdot f_{sw} = \frac{V_{DC} \cdot I_0 \cdot t_{on}}{2} \cdot f_{sw}$$

$$P_{S,cond}(T_{sw}) = \frac{E_{S,cond}(T_{sw})}{T_{sw}} = V_{S(on)} \cdot I_0 \cdot \frac{t_{cond}}{T_{sw}} = V_{S(on)} \cdot I_0 \cdot D_S$$

$$P_{S,off}(T_{sw}) = \frac{E_{S,off}(T_{sw})}{T_{sw}} = E_{S,off}(T_{sw}) \cdot f_{sw} = \frac{V_{DC} \cdot I_0 \cdot t_{off}}{2} \cdot f_{sw}$$

$$P_{S,sw}(T_{sw}) = P_{S,on}(T_{sw}) + P_{S,off}(T_{sw})$$

Turn on t_{on}
On-state t_{cond}
Turn off t_{off}

Reverse recovery losses

If specified, use:

$$E_{S,on}(T_{sw}) = \frac{E_{on,n}}{V_{DC,n} \cdot I_{0n}} \cdot V_{DC} \cdot I_0$$

$$E_{S,off}(T_{sw}) = \frac{E_{off,n}}{V_{DC,n} \cdot I_{0n}} \cdot V_{DC} \cdot I_0$$

For the freewheeling diode:

$$P_{D,cond}(T_{sw}) = V_{D(on)} \cdot I_0 \cdot D_D \quad V_{D(on)} = V_{D0} + R_D \cdot I_0$$

$$D_D \approx 1 - D_S$$

$$P_{D,rr} = V_{DC} \cdot Q_f \cdot f_{sw} \quad Q_f \approx \frac{1}{S+1} \cdot Q_{rr} \quad \text{where } S = \frac{t_{rr1}}{t_{rr2}}$$

If specified, use:

$$P_{D,off} = E_{D,off}(T_{sw}) \cdot f_{sw} \quad E_{D,off}(T_{sw}) = \frac{E_{off,n}}{V_{DC,n} \cdot I_{0n}} \cdot V_{DC} \cdot I_0$$

$$Q_f = \frac{Q_{f,n}}{I_{0n}} \cdot I_0$$

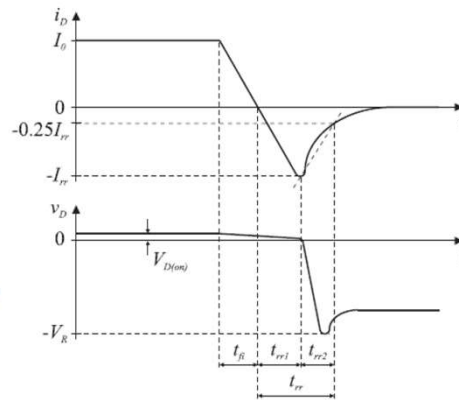


Figure 6.3: Diode turn-off.

Fall t_{ff}
 $di/dt < 0$ t_{rr1}
 $di/dt > 0$ t_{rr2}