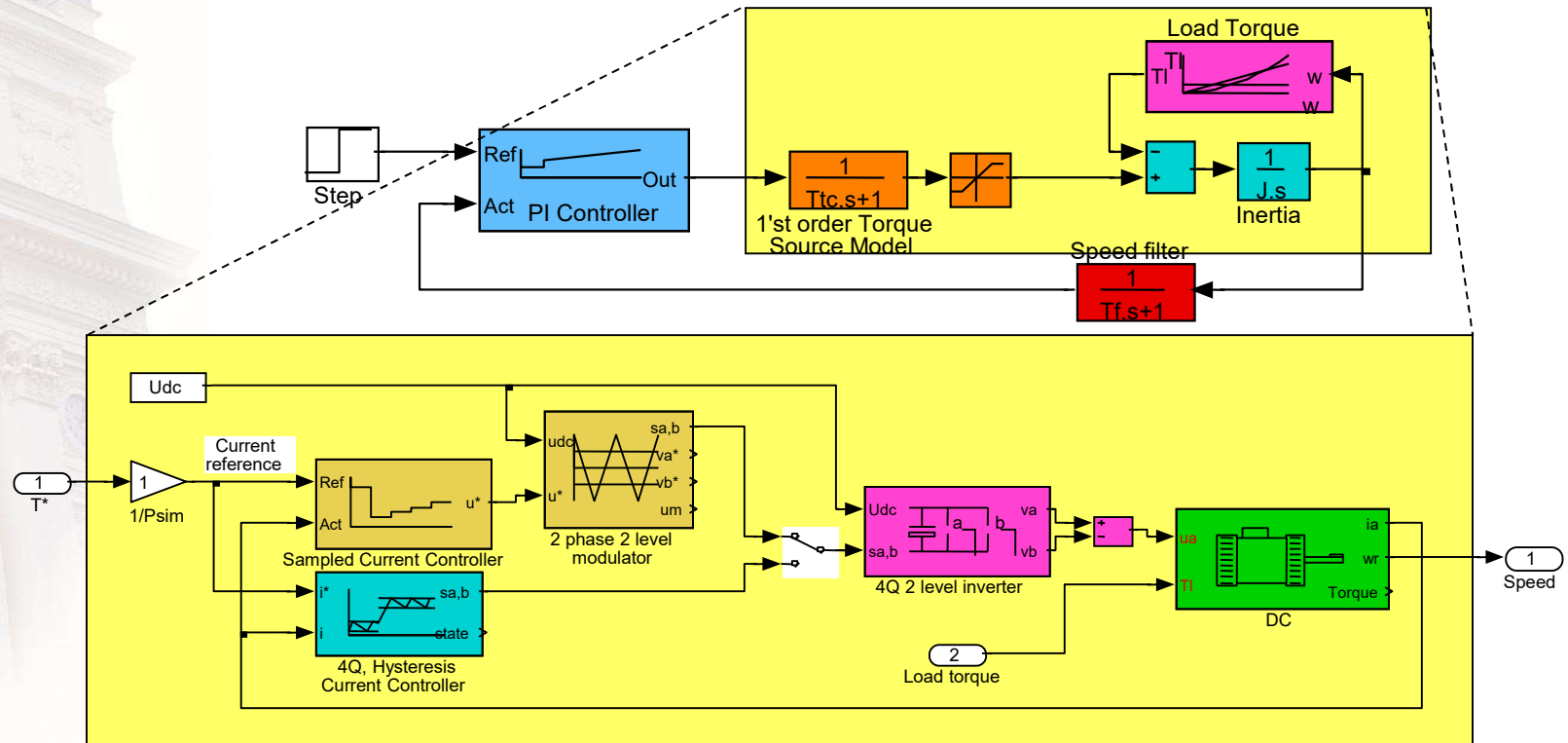




Current Control with 2 and 4-quadrant converters

L6 – Current Control (DC)


Loops



L6 – Current Control (DC)

So far

Modulation ...

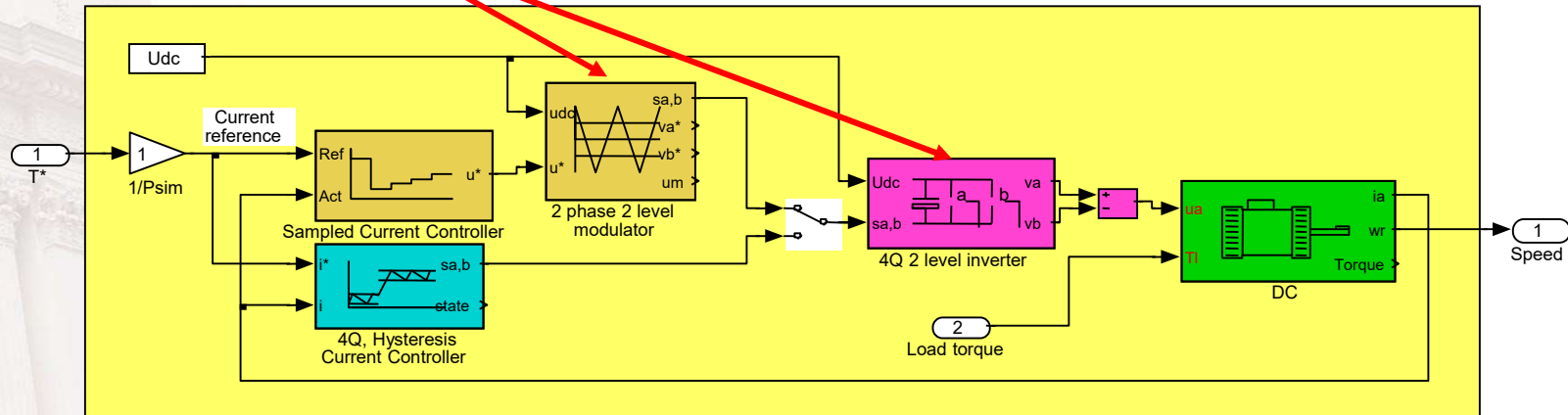


... or, how to convert a voltage reference into a pulse with modulated voltage

L6 – Current Control (DC)

Next step


Current control ...

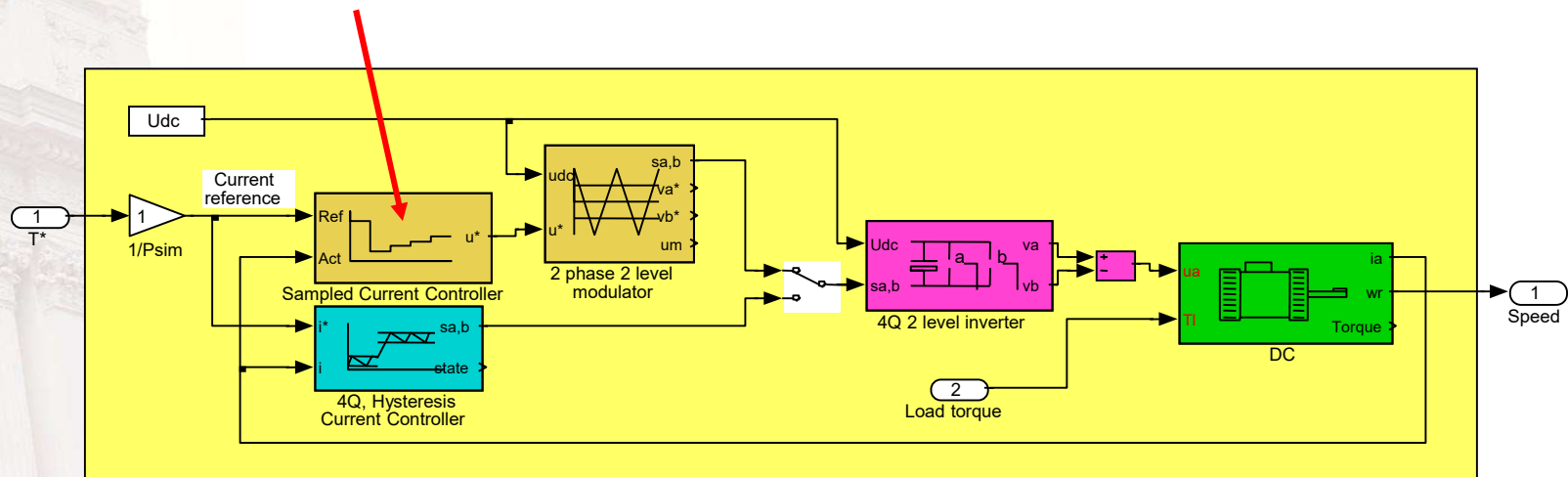


... or, how to convert a current reference into voltage references, or maybe a PWM pattern directly ...

Problems and means to control current

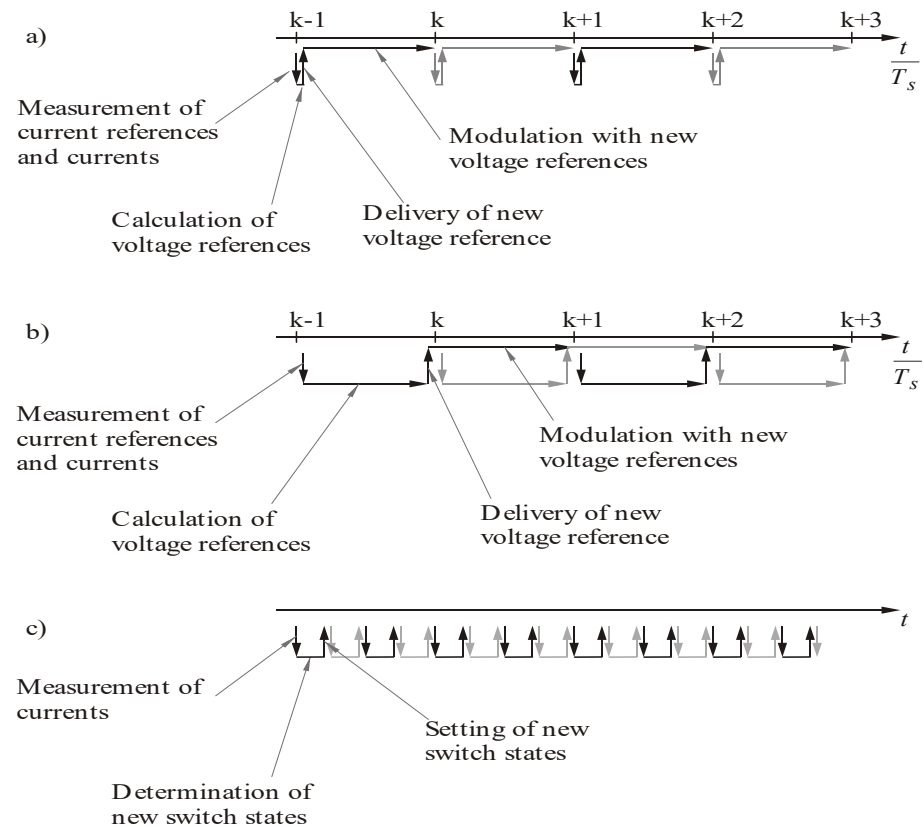- **Problem:**
 - *Current dynamics are extremely fast*
- **Means**
 - *Analogue controllers*
 - Fast, but prone to drift
 - Difficult to implement non linear control laws
 - *Digital controllers*
 - Not as fast, but exact
 - Easy to implement non linear control laws
 - Speed matters!




Generic Load

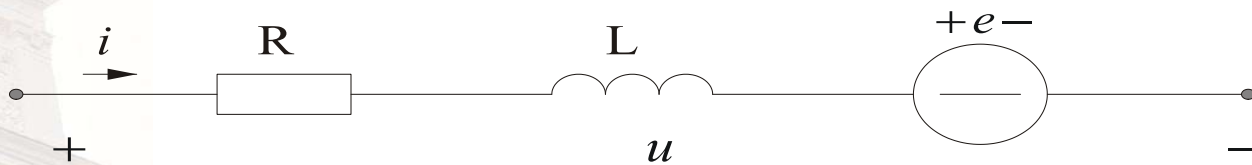

$$u = R \cdot i + L \cdot \frac{di}{dt} + e$$

Sampling of the current?

- Controllers are usually digital, with a fixed sampling frequency
- The current has a large ripple
- How to measure the current?
 - *Let's recapitulate the 2Q Modulations examples ...*
 - *Notice that the current passes through its average value every time the carrier wave turns ...*
- The solution is to **sample the current when the carrier wave turns**, in the 2 quadrant case, i.e. A twice the switching frequency.
- So, we go on with a sampled current controller

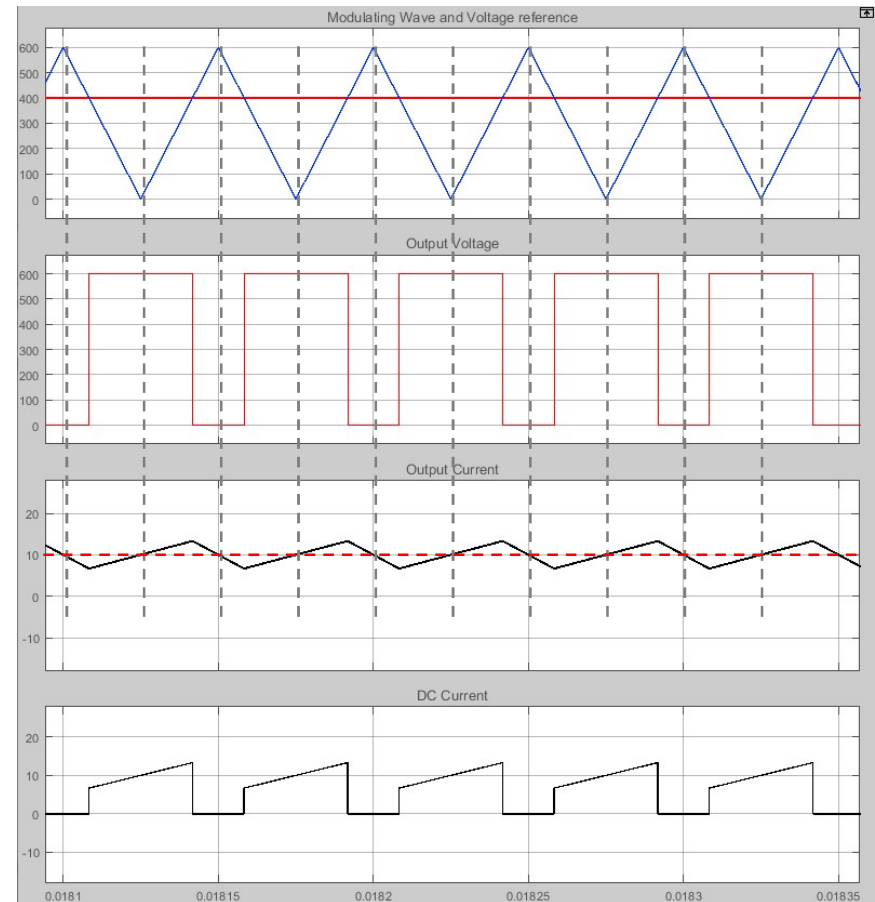

L6 – Current Control (DC)

Current controller, derived from the voltage equation

$$\frac{\int_{k \cdot T_s}^{(k+1)T_s} u \cdot dt}{T_s} = \frac{R \cdot \int_{k \cdot T_s}^{(k+1)T_s} i \cdot dt + L \cdot \int_{k \cdot T_s}^{(k+1)T_s} \frac{di}{dt} \cdot dt + \int_{k \cdot T_s}^{(k+1)T_s} e \cdot dt}{T_s} =$$
$$= \bar{u}(k, k+1) = R \cdot \bar{i}(k, k+1) + L \cdot \frac{i(k+1) - i(k)}{T_s} + \bar{e}(k, k+1)$$

$$\bar{u}(k, k+1) = u^*(k) \quad (a)$$

$$i(k+1) = i^*(k) \quad (b)$$

$$\bar{i}(k, k+1) = \frac{i^*(k) + i(k)}{2} \quad (c)$$

$$\bar{e}(k, k+1) = e(k) \quad (d)$$



$$i(k) = \sum_{n=0}^{k-1} (i^*(n) - i(n)) \quad (e)$$

Current Controller continued

$$\begin{aligned} u^*(k) &= R \cdot \frac{i^*(k) + i(k)}{2} + L \cdot \frac{i^*(k) - i(k)}{T_s} + e(k) = \\ &= R \cdot \frac{i^*(k) - i(k)}{2} + R \cdot i(k) + L \cdot \frac{i^*(k) - i(k)}{T_s} + e(k) = \\ &= \left(\frac{L}{T_s} + \frac{R}{2} \right) (i^*(k) - i(k)) + R \cdot \sum_{n=0}^{n=k-1} (i^*(n) - i(n)) + e(k) = \\ &= \left(\frac{L}{T_s} + \frac{R}{2} \right) \cdot \left(\underbrace{(i^*(k) - i(k))}_{\text{Proportional}} + \underbrace{\frac{T_s}{\left(\frac{L}{R} + \frac{T_s}{2} \right)} \cdot \sum_{n=0}^{n=k-1} (i^*(n) - i(n))}_{\text{Integral}} \right) + \underbrace{e(k)}_{\substack{\text{Feed} \\ \text{forward}}} \end{aligned}$$

Current Control of a 2Q DC converter

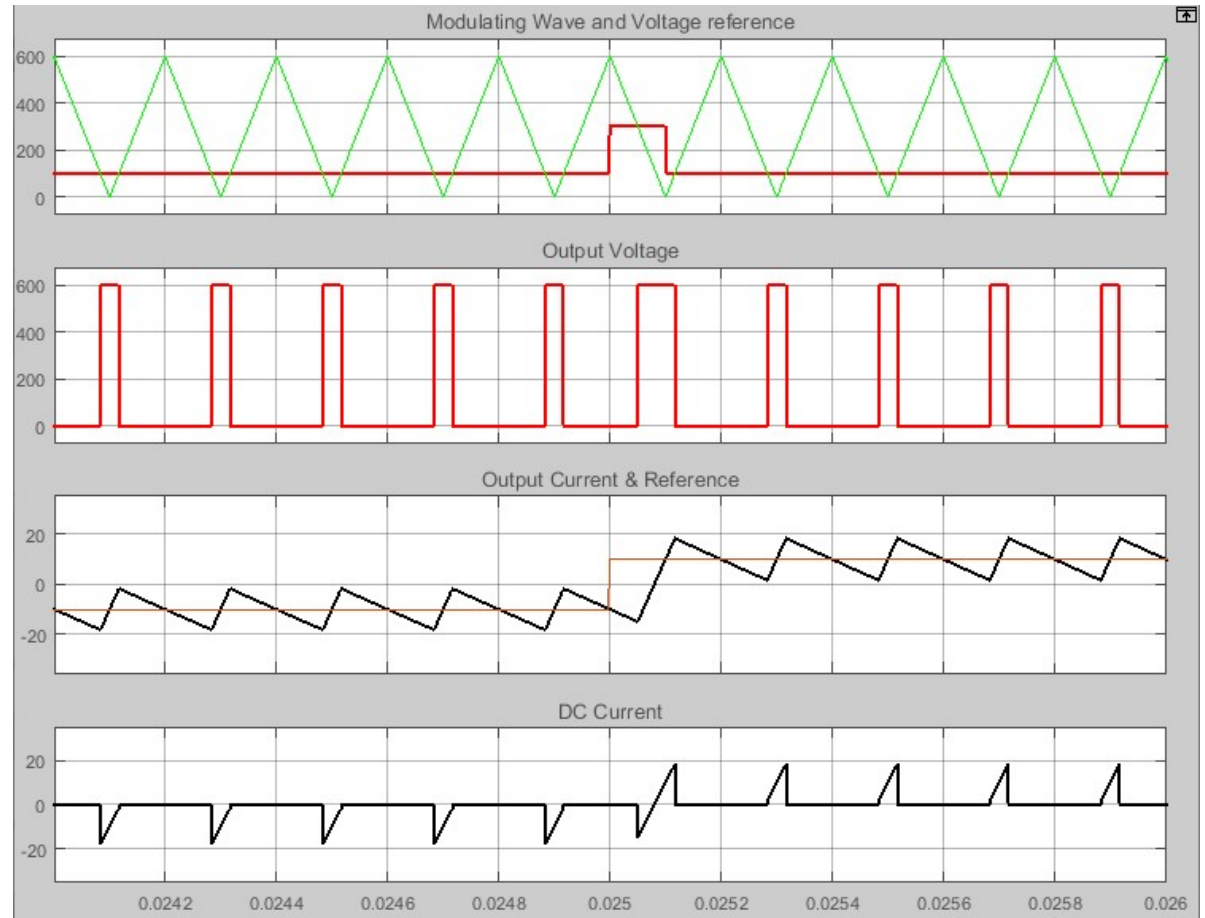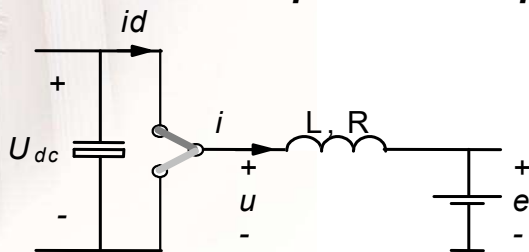- **Example:**
 - $U_{dc}=600$;
 - $L_a=1e-3$;
 - $R_a=0.1$;
 - $e_a=100$;
 - $T_s=100e-6$
 - $i^* = \pm 10$ A square wave @ 20 Hz
- **1 millisecond around step**
- **Notice:**
 - **Positive step in one sample**



Current Controller continued



- **Example:**

- $U_{dc}=600$;
- $L_a=1e-3$;
- $R_a=0.1$;
- $e_a=100$;
- $T_s=100e-6$


$$u^*(k) = \left(\frac{L}{T_s} + \frac{R}{2} \right) \cdot \left(\underbrace{(i^*(k) - i(k))}_{\text{Proportional}} + \underbrace{\frac{T_s}{\left(\frac{L}{R} + \frac{T_s}{2} \right)} \cdot \sum_{n=0}^{n=k-1} (i^*(n) - i(n))}_{\text{Integral}} \right) + \underbrace{e(k)}_{\text{Feed forward}}$$

Current Control of a 2Q DC converter

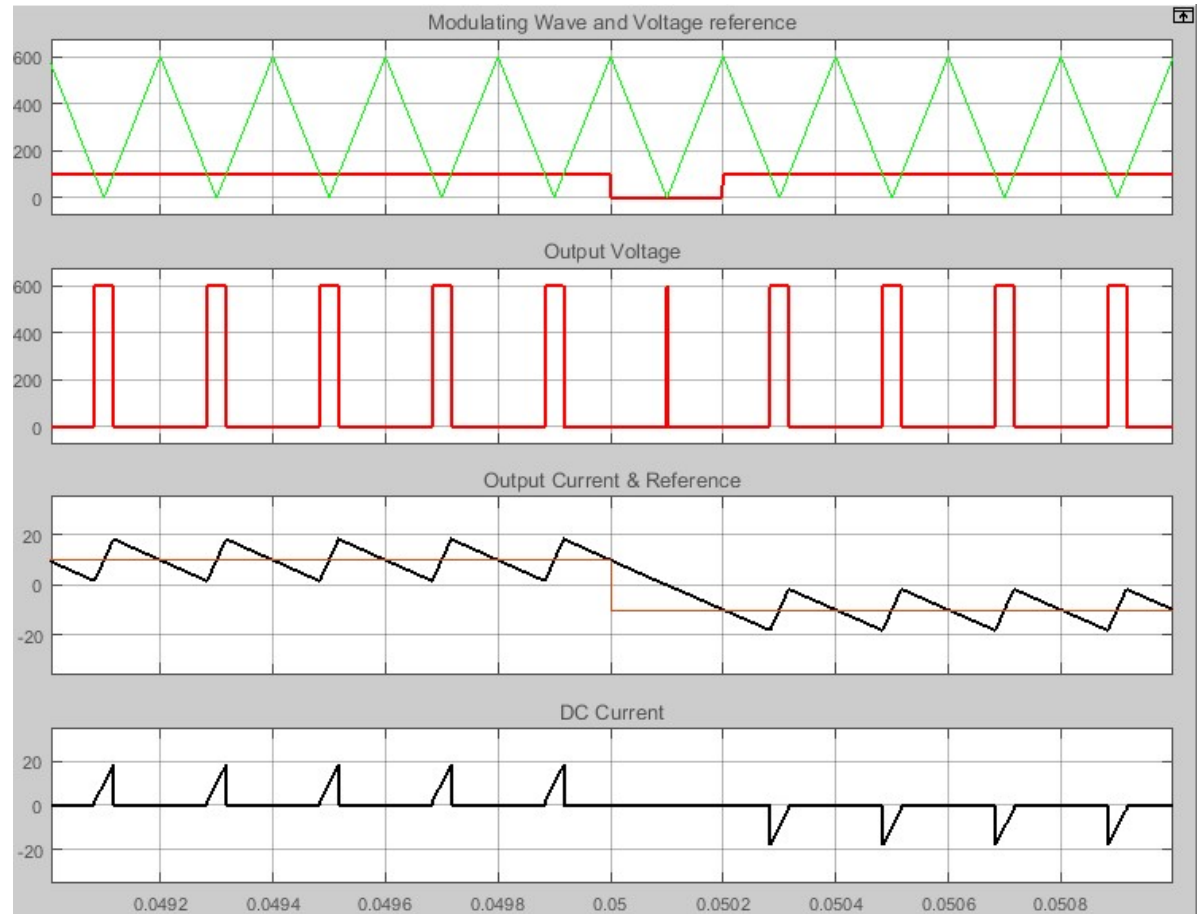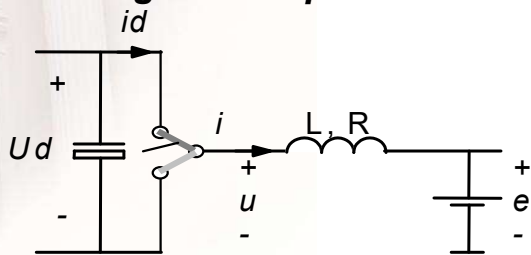- **Example:**
 - $U_{dc}=600$;
 - $L_a=1e-3$;
 - $R_a=0.1$;
 - $e_a=100$;
 - $T_s=100e-6$
 - $i^* = \pm 10$ A square wave @ 20 Hz
- **1 millisecond around step**
- **Notice:**
 - **Negative step SLOW!**



Current ripple

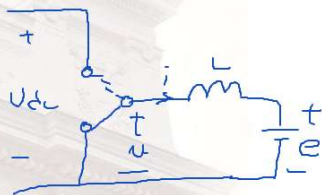

Stationary $\rightarrow t_p = \frac{e}{U_{dc}} \cdot 2 \cdot T_s$

$$\frac{di}{dt} = \begin{cases} \frac{U_{dc} - e}{L} & \text{if } u = U_{dc} \\ -\frac{e}{L} & \text{if } u = 0 \end{cases}$$



$$\Delta i = \frac{U_{dc} - e}{L} \cdot t_p$$

$$\Delta i = \frac{U_{dc} - e}{L} \cdot \frac{e}{U_{dc}} \cdot 2T_s = e \cdot \frac{U_{dc} \cdot 2T_s}{L \cdot U_{dc}} - \frac{e^2 \cdot 2T_s}{U_{dc} L}$$

$$\frac{d\Delta i}{de} = \frac{2T_s}{L} - 2 \cdot e \cdot \frac{2T_s}{L \cdot U_{dc}} = 0 \rightarrow \frac{2T_s}{L} = 2 \cdot e \cdot \frac{2T_s}{U_{dc} L}$$

$$e = \frac{U_{dc}}{2}$$
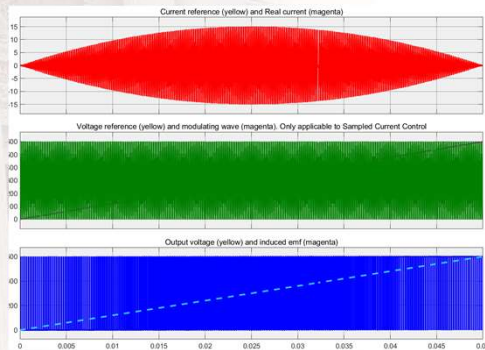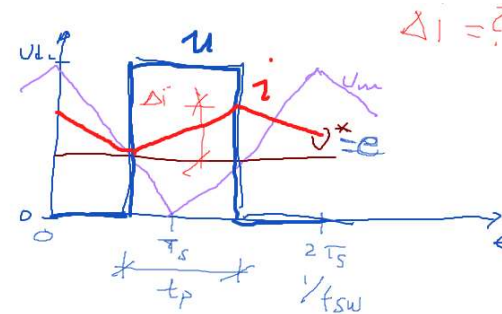
$$\Delta i_{\max} = \frac{U_{dc}}{2} \cdot \frac{2T_s}{L} - \frac{U_{dc} \cdot 2T_s}{4 \cdot L} = \frac{U_{dc} \cdot T_s}{L} - \frac{U_{dc} \cdot 2T_s}{4 \cdot L} = \frac{U_{dc}}{L} \cdot T_s$$



L6 – Current Control (DC)

Current Control of a 4Q DC converter (POSITIVE STEP)


- **Example:**

- $U_{dc} = 600$ [V]
- $R_a = 0.1$ [Ohm]
- $e_a = 100$ [V]
- $L = 2$ [mH]
- Switchfrequency: 6.67 [kHz]
- $i^* = \pm 10$ A square wave at 20 Hz.

- **1 millisecond around step**

- **Notice:**

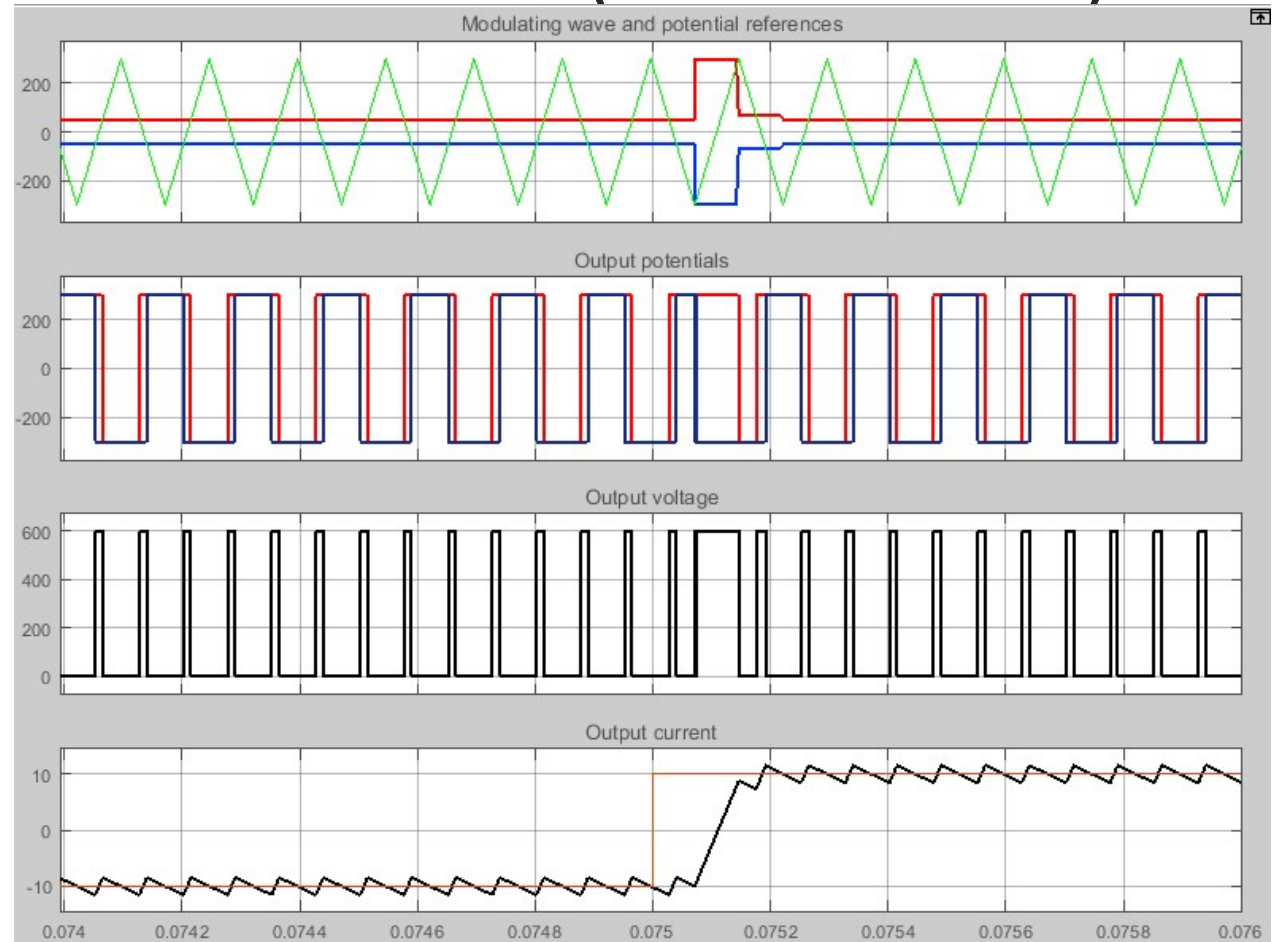- One sample interval **ALMOST** enough for **positive step**



Current Control of a 4Q DC converter (NEGATIVE STEP)


- **Example:**

- $U_{dc} = 600$ [V]
- $R_a = 0.1$ [Ohm]
- $e_a = 100$ [V]
- $L = 2$ [mH]
- Switchfrequency: 6.67 [kHz]
- $i^* = \pm 10$ A square wave at 20 Hz.

- **1 millisecond around step**

- **Notice:**

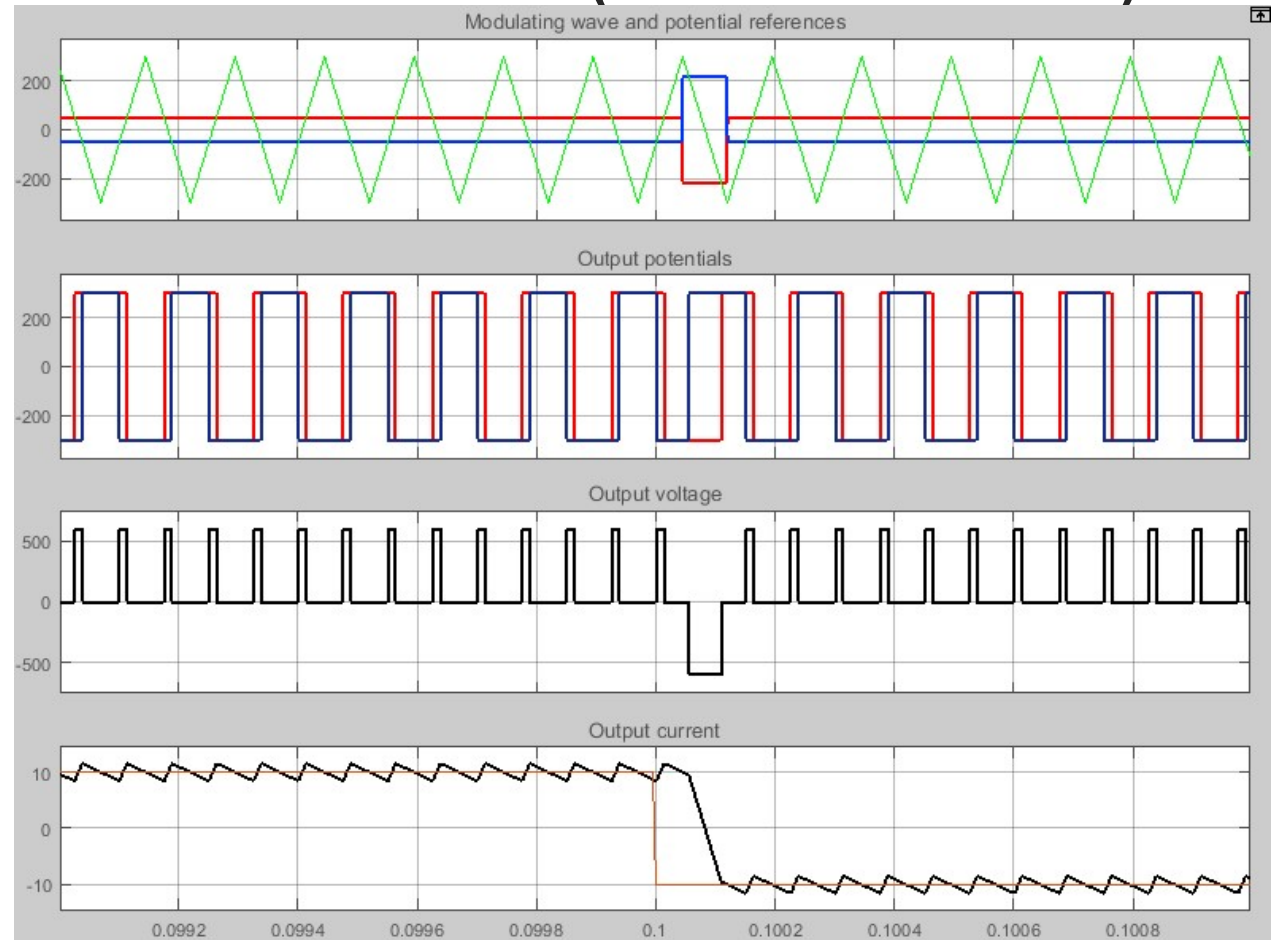- One sample interval enough for **negative step**




Current Control of a 4Q DC converter (POSITIVE STEP)

- **Example:**

- $U_{dc} = 600$ [V]
- $R_a = 0.1$ [Ohm]
- $e_a = 100$ [V]
- $L = 2$ [mH]
- Switchfrequency: 6.67 [kHz]
- $i^* = \pm 10$ A square wave at 20 Hz

- **First two milliseconds:**

- **Notice:**

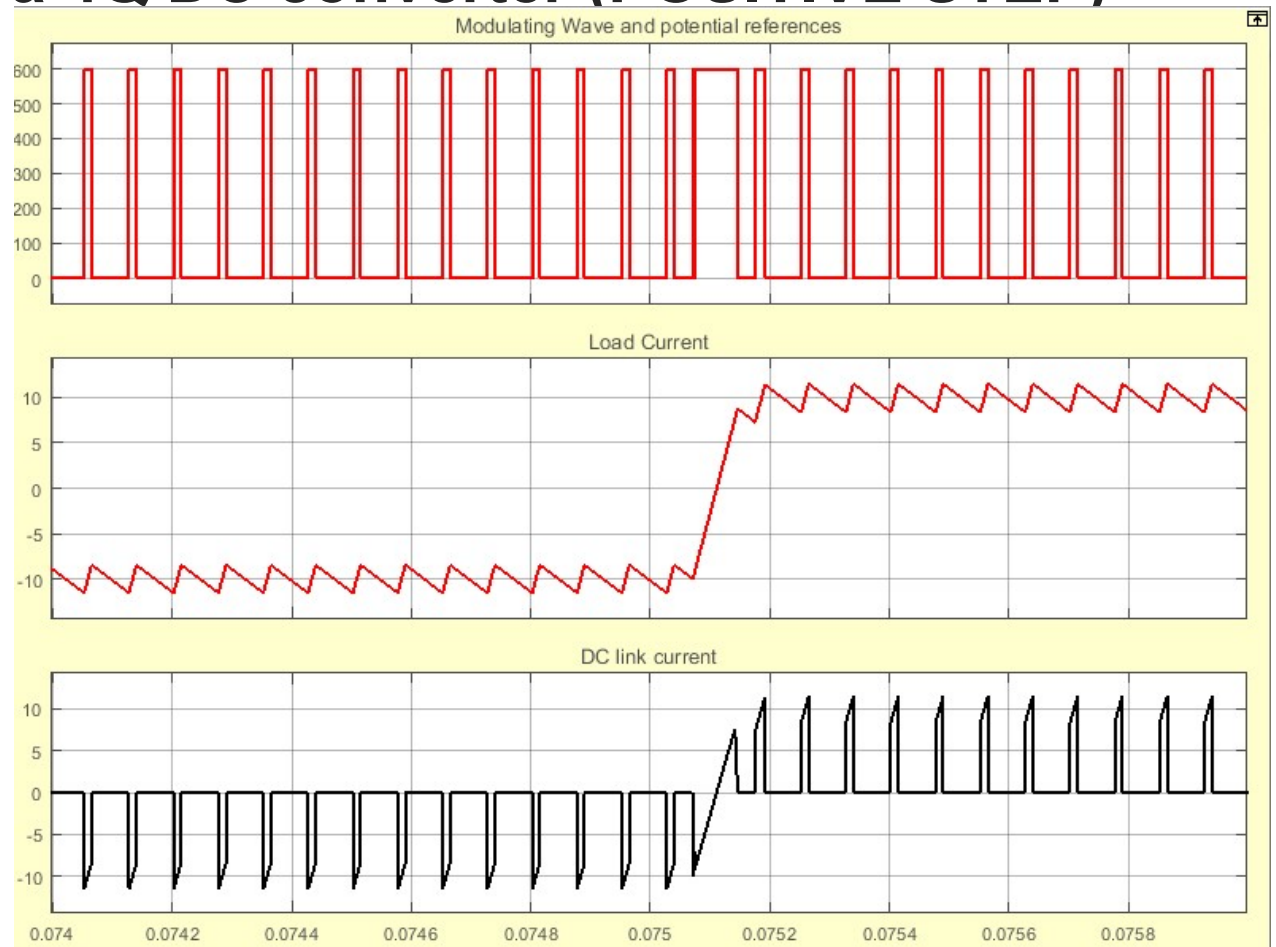


Current Control of a 4Q DC converter (NEGATIVE STEP)

- **Example:**


- $U_{dc} = 600$ [V]
- $R_a = 0.1$ [Ohm]
- $e_a = 100$ [V]
- $L = 2$ [mH]
- Switchfrequency: 6.67 [kHz]
- $i^* = \pm 10$ A square wave at 20 Hz

- **First two milliseconds:**

- **Notice:**

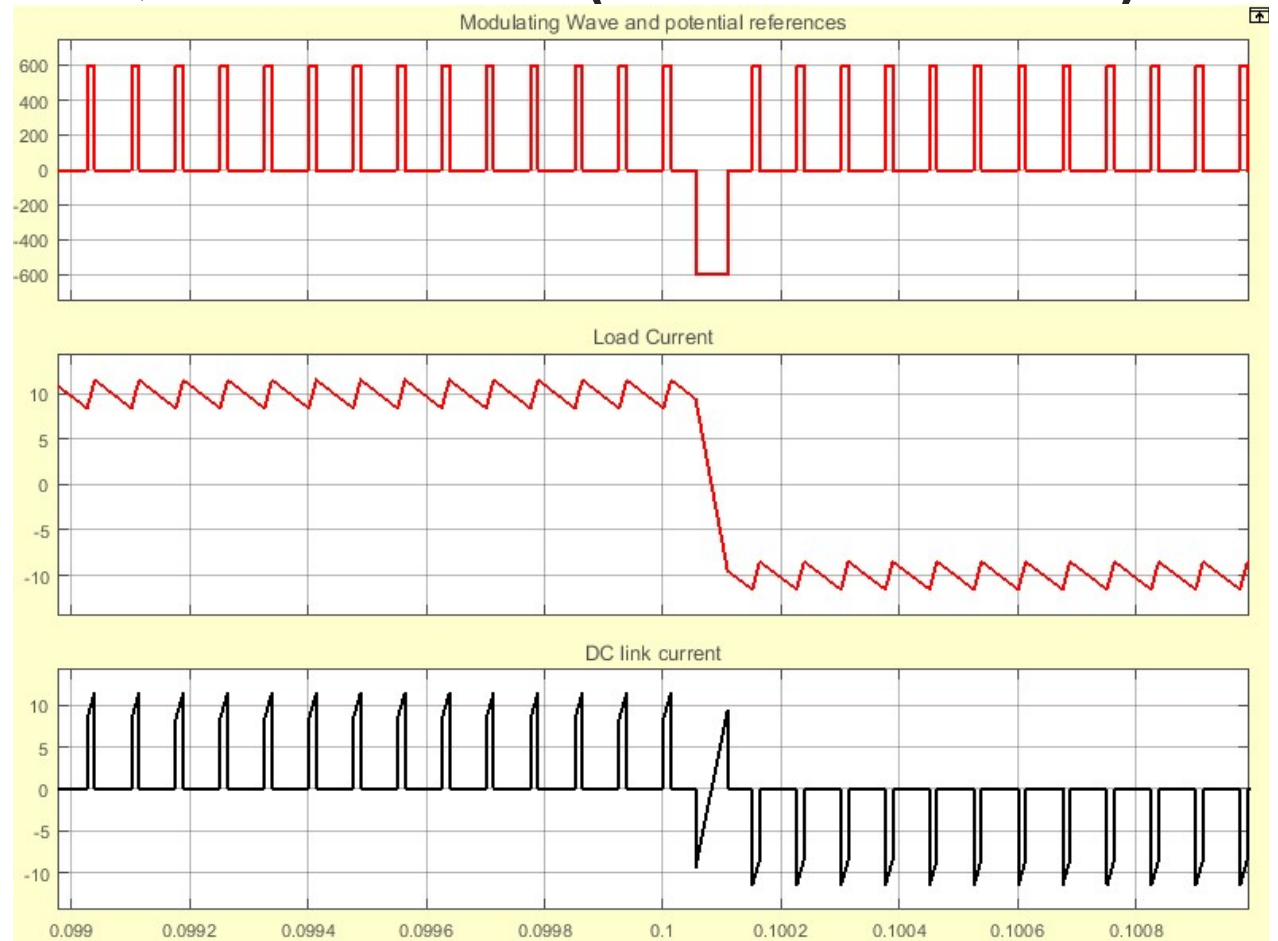

Go to Simulation

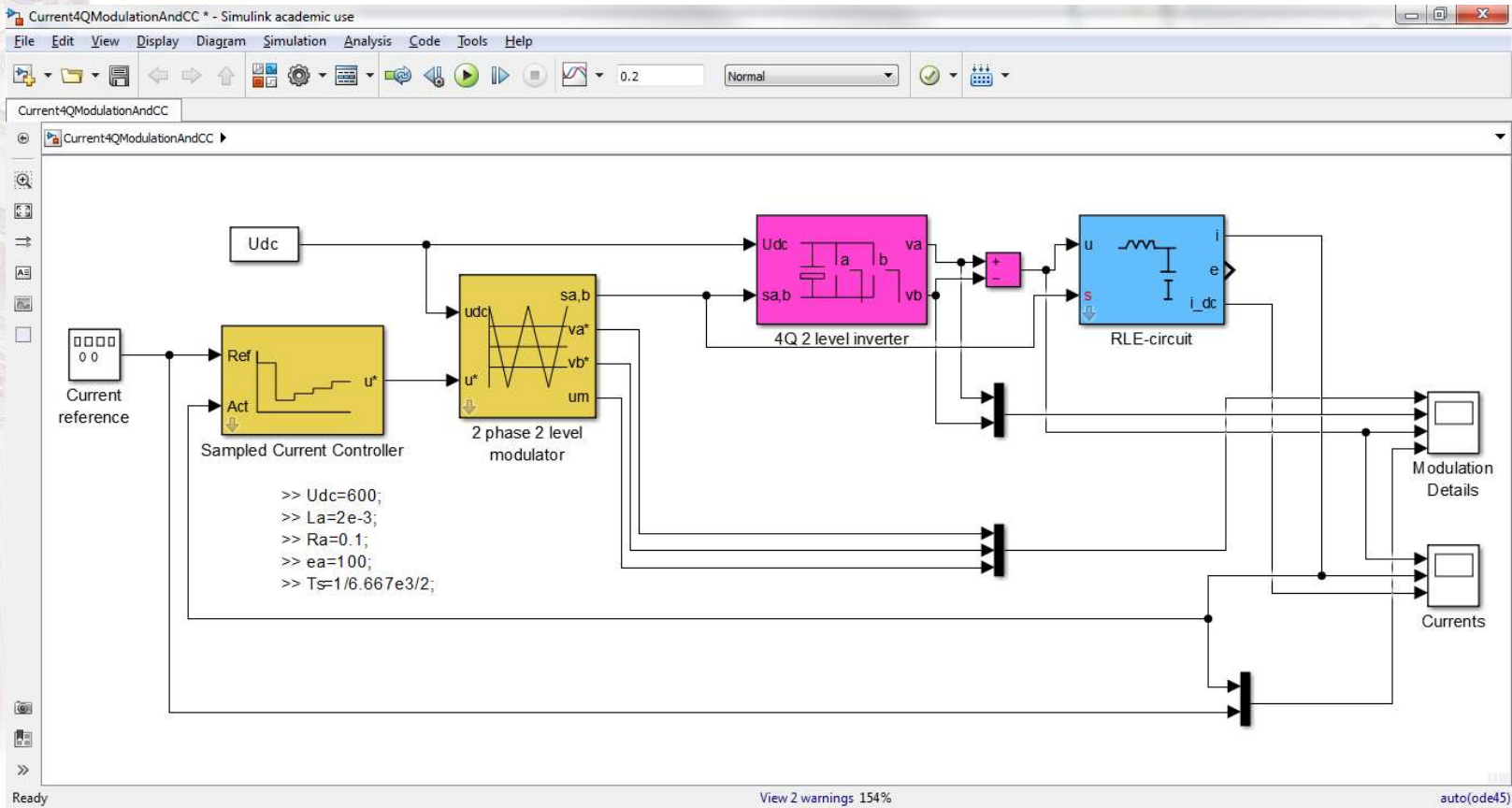




If the computer is to slow ?

L6 – Current Control (DC)

Compensation for a slow computer

- the Smith predictor

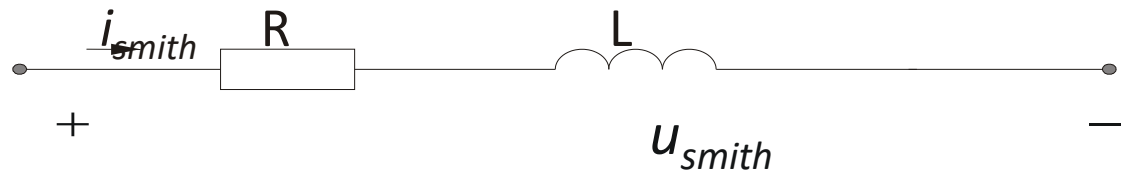- Use a "dummy" system that simulates the current response to voltage references.
- Let the dummy system be purely Resistive-Inductive, i.e. NO EMF!



$$u = R \cdot i_{smith} + L \cdot \frac{di_{smith}}{dt}$$

The Smith Predictor : II

- *The SP will have the same dynamics as the real system, but not the same statics.*

$$i_{smith,static} = \frac{u}{R}$$

$$i_{real,static} = \frac{u - e}{R}$$

$$\frac{di_{smith}}{dt} = \frac{u - R \cdot i_{smith}}{L}$$

$$\frac{di_{real}}{dt} = \frac{u - e - R \cdot i_{real}}{L}$$

- *Think like this:*
 - *Assume stationarity -> nominator of the current derivative = 0*
 - *A voltage (u) change gives the same derivative in both cases.*

The Smith Predictor : III

- Calculate the current of the next sampling instant as the sum of:
 - The current measured at the last sampling instant
 - The change of the current based on the voltage reference at the last sampling instant.
 - i.e.:

$$\hat{i}(k) = i(k-1) + \Delta i_{smith}(k)$$

$$\Delta i_{smith}(k) = i_{smith}(k) - i_{smith}(k-1)$$


$$u^*(k-1) \approx R \cdot i_{smith}(k-1) + L \cdot \frac{i_{smith}(k) - i_{smith}(k-1)}{T_s}$$

$$i_{smith}(k) - i_{smith}(k-1) = u^*(k-1) \cdot \frac{T_s}{L} - R \cdot i_{smith}(k-1) \cdot \frac{T_s}{L}$$

$$i_{smith}(k) = u^*(k-1) \cdot \frac{T_s}{L} + \left(1 - R \cdot \frac{T_s}{L}\right) \cdot i_{smith}(k-1)$$

The Smith Predictor : IV
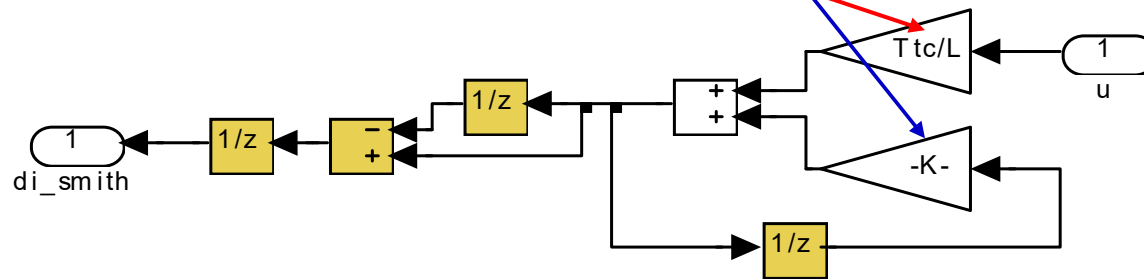
$$i_{smith}(k) = u^*(k-1) \cdot \frac{T_s}{L} + \left(1 - R \cdot \frac{T_s}{L}\right) \cdot i_{smith}(k-1)$$



L6 – Current Control (DC)

Current Control with a slow computer – II

$$u^*(k) = \left(\frac{L}{T_s} + \frac{R}{2} \right) \cdot \left(i^*(k) - \hat{i}(k) \right) + \frac{T_s}{\left(\frac{L}{R} + \frac{T_s}{2} \right)} \cdot \sum_{n=0}^{k-1} \left(i^*(n) - \hat{i}(n) \right) + \hat{e}(k)$$




Direct Current Control

- **Switch state only a function of current error**
- **No intermediate current control or modulation**



2-Quadrant Direct Current Controller
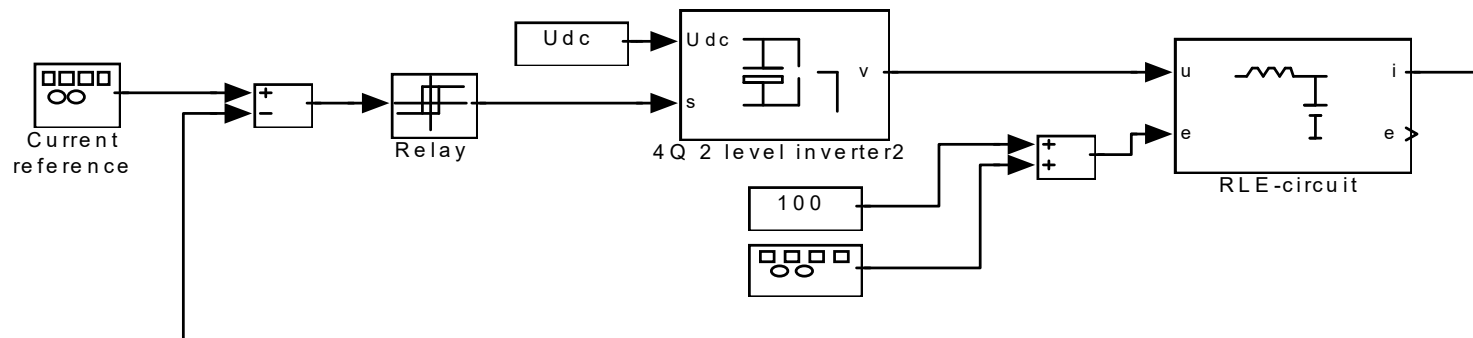
$$s = \begin{cases} 1 & \text{if } i < i^* - \frac{\Delta i}{2} \\ -1 & \text{if } i > i^* + \frac{\Delta i}{2} \\ s & \text{if } i^* - \frac{\Delta i}{2} < i < i^* + \frac{\Delta i}{2} \end{cases}$$



L6 – Current Control (DC)


Example

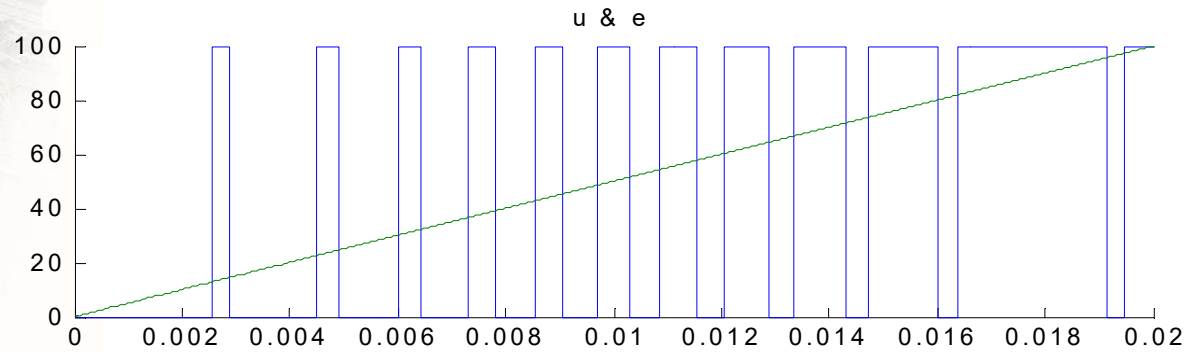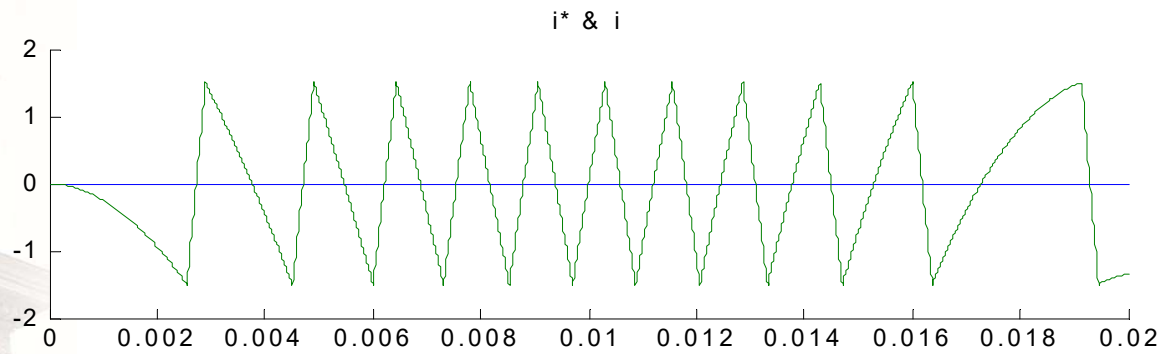

L6 – Current Control (DC)

4-Quadrant Direct Current Controller

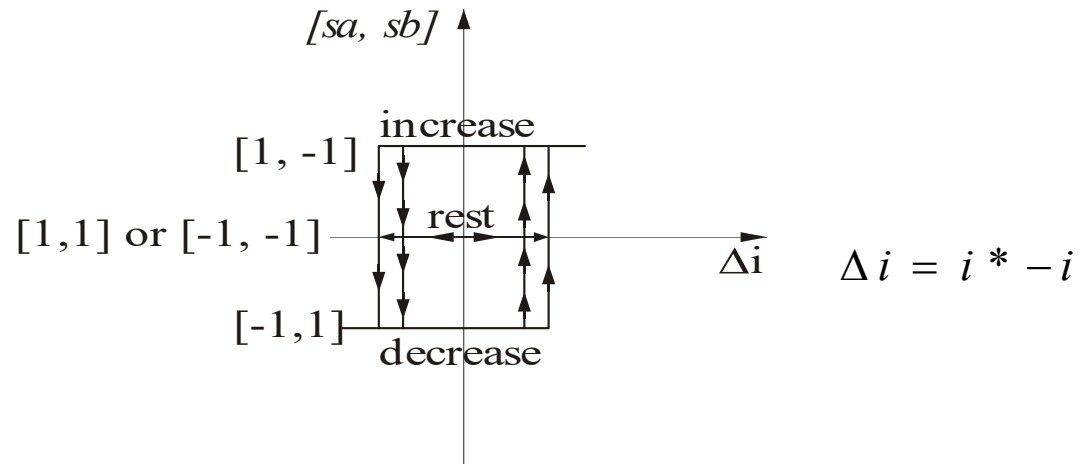- **More tricky:**
 - 4 states ($[-1,-1]$, $[1,1]$, $[1,-1]$ & $[-1,1]$),
but
 - Only 3 output voltages ($-U_{dc}$, 0 , U_{dc})
- **One solution:**




L6 – Current Control (DC)

Q hysteresis control in detail

State	u	di/dt	
[-1,-1]	0	-e/L	
[1,-1]	U _{dc}	(U _{dc} -e)/L	
[-1,1]	-U _{dc}	(-U _{dc} -e)/L	
[1,1]	0	-e/L	

Example

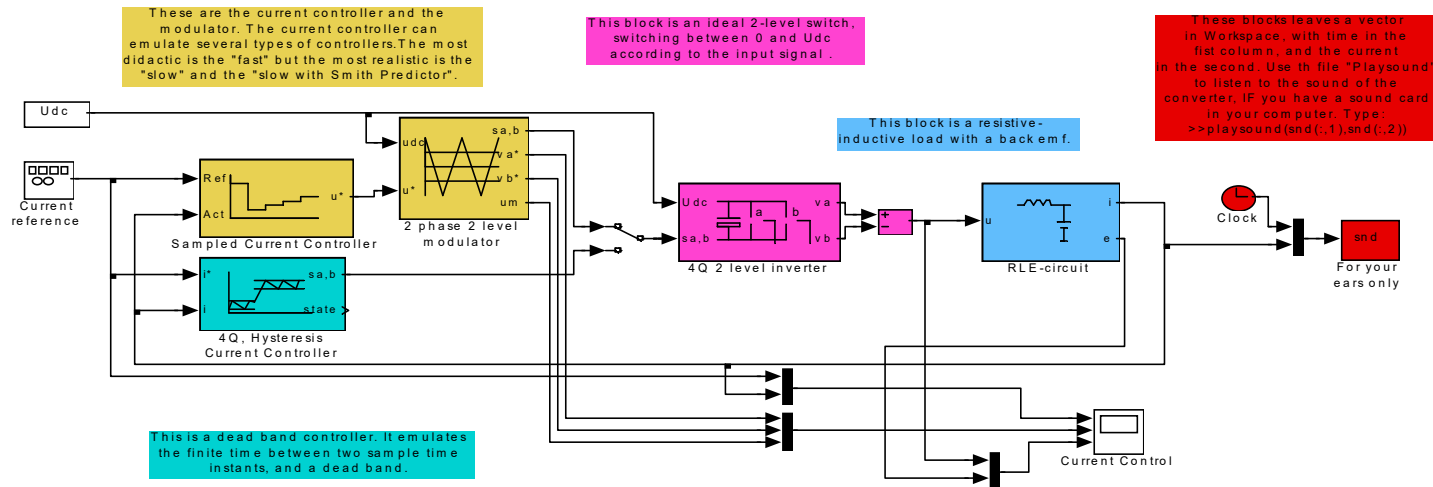

L6 – Current Control (DC)