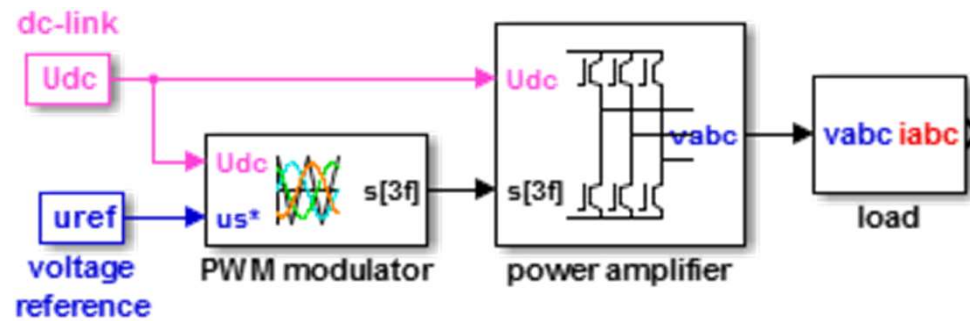





## L9: AC power + 3 $\phi$ modulation


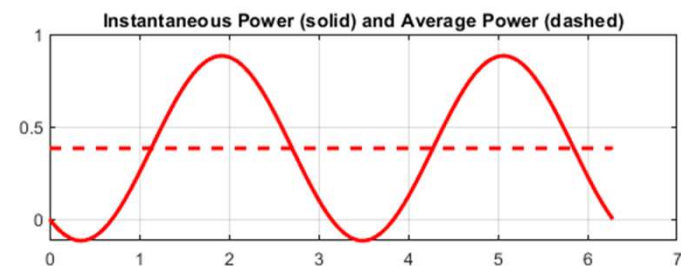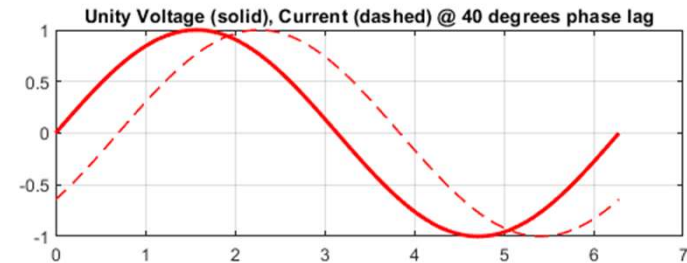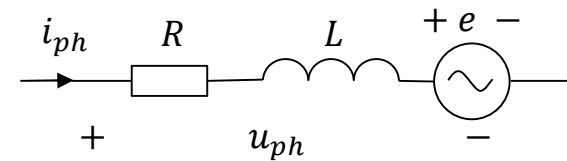
## Single phase power (with sine functions)


$$\begin{cases} u(t) = \hat{u}_{ph} \cdot \cos(\omega t) \\ i(t) = \hat{i}_{ph} \cdot \cos(\omega t - \varphi) \end{cases}$$

$$\begin{aligned} p(t) &= \hat{u}_{ph} \cdot \hat{i}_{ph} \cdot (\cos(\omega t) \cdot \cos(\omega t - \varphi)) = \\ &= \left\{ \cos(x) \cdot \cos(x - y) = \frac{\cos(y) + \cos(2x + y)}{2} \right\} = \\ &= \frac{\hat{u}_{ph} \cdot \hat{i}_{ph}}{2} \cdot (\cos(\varphi) + \cos(2\omega t - \varphi)) = \\ &= \frac{\sqrt{2} \cdot U_{ph} \cdot \sqrt{2} \cdot I_{ph}}{2} \cdot \cos(\varphi) = \\ &= U_{ph} \cdot I_{ph} \cdot \cos(\varphi) + U_{ph} \cdot I_{ph} \cdot \cos(2\omega t - \varphi) \end{aligned}$$


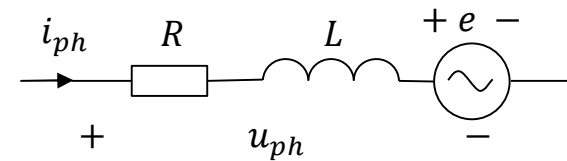
## Single phase power (with vectors)

$$\begin{cases} u(t) = \hat{u}_{ph} \cdot \cos(\omega t) = \hat{u}_{ph} \cdot \frac{e^{j\omega t} + e^{-j\omega t}}{2} \\ i(t) = \hat{i}_{ph} \cdot \cos(\omega t - \varphi) = \hat{i}_{ph} \cdot \frac{e^{j\omega t - j\varphi} + e^{-j\omega t + j\varphi}}{2} \end{cases}$$



$$p(t) = u(t) \cdot i(t) = \hat{u}_{ph} \cdot \hat{i}_{ph} \cdot \left( \frac{e^{j\omega t} + e^{-j\omega t}}{2} \right) \cdot \left( \frac{e^{j\omega t - j\varphi} + e^{-j\omega t + j\varphi}}{2} \right)$$

$$= \frac{U_{ph} \cdot I_{ph}}{2} \cdot [e^{j\omega t + j\omega t - j\varphi} + e^{j\omega t - j\omega t + j\varphi} + e^{-j\omega t + j\omega t - j\varphi} + e^{-j\omega t - j\omega t + j\varphi}] =$$

$$= \frac{U_{ph} \cdot I_{ph}}{2} \cdot [(e^{2j\omega t - j\varphi} + e^{-(2j\omega t - j\varphi)}) + (e^{j\varphi} + e^{-j\varphi})] =$$

$$= U_{ph} \cdot I_{ph} \cdot \cos(\varphi) + U_{ph} \cdot I_{ph} \cdot \cos(2\omega t - \varphi)$$

# Single phase active and reactive power

- **Voltage and current**

$$\begin{cases} u(t) = \hat{u}_{ph} \cdot \cos(\omega t) \\ i(t) = \hat{i}_{ph} \cdot \cos(\omega t - \varphi) \end{cases}$$

- **Active power**




$$P_{ave} = U_m \cdot I_m \cdot \cos(\varphi)$$

- **Reactive power**

$$Q_{av} = U_m \cdot I_m \cdot \sin(\varphi)$$

- **Apparent power**

$$S_{ave} = U_m \cdot I_m$$

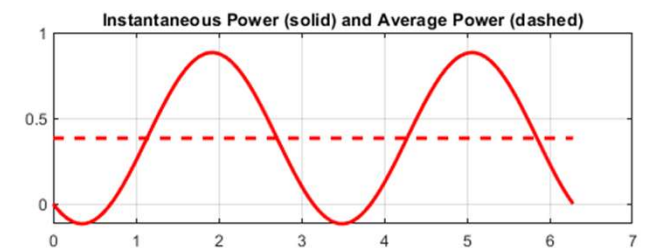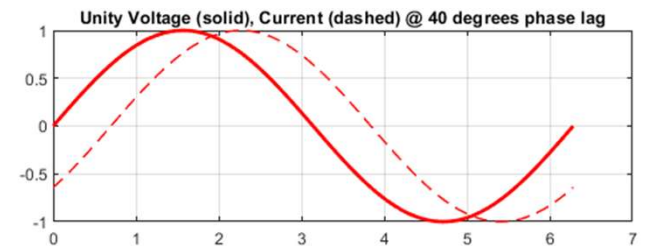
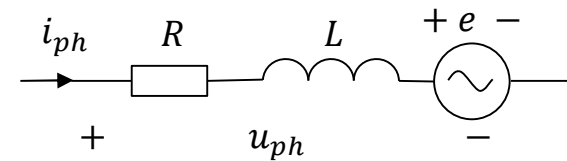


# Three phase voltage and current

$$\begin{cases} u_a(t) = \hat{u}_{ph} \cdot \cos(\omega t) = \sqrt{2} \cdot U_{ph} \cdot \cos(\omega t) \\ u_b(t) = \hat{u}_{ph} \cdot \cos\left(\omega t - \frac{2\pi}{3}\right) = \sqrt{2} \cdot U_{ph} \cdot \cos\left(\omega t - \frac{2\pi}{3}\right) \\ u_c(t) = \hat{u}_{ph} \cdot \cos\left(\omega t - \frac{4\pi}{3}\right) = \sqrt{2} \cdot U_{ph} \cdot \cos\left(\omega t - \frac{4\pi}{3}\right) \end{cases}$$

$$\begin{cases} i_a(t) = \hat{i}_{ph} \cdot \cos(\omega t - \varphi) = \sqrt{2} \cdot I_{ph} \cdot \cos(\omega t - \varphi) \\ i_b(t) = \hat{i}_{ph} \cdot \cos\left(\omega t - \frac{2\pi}{3} - \varphi\right) = \sqrt{2} \cdot I_{ph} \cdot \cos\left(\omega t - \frac{2\pi}{3} - \varphi\right) \\ i_c(t) = \hat{i}_{ph} \cdot \cos\left(\omega t - \frac{4\pi}{3} - \varphi\right) = \sqrt{2} \cdot I_{ph} \cdot \cos\left(\omega t - \frac{4\pi}{3} - \varphi\right) \end{cases}$$


$$\begin{cases} e_a = \hat{e} \cdot \cos(\omega \cdot t) = \sqrt{2} \cdot E_{ph} \cdot \cos(\omega \cdot t) \\ e_b = \hat{e} \cdot \cos\left(\omega \cdot t - \frac{2\pi}{3}\right) = \sqrt{2} \cdot E_{ph} \cdot \cos\left(\omega \cdot t - \frac{2\pi}{3}\right) \\ e_c = \hat{e} \cdot \cos\left(\omega \cdot t - \frac{4\pi}{3}\right) = \sqrt{2} \cdot E_{ph} \cdot \cos\left(\omega \cdot t - \frac{4\pi}{3}\right) \end{cases}$$

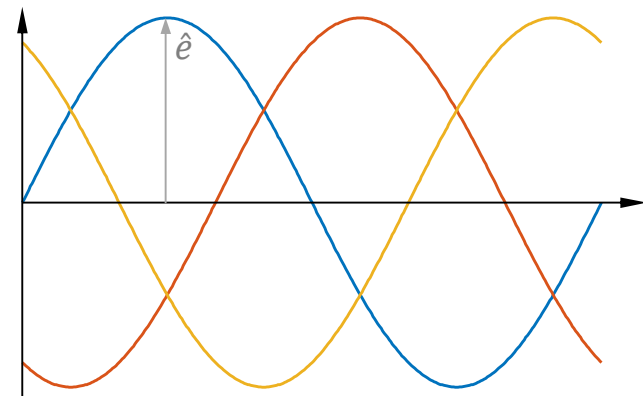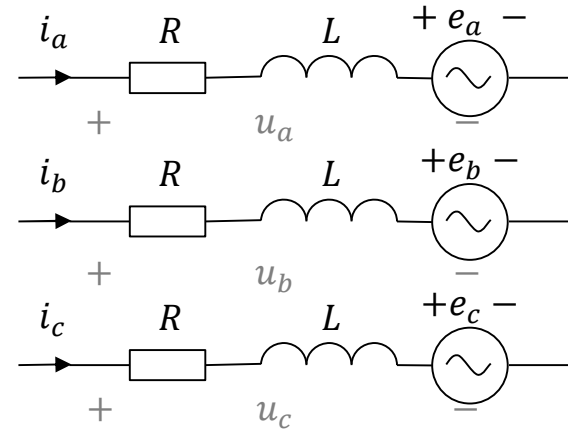
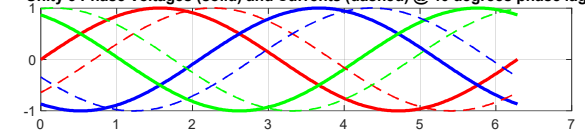
# Three phase power

$$\begin{aligned}
 p(t) &= \hat{u}_{ph} \cdot \hat{i}_{ph} \cdot \left( \cos(\omega t) \cdot \cos(\omega t - \varphi) + \cos\left(\omega t - \frac{2\pi}{3}\right) \cdot \cos\left(\omega t - \frac{2\pi}{3} - \varphi\right) + \cos\left(\omega t - \frac{4\pi}{3}\right) \cdot \cos\left(\omega t - \frac{4\pi}{3} - \varphi\right) \right) = \\
 &= \left\{ \cos(x) \cdot \cos(x - y) = \frac{\cos(y) + \cos(2 \cdot x + y)}{2} \right\} = \\
 &= \frac{\hat{u}_{ph} \cdot \hat{i}_{ph}}{2} \cdot \left( \cos(\varphi) + \cos(2\omega t - \varphi) + \cos(\varphi) + \cos\left(2\omega t - \frac{4\pi}{3} - \varphi\right) + \cos(\varphi) + \cos\left(2\omega t - \frac{8\pi}{3} - \varphi\right) \right) = \\
 &= \frac{\hat{u}_{ph} \cdot \hat{i}_{ph}}{2} \cdot \left( 3 \cdot \cos(\varphi) + \underbrace{\cos(2\omega t - \varphi) + \cos\left(2\omega t - \frac{2\pi}{3} - \varphi\right) + \cos\left(2\omega t - \frac{4\pi}{3} - \varphi\right)}_{=0} \right) = \\
 &= 3 \cdot \frac{\sqrt{2} \cdot U_{ph} \cdot \sqrt{2} \cdot I_{ph}}{2} \cdot \cos(\varphi) = \\
 &= 3 \cdot U_{ph} \cdot I_{ph} \cdot \cos(\varphi) = \sqrt{3} \cdot U_{ph\_ph} \cdot I_{ph} \cdot \cos(\varphi)
 \end{aligned}$$


Unity 3 Phase Voltages (solid) and Currents (dashed) @ 40 degrees phase lag





3 Phase Powers



Total Power

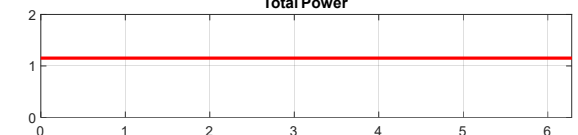

# The generic 3-phase load

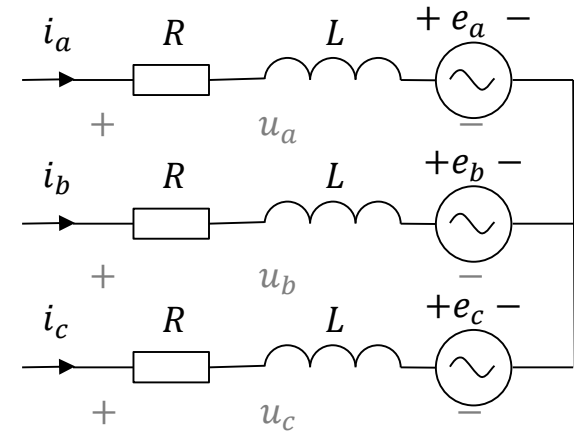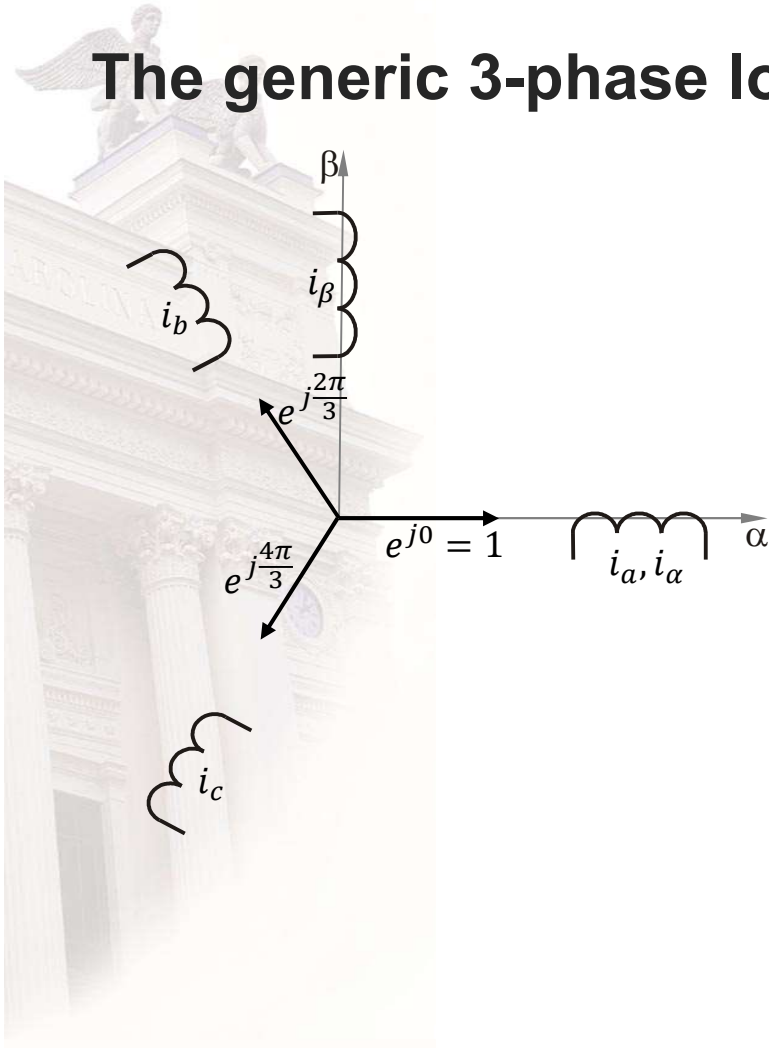

$$\begin{aligned} & \sqrt{\frac{2}{3}} \cdot e^{j0} \cdot \left( u_a = R \cdot i_a + L \cdot \frac{di_a}{dt} + e_a \right) \\ & \sqrt{\frac{2}{3}} \cdot e^{j\frac{2\pi}{3}} \cdot \left( u_b = R \cdot i_b + L \cdot \frac{di_b}{dt} + e_b \right) \\ & + \sqrt{\frac{2}{3}} \cdot e^{j\frac{4\pi}{3}} \cdot \left( u_c = R \cdot i_c + L \cdot \frac{di_c}{dt} + e_c \right) \end{aligned}$$


---


$$\vec{u} = R \cdot \vec{i} + L \cdot \frac{d\vec{i}}{dt} + \vec{e}$$

$$p(t) = u_a \cdot i_a + u_b \cdot i_b + u_c \cdot i_c = u_\alpha \cdot i_\alpha + u_\beta \cdot i_\beta$$


## Example, grid voltage vector

$$\begin{aligned}\vec{e} &= \sqrt{\frac{2}{3}} \cdot (e_a + e_b \cdot e^{j\frac{2\pi}{3}} + e_c \cdot e^{j\frac{4\pi}{3}}) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left( \cos(\omega \cdot t) + \cos\left(\omega \cdot t - \frac{2\pi}{3}\right) \cdot \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) + \cos\left(\omega \cdot t - \frac{4\pi}{3}\right) \cdot \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \right) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left( \cos(\omega \cdot t) + \left( \cos(\omega \cdot t) \cdot \cos\left(\frac{2\pi}{3}\right) + \sin(\omega \cdot t) \cdot \sin\left(\frac{2\pi}{3}\right) \right) \cdot \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) \right. \\ &\quad \left. + \left( \cos(\omega \cdot t) \cdot \cos\left(\frac{4\pi}{3}\right) + \sin(\omega \cdot t) \cdot \sin\left(\frac{4\pi}{3}\right) \right) \cdot \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \right) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left( \cos(\omega \cdot t) \cdot \left(1 + \frac{1}{4} + \frac{1}{4}\right) + j \cdot \sin(\omega \cdot t) \cdot \left(\frac{3}{4} + \frac{3}{4}\right) \right) = \\ &= \sqrt{\frac{3}{2}} \cdot \hat{e} \cdot (\cos(\omega \cdot t) + j \cdot \sin(\omega \cdot t)) = E \cdot e^{j\omega t}\end{aligned}$$



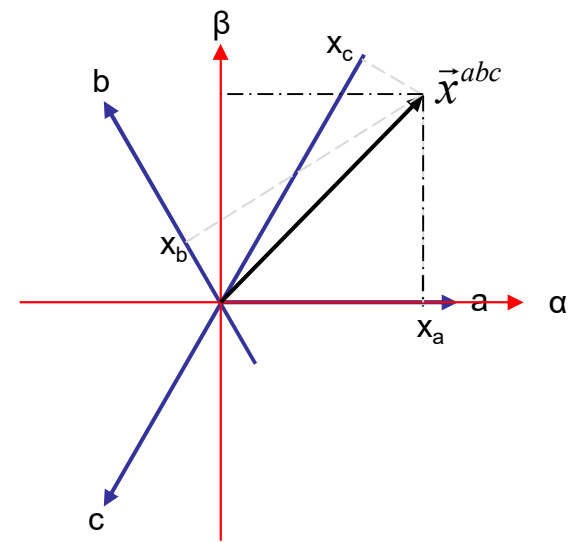
## Transformation example: $abc \rightarrow \alpha\beta$

$$\begin{aligned} \vec{x}^{\alpha\beta} &= x_\alpha + j \cdot x_\beta = \sqrt{\frac{2}{3}} \cdot (x_a \cdot e^{j0} + x_b \cdot e^{j\frac{2\pi}{3}} + x_c \cdot e^{j\frac{4\pi}{3}}) = \\ &= \sqrt{\frac{2}{3}} \cdot \left( x_a + x_b \cdot \left( -\frac{1}{2} + j \cdot \frac{\sqrt{3}}{2} \right) + x_c \cdot \left( -\frac{1}{2} - j \cdot \frac{\sqrt{3}}{2} \right) \right) \\ x_\alpha &= \sqrt{\frac{2}{3}} \cdot \left( x_a - \frac{x_b}{2} - \frac{x_c}{2} \right) = \sqrt{\frac{2}{3}} \cdot x_a - \frac{\sqrt{2}}{2 \cdot \sqrt{3}} \cdot x_b - \frac{\sqrt{2}}{2 \cdot \sqrt{3}} \cdot x_c = \\ &= \sqrt{\frac{2}{3}} \cdot x_a - \frac{1}{\sqrt{6}} \cdot (x_b + x_c) \\ x_\beta &= \sqrt{\frac{2}{3}} \cdot \left( \frac{\sqrt{3}}{2} \cdot x_b - \frac{\sqrt{3}}{2} \cdot x_c \right) = \frac{\sqrt{2}}{\sqrt{3}} \cdot \frac{\sqrt{3}}{2} \cdot x_b - \frac{\sqrt{2}}{\sqrt{3}} \cdot \frac{\sqrt{3}}{2} \cdot x_c = \\ &= \frac{1}{\sqrt{2}} \cdot (x_b - x_c) \end{aligned}$$



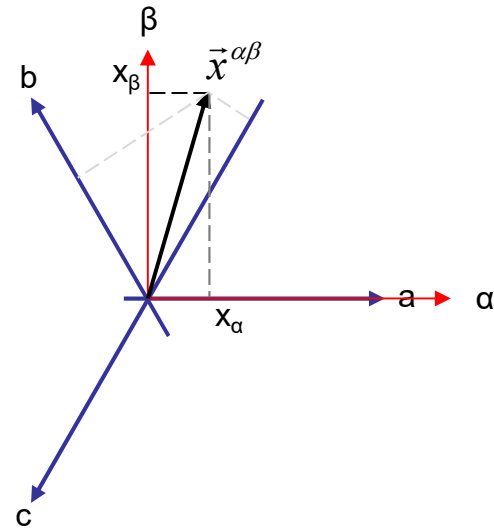
## Transformation example: $\alpha\beta \rightarrow abc$

$$\begin{cases} x_a = \sqrt{\frac{2}{3}} \cdot x_\alpha \\ x_b = \sqrt{\frac{2}{3}} \cdot \left( -\frac{x_\alpha}{2} + x_\beta \cdot \frac{\sqrt{3}}{2} \right) = -\frac{x_\alpha}{\sqrt{6}} + x_\beta \cdot \frac{1}{\sqrt{2}} \\ x_c = \sqrt{\frac{2}{3}} \cdot \left( -\frac{x_\alpha}{2} - x_\beta \cdot \frac{\sqrt{3}}{2} \right) = -\frac{x_\alpha}{\sqrt{6}} - x_\beta \cdot \frac{1}{\sqrt{2}} \end{cases}$$




# 3-phase converter

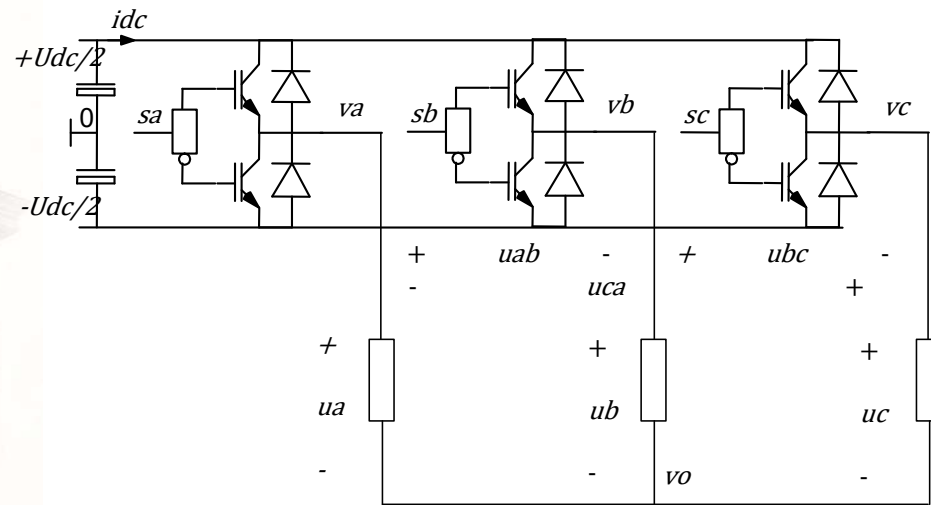

$$v_o = \frac{v_a + v_b + v_c}{3}$$

# 3-phase output voltage → as vector : I

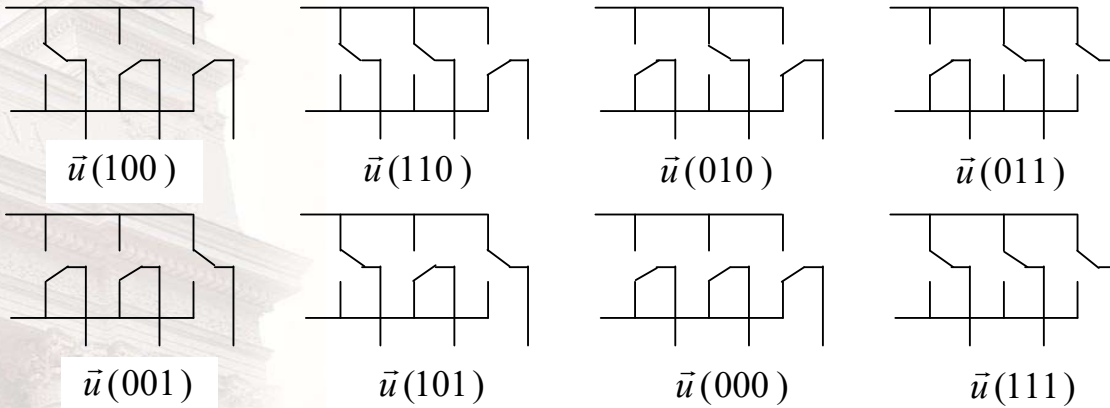


$v_a$	$v_b$	$v_c$	$v_o$	$u_a$	$u_b$	$u_c$	$u_\alpha$	$u_\beta$
-1	-1	-1						
-1	-1	1						
-1	1	-1						
-1	1	1						
1	-1	-1						
1	-1	1						
1	1	-1						
1	1	1						

$u_a = v_a - v_o$



$v_o = (v_a + v_b + v_c)/3$

$\times U_{dc}/2$

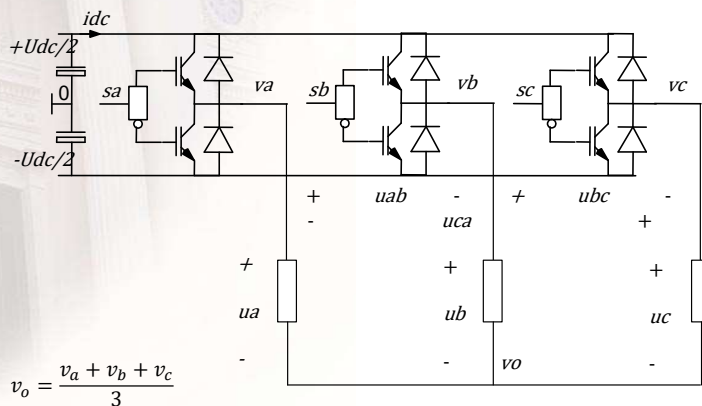

$$\vec{u}^{\alpha\beta} = \sqrt{\frac{3}{2}} \cdot u_a + j \frac{1}{\sqrt{2}} \cdot (u_b - u_c) = u_\alpha + j \cdot u_\beta$$

# 3-phase converters – 8 switch states

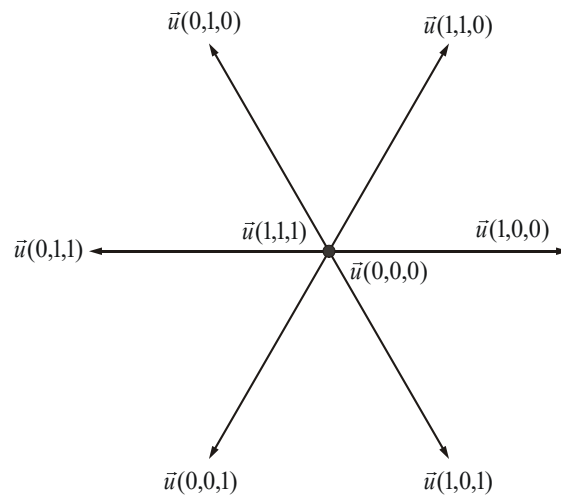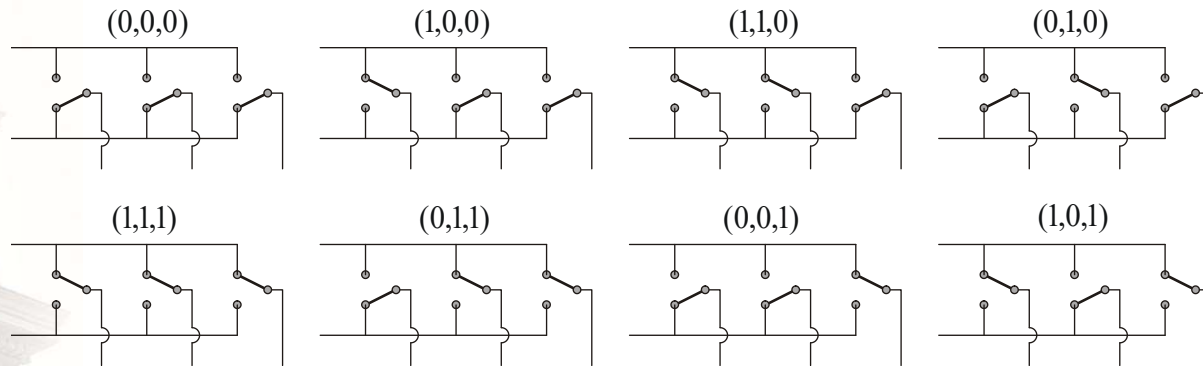

$$\bar{u}(1,0,0) = \sqrt{\frac{2}{3}} U_{dc} = -\bar{u}(0,1,1)$$

$$\bar{u}(0,1,0) = \sqrt{\frac{2}{3}} U_{dc} \cdot e^{j\frac{2\pi}{3}} = -\bar{u}(1,0,1)$$


$$\bar{u}(0,0,1) = \sqrt{\frac{2}{3}} U_{dc} \cdot e^{j\frac{4\pi}{3}} = -\bar{u}(1,1,0)$$

$$\bar{u}(0,0,0) = 0 = \bar{u}(1,1,1)$$
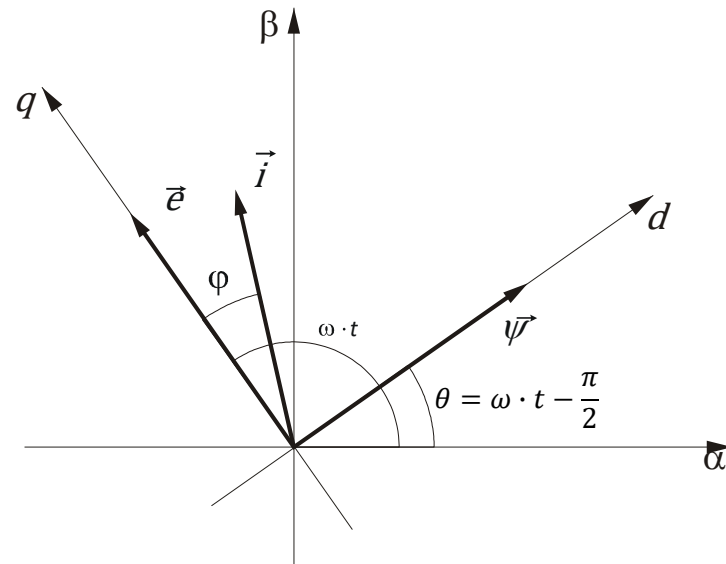
## Rotating reference frame

- Use the integral of the grid back emf vector:

$$\begin{aligned}\vec{\psi} &= \int_0^t \vec{e} \cdot dt = \int_0^t E \cdot e^{j\omega \cdot t} dt = \frac{\vec{e}}{j \cdot \omega} \\ &= \frac{E}{\omega} e^{j(\omega \cdot t - \frac{\pi}{2})}\end{aligned}$$



# Introduce the grid flux reference frame (d,q) ...

- Express the stator equation in the rotor reference frame

$$\vec{u}^{\alpha\beta} = R \cdot \vec{i}^{\alpha\beta} + L \cdot \frac{d\vec{i}^{\alpha\beta}}{dt} + \vec{e}^{\alpha\beta}$$

$$\left\{ \vec{s}^{\alpha\beta} = \vec{s}^{dq} \cdot e^{j\theta} \right\}$$


$$\begin{aligned} \vec{u}_s^{dq} \cdot e^{j\theta} &= R \cdot \vec{i}^{dq} \cdot e^{j\theta} + L \cdot \frac{d}{dt} (\vec{i}^{dq} \cdot e^{j\theta}) + \vec{e}^{dq} \cdot e^{j\theta} = \\ &= R \cdot \vec{i}^{dq} \cdot e^{j\theta} + L \cdot \frac{d\vec{i}^{dq}}{dt} \cdot e^{j\theta} + j \cdot \frac{d\theta}{dt} \cdot L \cdot \vec{i}^{dq} \cdot e^{j\theta} + \vec{e}^{dq} \cdot e^{j\theta} = \end{aligned}$$

$$\vec{u}_s^{dq} = R \cdot \vec{i}^{dq} + L \cdot \frac{d\vec{i}^{dq}}{dt} + j \cdot \omega \cdot L \cdot \vec{i}^{dq} + \vec{e}^{dq}$$

- Split up the complex equation in real- and imaginary parts:

$$u_d = R \cdot i_d + L \cdot \frac{di_d}{dt} - \omega \cdot L \cdot i_q$$
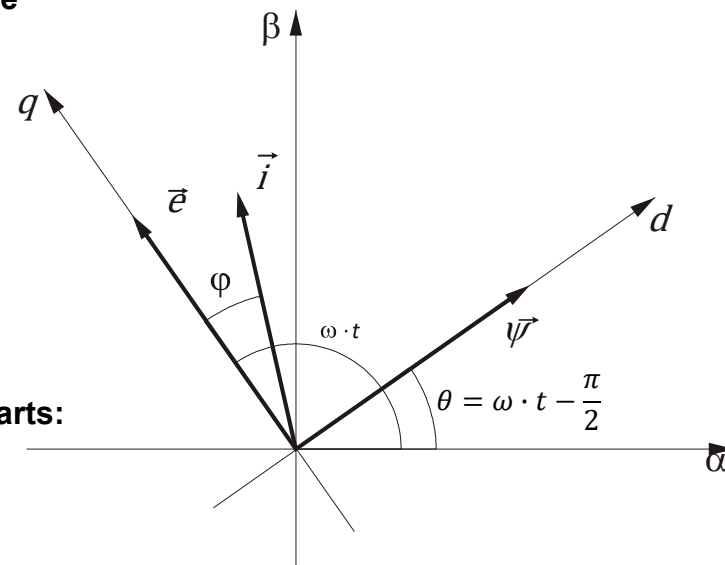
$$u_q = R \cdot i_q + L \cdot \frac{di_q}{dt} + \omega \cdot L \cdot i_d + e_q$$



## Active power ...

- Express the terminal power of the load

$$\vec{u} = R \cdot \vec{i} + L \cdot \frac{d\vec{i}}{dt} + j \cdot \omega \cdot L \cdot \vec{i} + \vec{e}$$

$$p(t) = \text{Re}\{\vec{u} \cdot \vec{i}^*\} = \text{Re}\left\{R \cdot \vec{i} \cdot \vec{i}^* + L \cdot \frac{d\vec{i}}{dt} \cdot \vec{i}^* + j \cdot \omega \cdot L \cdot \vec{i} \cdot \vec{i}^* + \vec{e} \cdot \vec{i}^*\right\} =$$

$$= \underbrace{Ri_d^2 + Ri_q^2}_1 + \underbrace{L \frac{di_d}{dt} i_d + L \frac{di_q}{dt} i_q}_2 + \underbrace{e_q i_q}_3$$



Resistive losses

Energizing inductances

Power absorbed by the grid back emf

Stationarity:

$$p(t) = E \cdot |\vec{i}| \cdot \cos(\varphi) = E \cdot \sqrt{\frac{3}{2}} \cdot |\hat{i}_{phase}| \cdot \cos(\varphi) = \sqrt{3} \cdot E \cdot I_{rms,phase} \cdot \cos(\varphi)$$

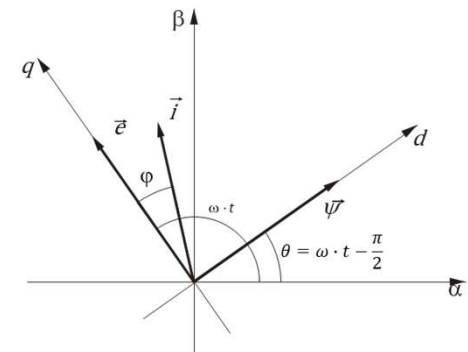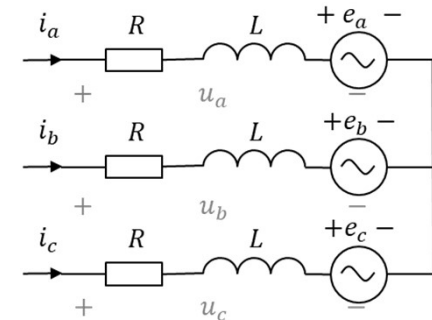




## 3-phase converters - sinusoidal references

- Assume a rotating voltage reference vector

$$\vec{u}^* = u^* \cdot e^{j\omega t} = u^* \cdot (\cos(\omega t) + j \cdot \sin(\omega t)) = u_\alpha^* + j \cdot u_\beta^*$$

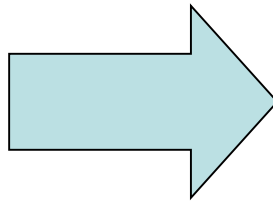
$$\begin{aligned} u_a^* &= \sqrt{\frac{2}{3}} u_\alpha^* \\ u_b^* &= \frac{1}{\sqrt{2}} u_\beta^* - \frac{1}{\sqrt{6}} u_\alpha^* \\ u_c^* &= -\frac{1}{\sqrt{2}} u_\beta^* - \frac{1}{\sqrt{6}} u_\alpha^* \end{aligned}$$



$$\begin{aligned} u_a^* &= \sqrt{\frac{2}{3}} \cdot u^* \cos(\omega t) \\ u_b^* &= \sqrt{\frac{2}{3}} \cdot u^* \cos\left(\omega t - \frac{2\pi}{3}\right) \\ u_c^* &= \sqrt{\frac{2}{3}} \cdot u^* \cos\left(\omega t - \frac{4\pi}{3}\right) \end{aligned}$$

## 3-phase converters modulation

Simplest with sinusoidal references...

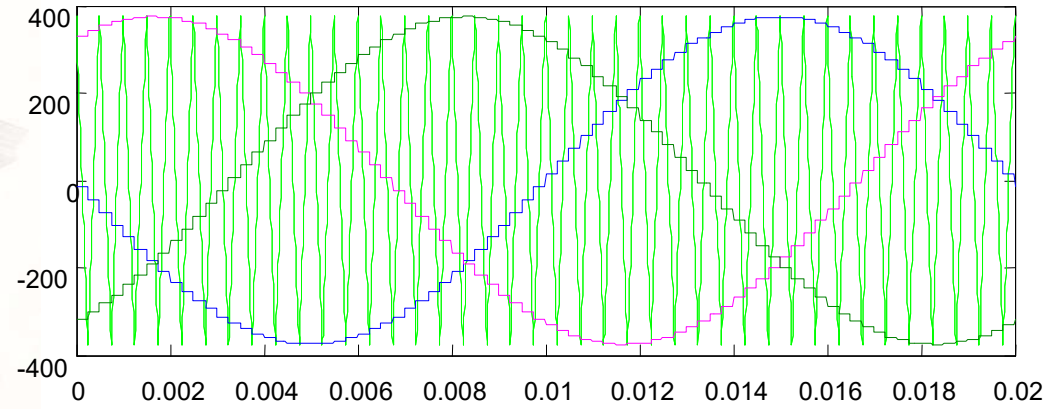

... but the DC link voltage is badly utilized.


## 3-phase converters – symmetrization

- 3 phase potentials, only 2 vector components. One degree of freedom to be used for other purposes.

$$v_{az}^* = u_a^* - v_z^*$$



$$v_{bz}^* = u_b^* - v_z^*$$

$$v_{cz}^* = u_c^* - v_z^*$$

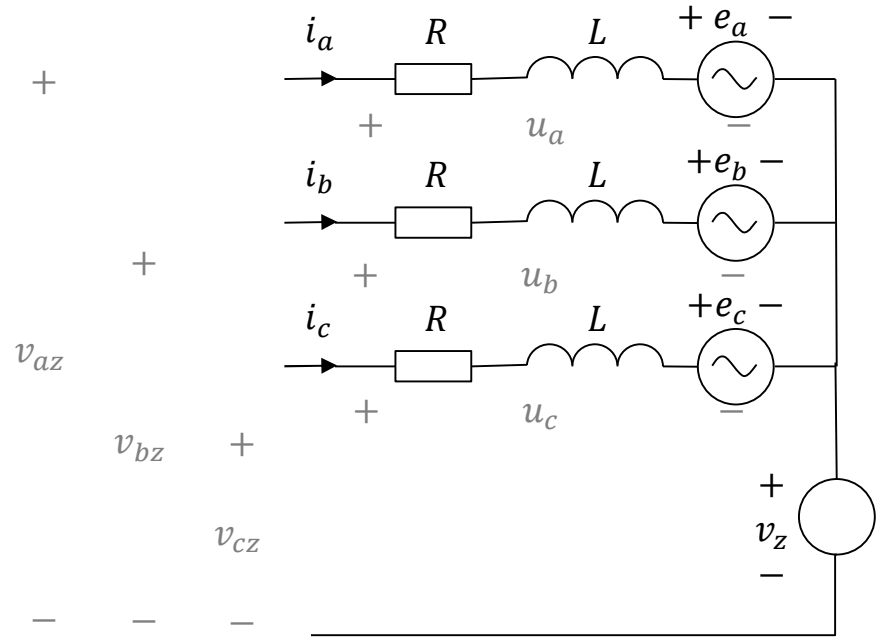
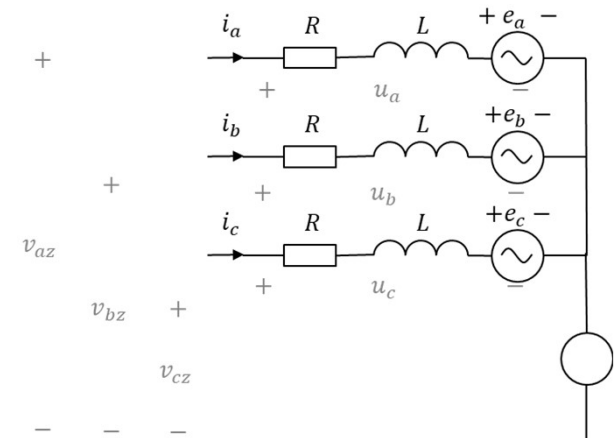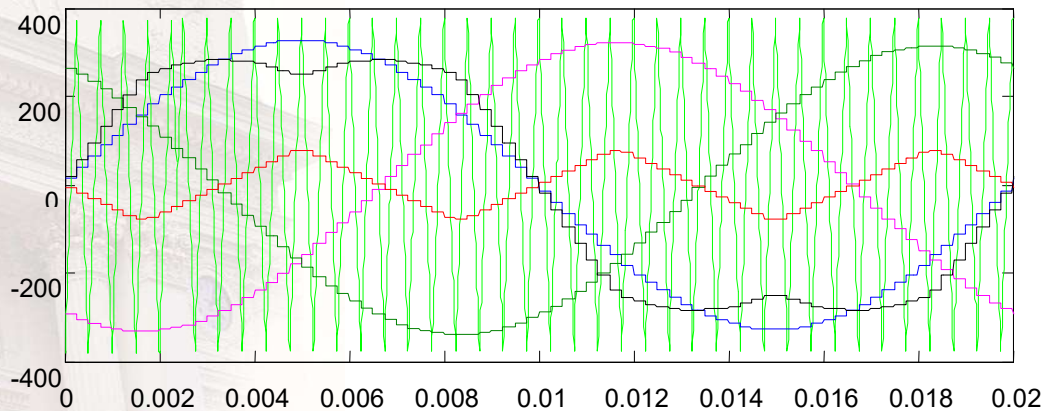
### 3-phase symmetrized modulation


$$v_z^* = \frac{\max(u_a^*, u_b^*, u_c^*) + \min(u_a^*, u_b^*, u_c^*)}{2}$$



Maximum phase voltage with sinusoidal modulation :  $U_{dc}/2$   
 Maximum phase-to phase voltage with symmetrized modulation :  $U_{dc}$  -  
 > Phase voltage  $U_{dc}/\sqrt{3}$ , i.e.  $2/\sqrt{3}=1.15$  times larger than with  
 sinusoidal modulation.


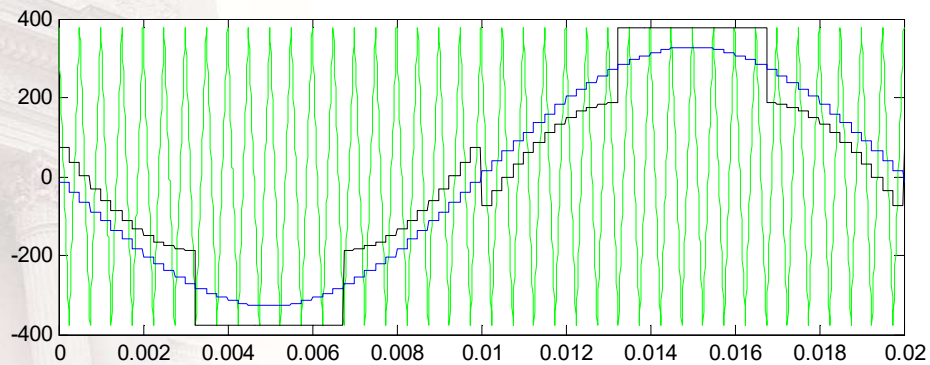
### 3-phase minimum switching modulation

$$v_z^* = - \min \left( \frac{U_{dc}}{2} - \max(u_a^*, u_b^*, u_c^*), -\frac{U_{dc}}{2} - \min(u_a^*, u_b^*, u_c^*) \right)$$




One phase is not switching for 2 60 degree intervals ...

# Modulation sequence vs. ripple

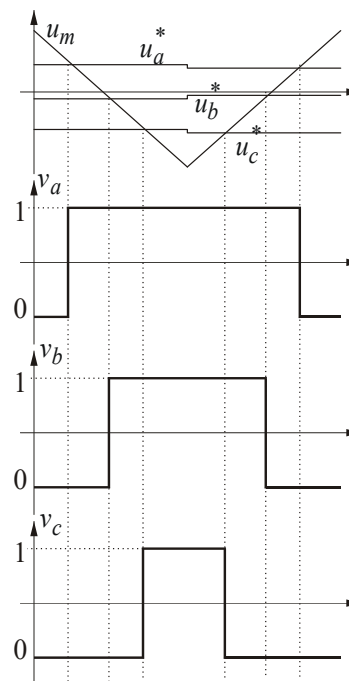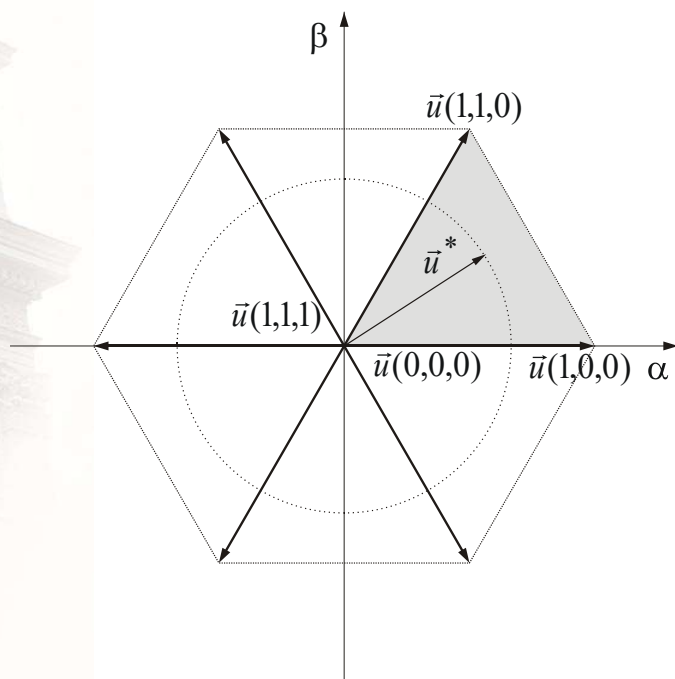

$$\vec{u}^{\alpha\beta} = R \cdot \vec{i}^{\alpha\beta} + L \cdot \frac{d\vec{i}^{\alpha\beta}}{dt} + \vec{e}^{\alpha\beta}$$

# Modulation sequence vs. ripple

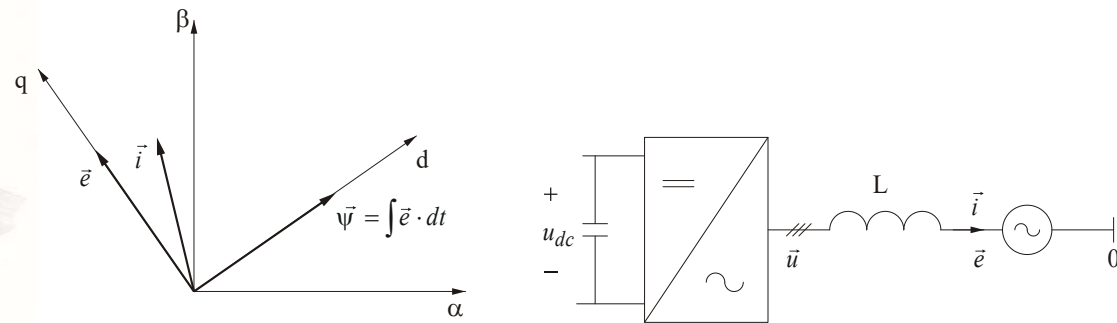

Current ripple in the (d,q)-frame

$$\frac{d\vec{i}}{dt} = \frac{\vec{u} - \vec{e}}{L}$$

