

Structures of the Energy flow system

Mechatronics 2007



Mekatronics - energiflow

Structures of the energy conversion system (< 1 h)

- Primary energy to output
- Electrical as intermediate

Power electronic converters as components (< 3 h)

- AC/DC/AC
- Modulation
- Power Units (50 Hz / SMPS / Integration)
- Passive components / Integration of passives

Electromechanical converters as components (< 3 h)

- Conv. machine types
- Elektrostrictive/magnetostrictive converters
- Cooling
- Power and Energy density

Energyconverters as construction elements (< 1 h)

- Laminated steel / powder pressing / injection moulding

Powerelectronic measurements (< 2 h)

- Current / voltage / flux
- Torque /speed / position
- Preassure / flow (in pumps)



Energy processed in several steps





- **Primary energy source**
 - (chemical, mechanical, electrical)
- **Intermediate electrical energy storage**
 - (capacitive, inductive, ...)
- **Output energy**
 - (mechanical, heat, light, sound,...)



Primary energy sources

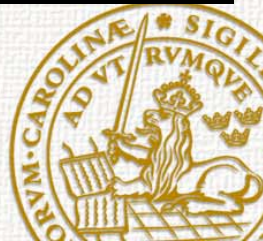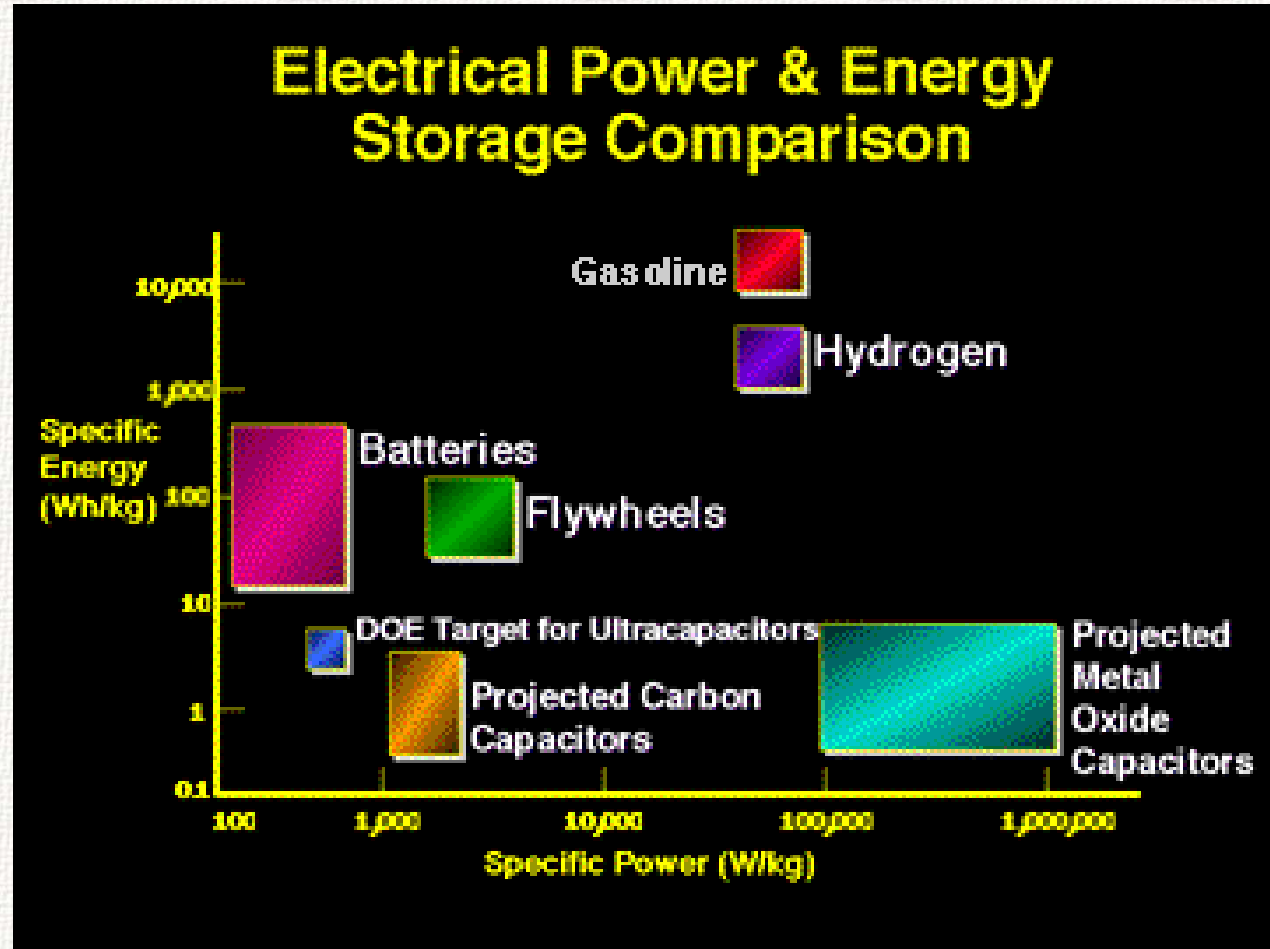- **Chemical**
 - Batteries
 - fuel cell with hydrogen
 - Combustion
 - Capacitors
- **Electrical**
 - Power grid
- **Mechanical**
 - Flywheel
- **Solar power**
 - Max 10...15%
1000 W/m²





Primary to intermediate energy conversion

- **AC to rectified DC**
 - 230 V / 50 Hz to almost 325 V (single phase rectifier)
 - 400 V / 50 Hz to almost 540 V (three phase rectifier)
- **AC to low voltage DC**
 - Transformer + rectifier
 - Switched Mode Power Supply (SMPS)
- **DC to DC**
 - Non-isolated, step down
 - Non-isolated, step up
 - Isolated



AC to rectified DC – 1 phase

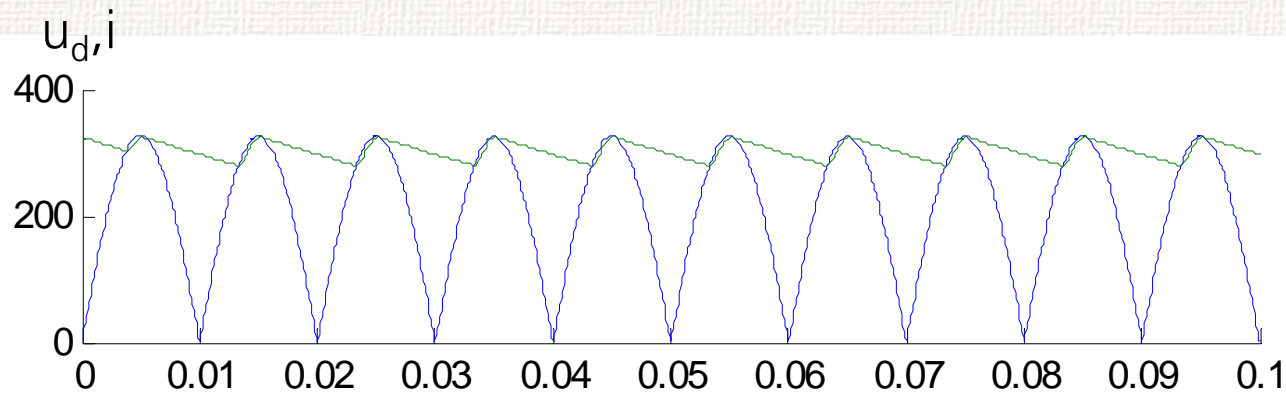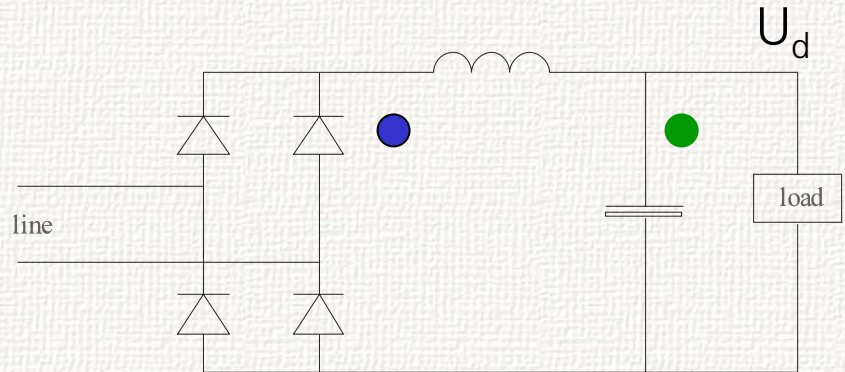- **High harmonic content in the line current**





$$U_d = \frac{2}{\pi} * \hat{U} \approx 0.9 * U_{rms}$$



AC to rectified DC – 3 phase

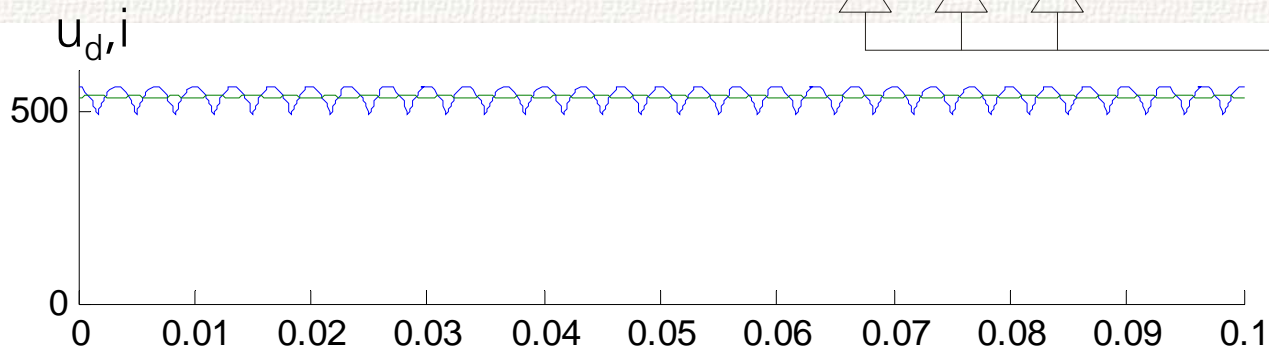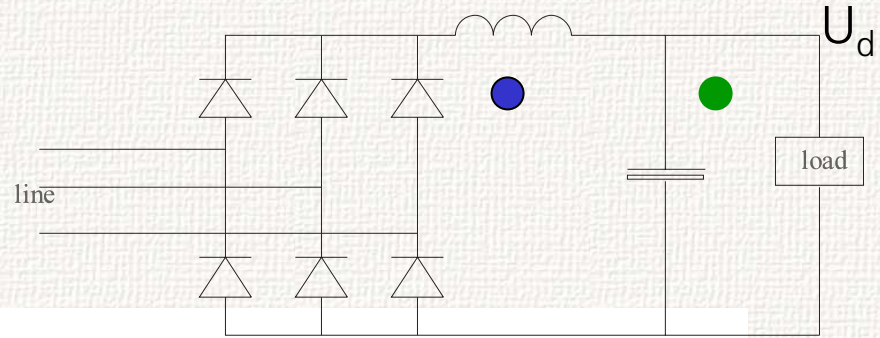- **High harmonic content in the line current**




$$U_d = \frac{3}{\pi} * \hat{U}_h \approx 1.35 * U_{h,rms}$$



AC to low voltage DC

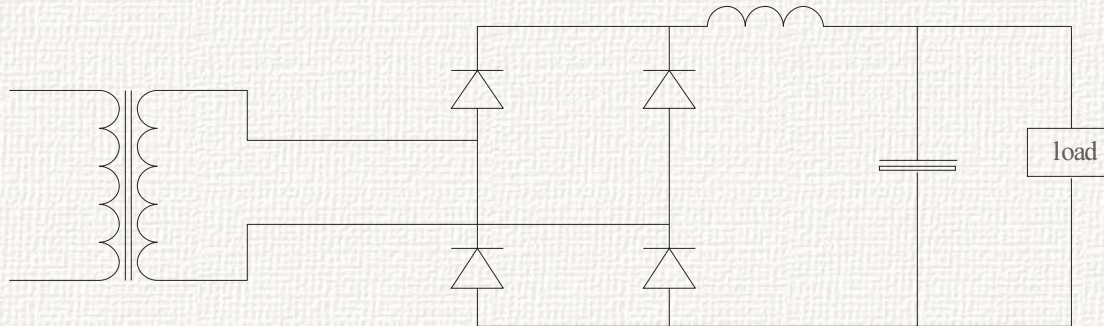
- **Step down transformer + rectifier. Still the same problem with high harmonics in the line current.**
- **Galvanic isolation**



SMPS – Switched Mode Power Supplies


• Function

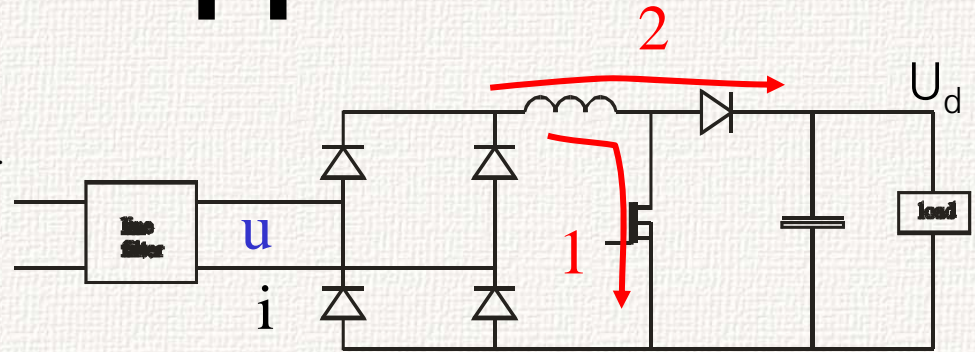- Transistor “on” -> increasing inductor current through transistor
- Transistor off -> decreasing inductor current through diode



• Advantages:

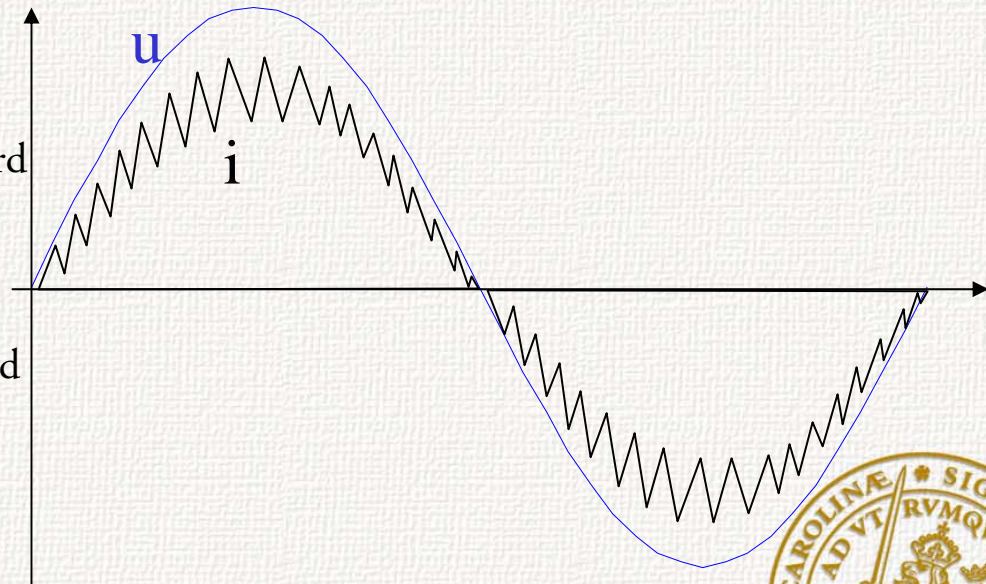
- Output voltage greater than input voltage (universal input);
- Simple control;
- Input inductance acts like a filter toward AC line;
- Many control ICs available on the market.
- PFC of 0.95 or better over line and load variations.






Switched mode power supplies for low voltage DC with flyback

- **Features:**

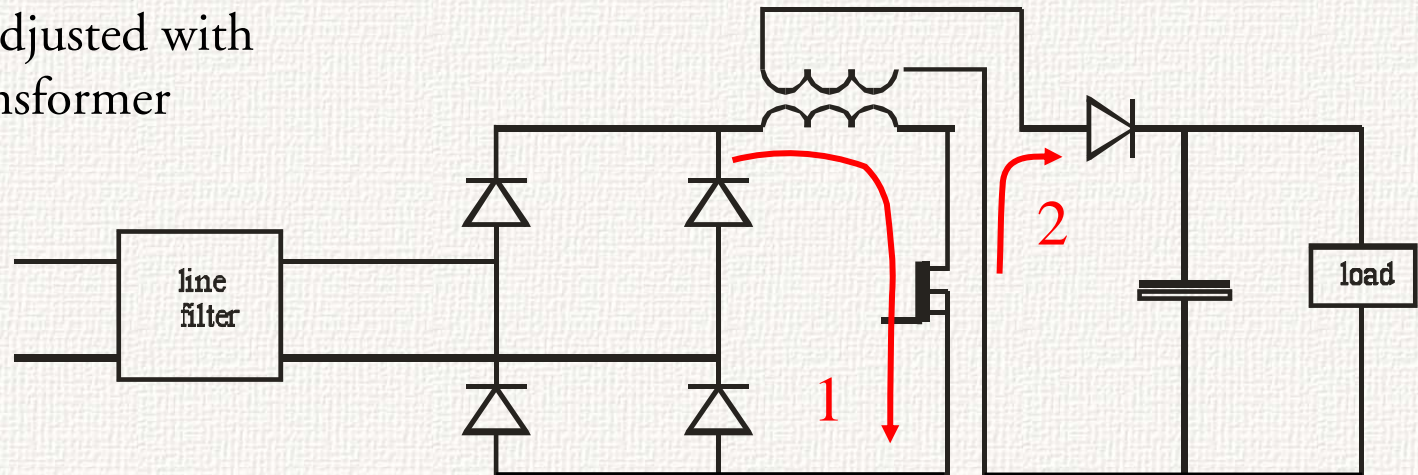
- Galvanic isolation to the feeding grid
- Output voltage range adjusted with the transformer ratio



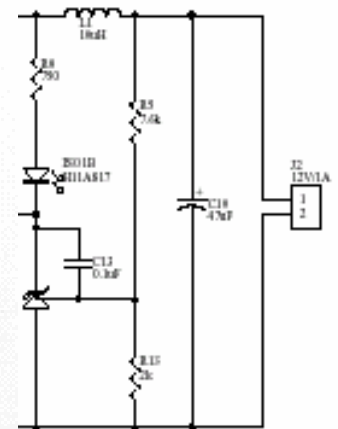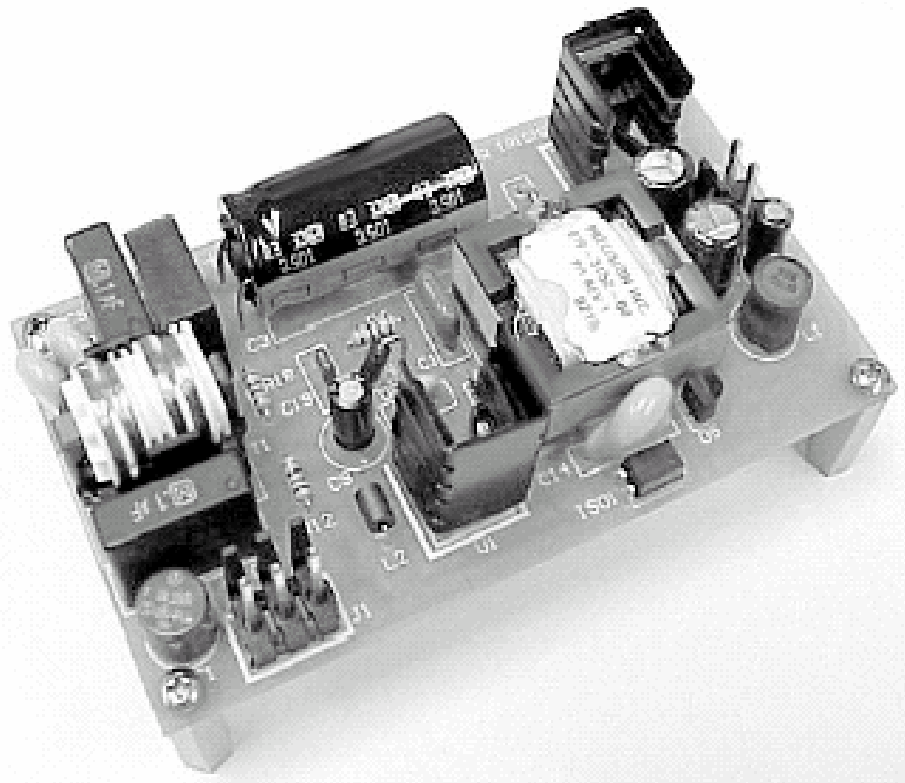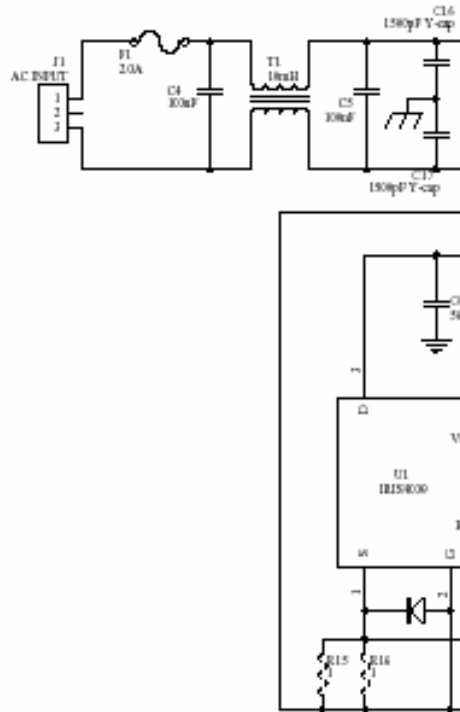
Example from <http://www.irf.com/technical-info/refdesigns/irismmps4.pdf>




Kvadranter

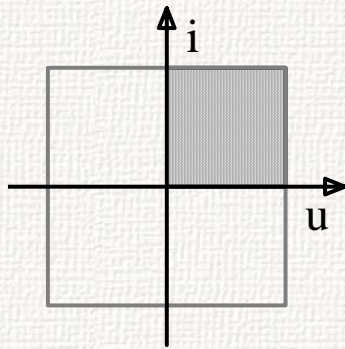


1-kvadrant

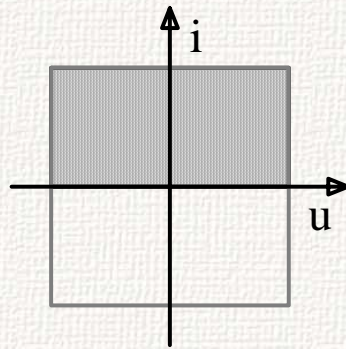

2-kvadrant

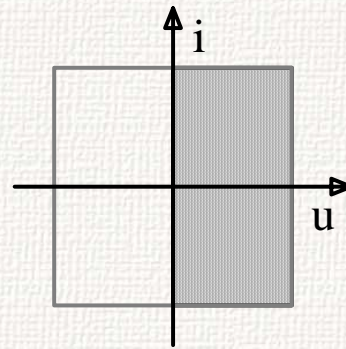

3-kvadrant

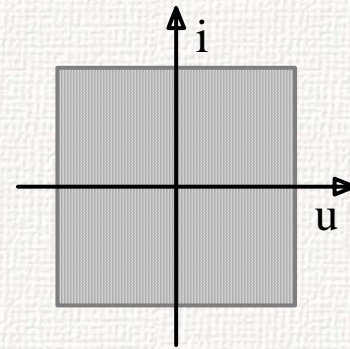


4-kvadrant





1-quadrant step down converter (buck-converter)

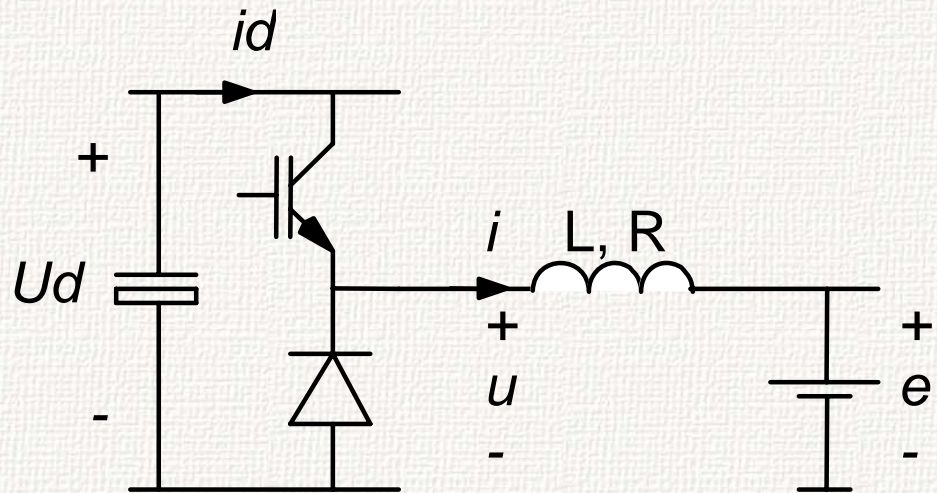- Output voltage lower than input voltage
- Output current positive




Control of 1-q. buck converter.

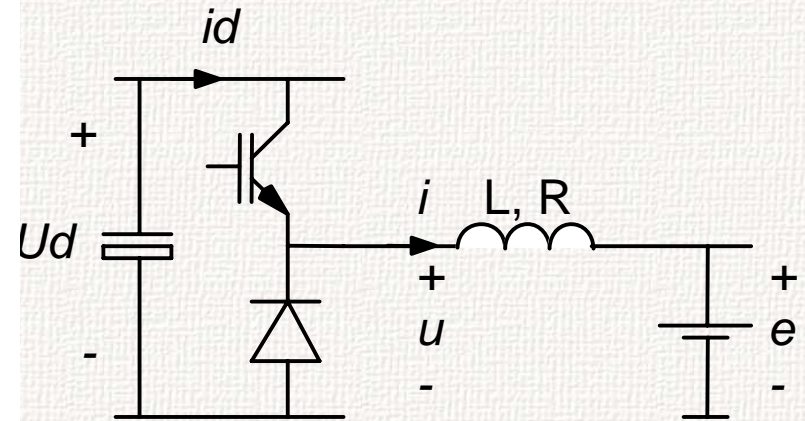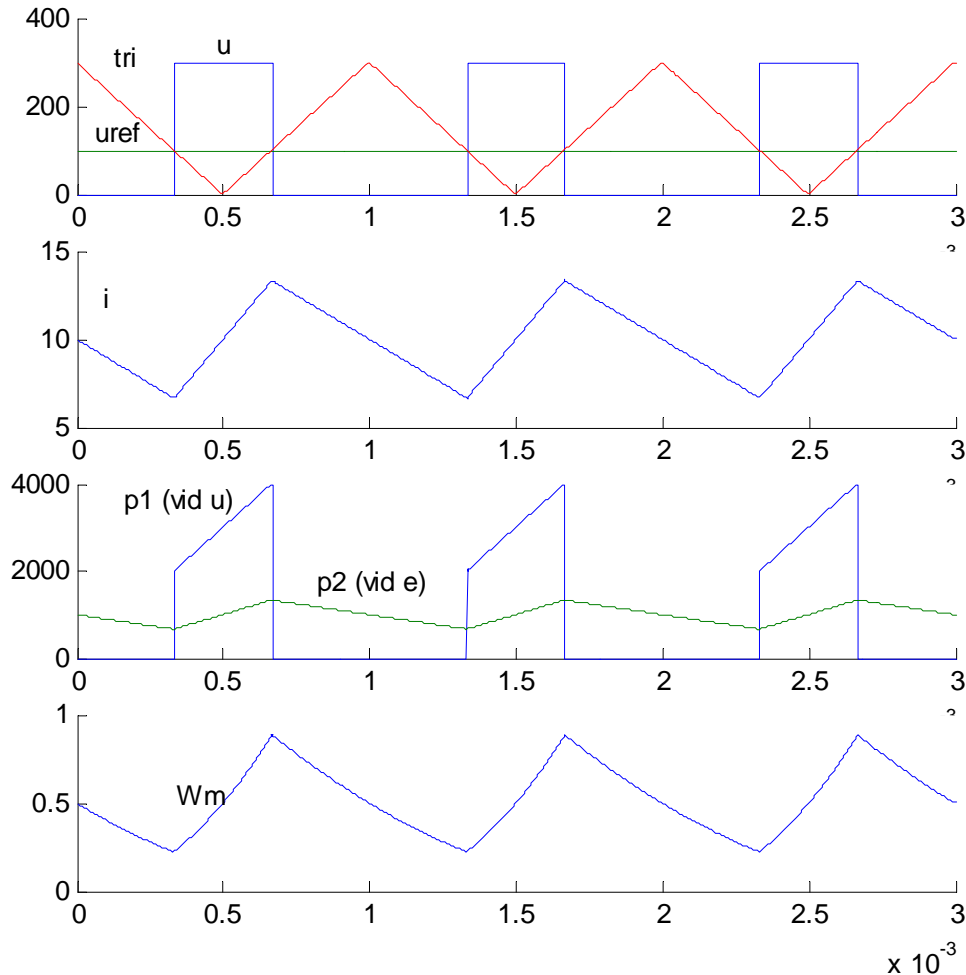


1-quadrant **step up converter** (**boost-converter**)

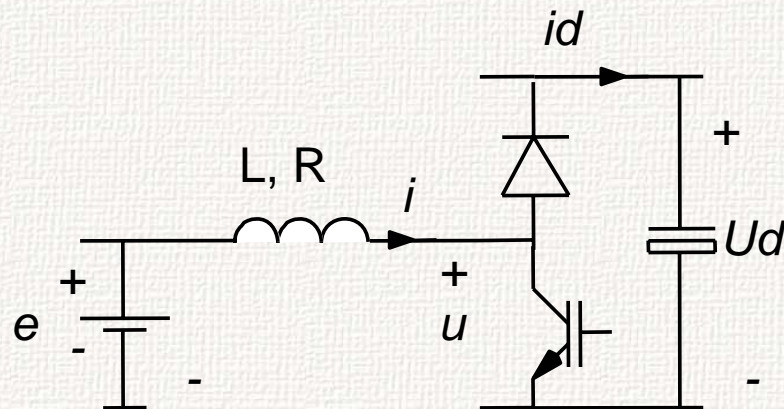- **Output voltage higher than input voltage**
- **Output current positive**




Styrning av 1-kv. Uppsp.omv



U

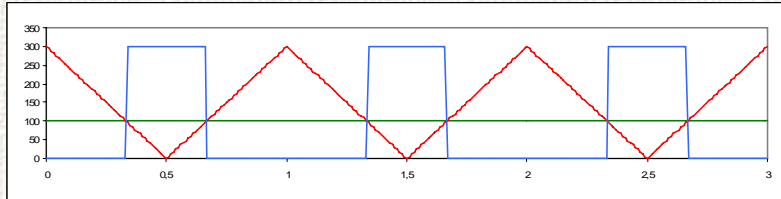

i


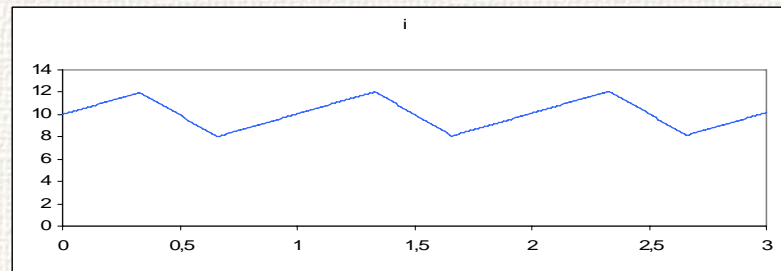


i_d

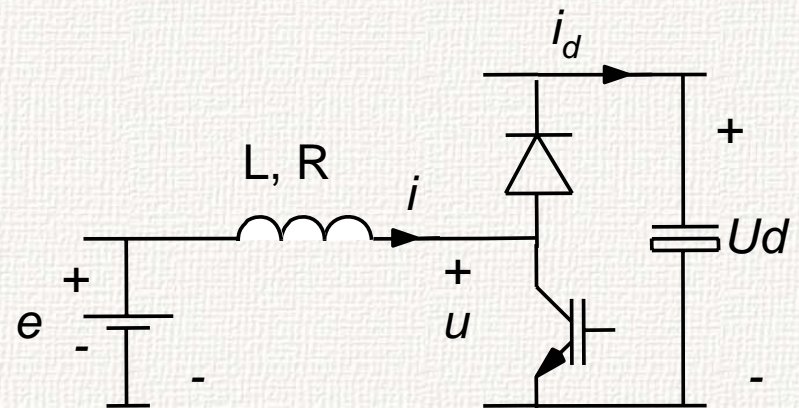
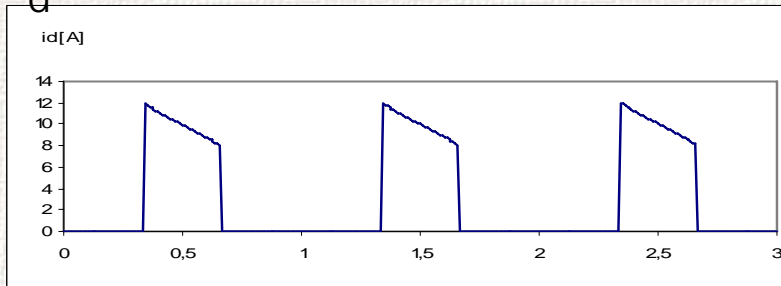


2-quadrant DC converter

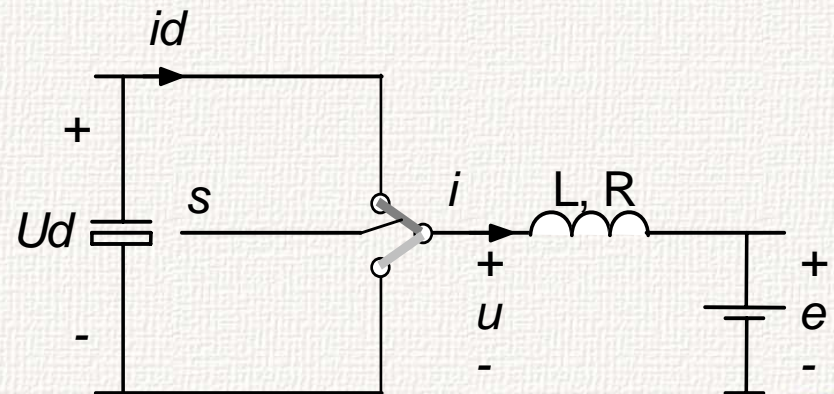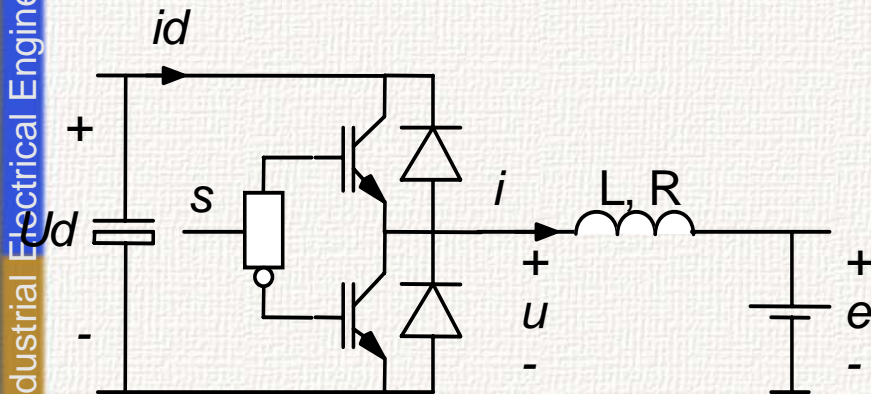- Current can be negative
- Both directions for energy flow
 - Voltage unipolar, current bipolar
- Equivalent switch:




Control of 2-Q. converter.

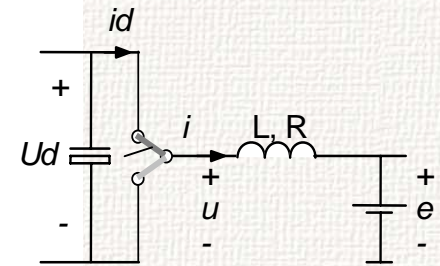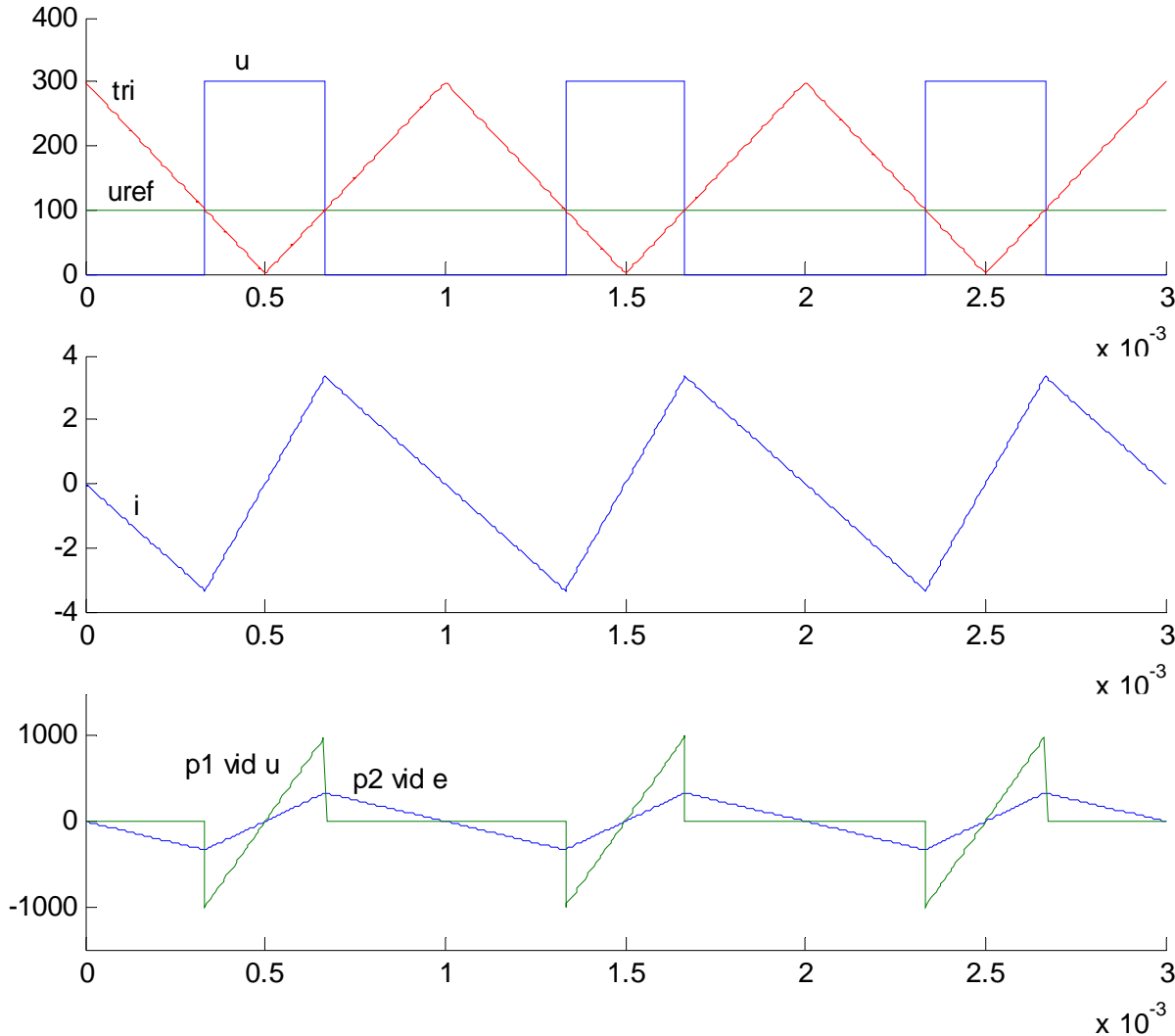


4-Quadrant DC converter

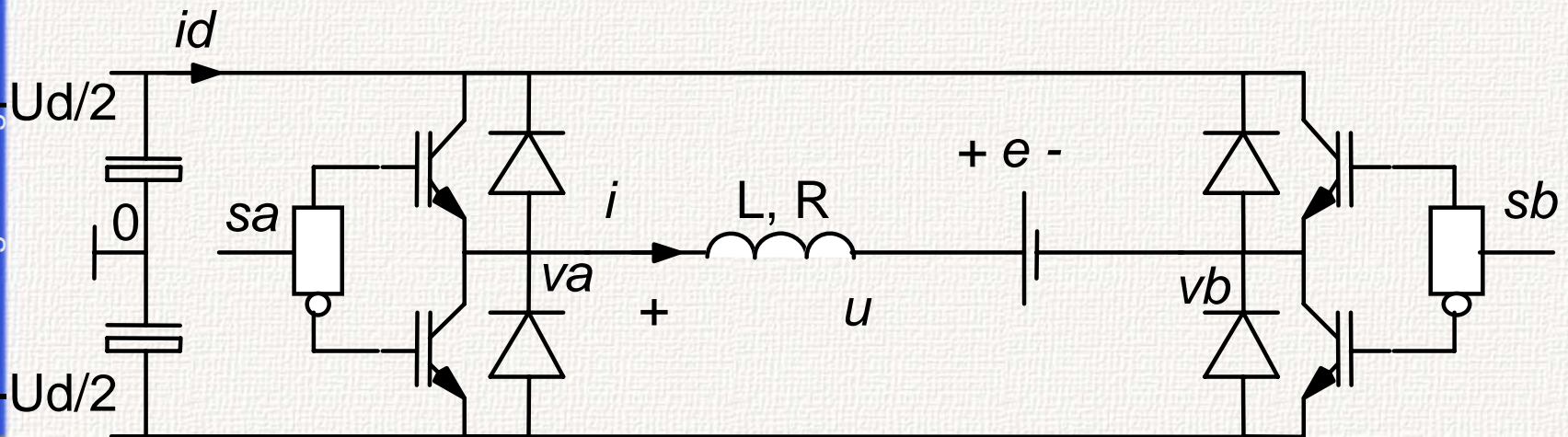
- All combinations of voltage and current
- AC-voltage
- Both directions for energy flow



Control of 4-Q converter

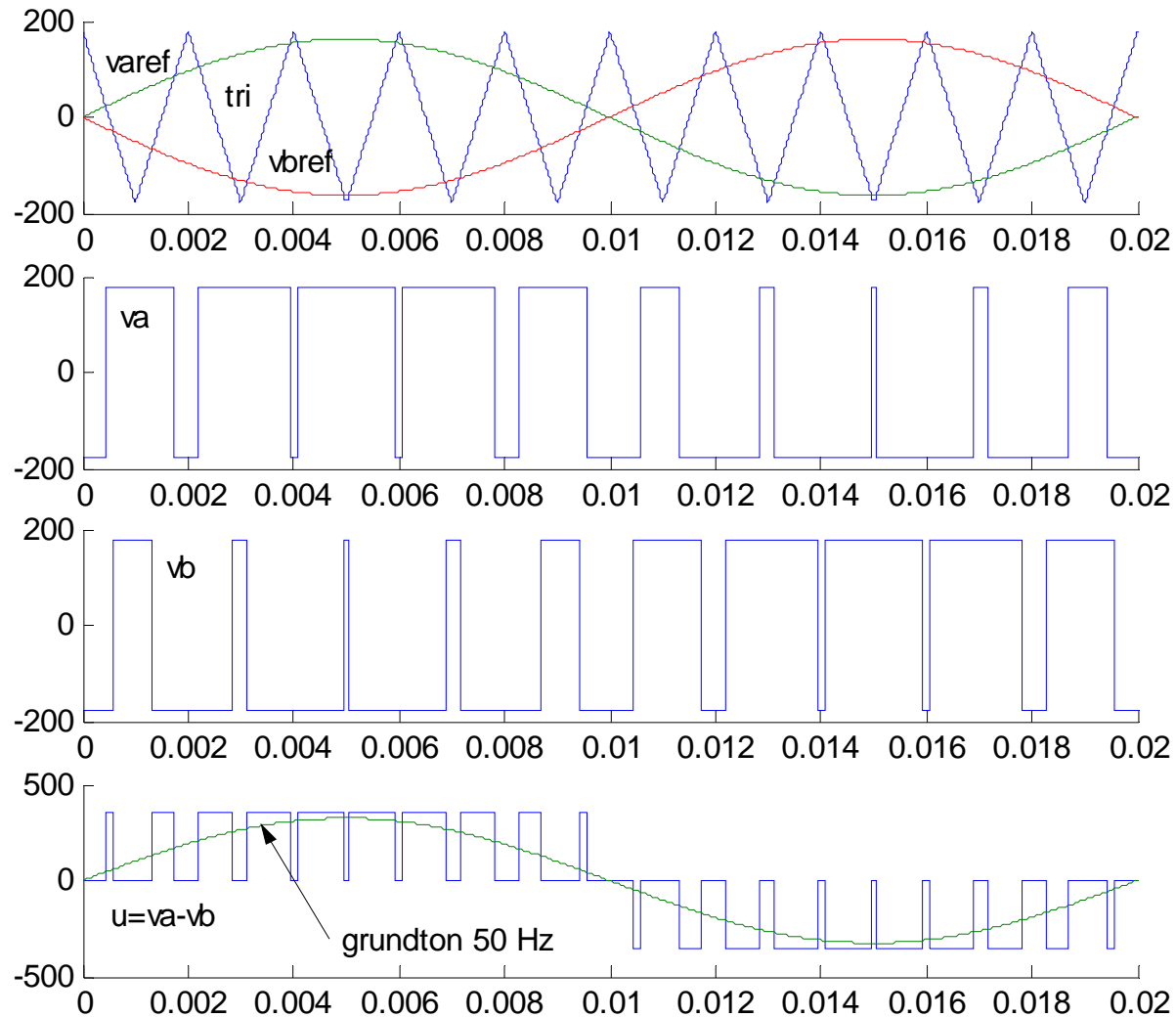


Class D Audio Amplifiers

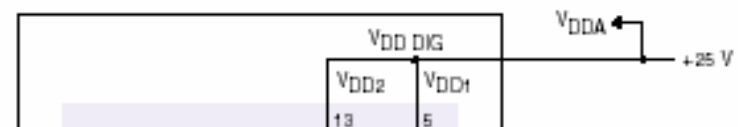


Features

- Power ranges from 20 to 150 W (up to 400 W with application support)
- Excellent power efficiency ($\leq 95\%$)
- Good EMC performance
- Excellent THD (0.01%)
- Symmetrical supply between 15 - 30 V
- Internal oscillator:
 - frequency adjustable between 200 and 600 kHz
 - can be overridden by an external clock (tracking option)
- Output stage protected against short circuit and overheating
- Simple SE and BTL applications
- Few external components
- Asymmetrical supply possible for BTL configurations (with application support)
- Powerpath ICs in Si17P and HSOP24 Power SMD package

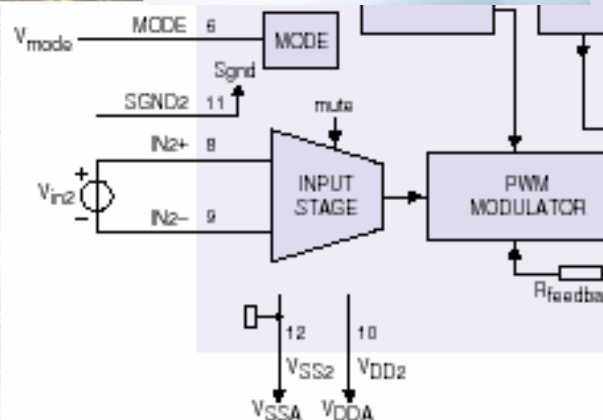


3-phase converter

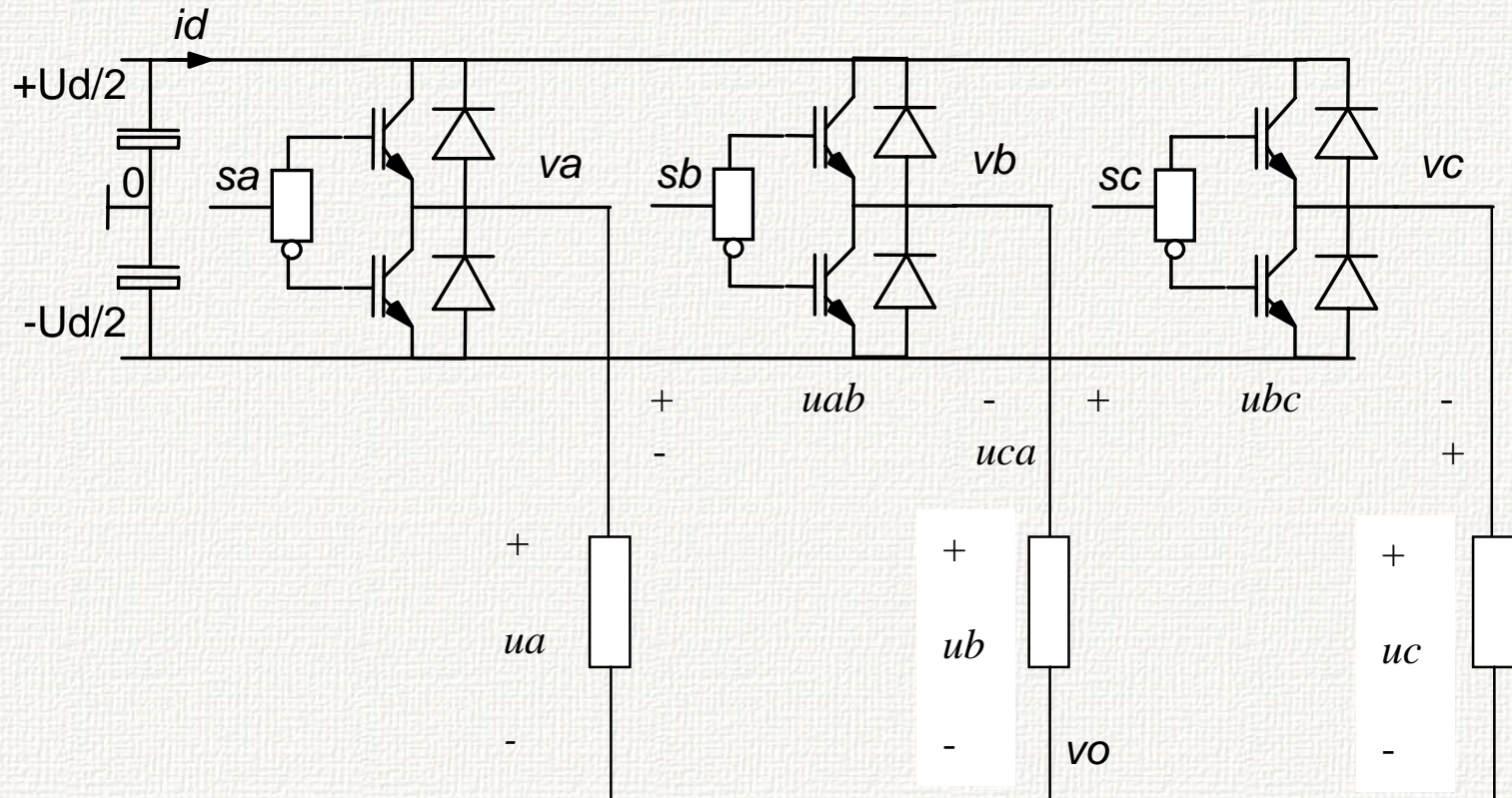

Drive circuits

- **All power transistors need a gate/base-driver to**
 - Switch between on- and off-state
 - Turn off at over current
 - Provide galvanic isolation to the control circuitry
- **Example of separate driver**
 - 600V and 1200V gate driver in a single IC for MOSFET and IGBTs
 - Multiple Configurations
 - Single high side
 - Half-bridge
 - 3 phase inverter driver
 - Up to +2.0/-2.0A output source/sink current enables fast switching
 - Integrated protection and feedback functions
 - Optional deadtime control
 - Tolerant to negative voltage transient
 - Up to 50V/ns dV/dt immunity
 - Optional soft turn-on
 - Uses low cost bootstrap power supply
 - CMOS and LSTTL input compatible

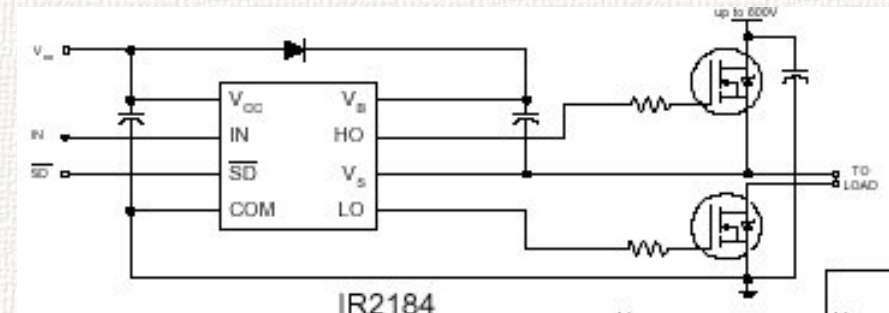



Fully integrated power semiconductors

International
IOR Rectifier

Bulletin I27147 01/03

PIIPM25P12B008
Programmable Isolated IPM

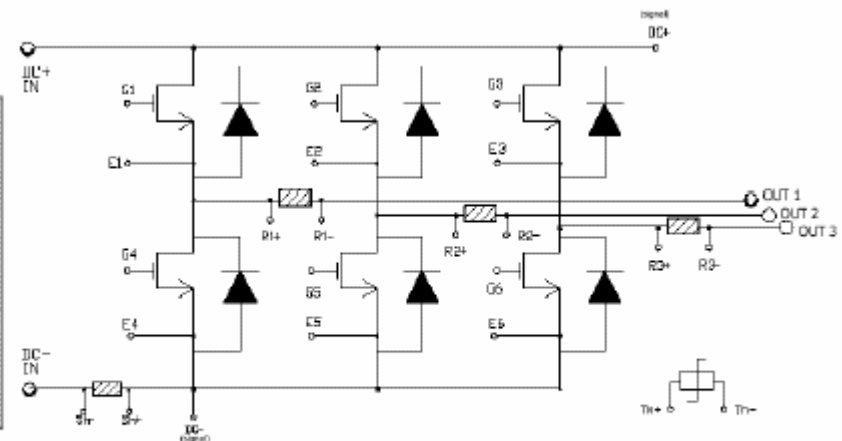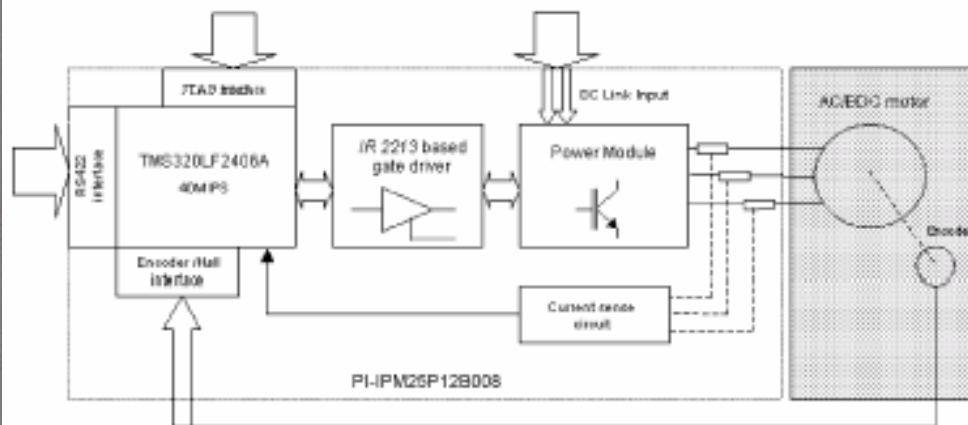- **Self-containing with built in:**
 - Drive circuit
 - Protection circuit
 - Galvanic isolation
 - Power transistor



Three phase inverter with current sensing resistors on all output phases and thermistor



Passive components

- Inductors
- Capacitors
- Heat sinks



Inductors

- Many types:
 - Ferrite type components
 - For SMPS transformers @ 100 kHz
 - Chokes & Coils & Inductors
 - For EMC suppression
 - Toroidal transformers
 - Laminated core transformers
 - Current transformers
 - Noise protection transformers
 - AC voltage stabilizers




Capacitors

- **Electrolytic**
 - For energy storage and filtering
- **Film**
 - For filtering
- **Must be selected with care, can be destroyed by:**
 - Harmonic currents
 - Over voltages
- **Most producers have software design tools available on their home page.**




Heat sinks

- **Extruded**

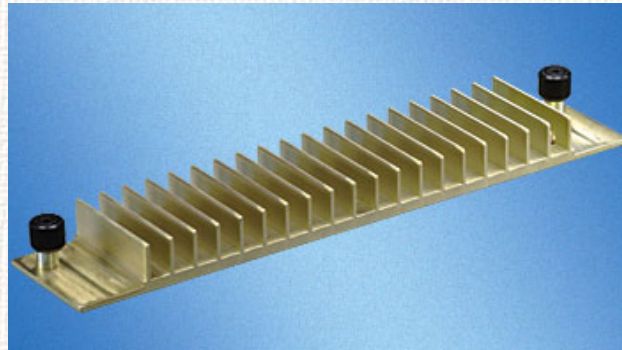


- **Stacked fin**

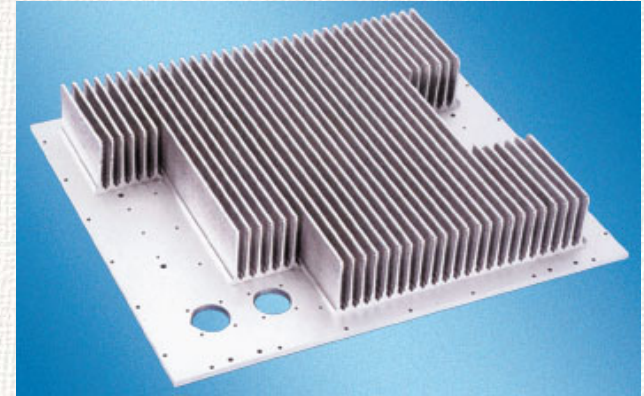

- **Water cooled**




- **Integrated in housing**

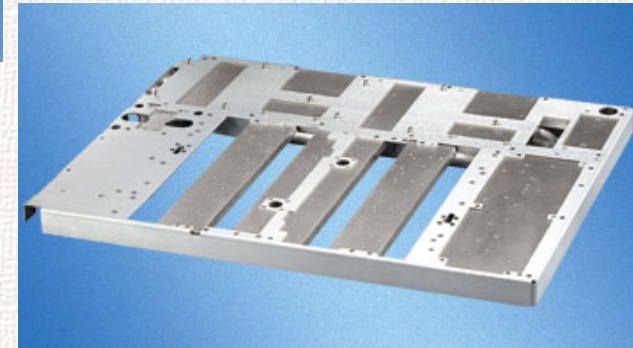


Power Electronic Design

- All circuits contain capacitive and inductive elements with switches in between.
- Non ideal components contribute to short circuit currents and over voltages that may harm/destroy the circuit.
- Example:

What should look like this:

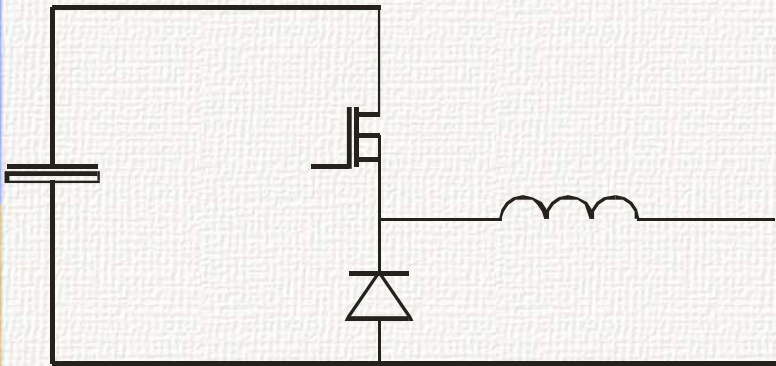

do instead look like this:

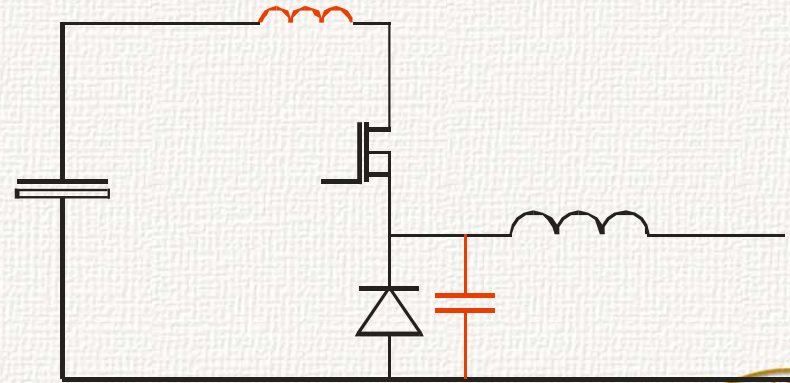


- Solution: - Minimize non ideal components and distances



How to improve a circuit

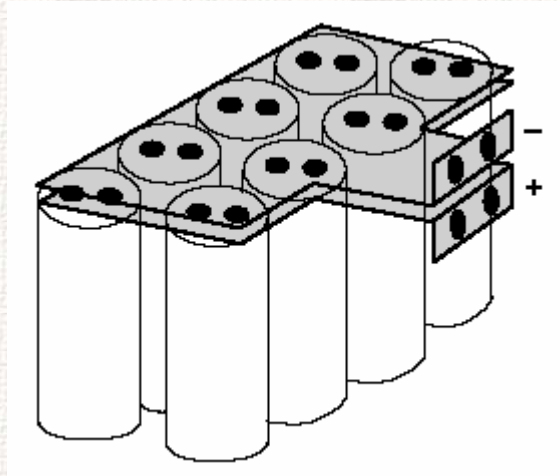- Minimize length of capacitive cables
- Example:



- Avoid capacitance in inductive circuits
 - Eg. keep primary and secondary winding of a transformer apart.



Integration of passive components

