




## Modulation

Industrial Electrical Engineering and Automation  
Lund University, Sweden



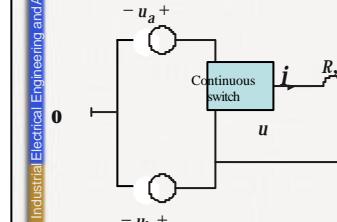**Why switching?**


- Continuous amplifiers have low efficiency



$p_{ut}(t) = u \cdot i$   
 $p_{in}(t) = (u_a - u_b) * i$   
 Antag:  
 $(u_a - u_b) = U_{dc}$   
 $P_{in} = U_{dc} \cdot i$   
 $h = \frac{P_{ut}}{P_{in}} = \frac{u \cdot i}{U_{dc} \cdot i} = \frac{u}{U_{dc}}$

© Mats Alaküla
L2 - modulation


**Switching amp. Losses**

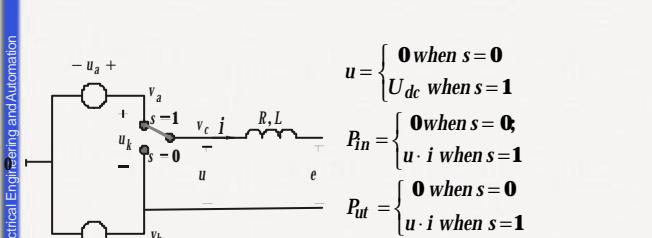

$u = \begin{cases} 0 & \text{when } s=0 \\ U_{dc} & \text{when } s=1 \end{cases}$   
 $P_{in} = \begin{cases} 0 & \text{when } s=0, \\ u \cdot i & \text{when } s=1 \end{cases}$   
 $P_{ut} = \begin{cases} 0 & \text{when } s=0 \\ u \cdot i & \text{when } s=1 \end{cases}$   
 $h = \frac{P_{ut}}{P_{in}} = \begin{cases} \text{undefined when } s=0, \\ 100\% & \text{when } s=1 \end{cases}$

© Mats Alaküla
L2 - modulation


**Converter topology**

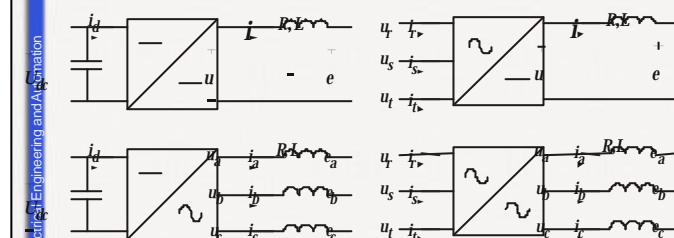

- 1 side capacitive
- 1 side inductive
- ALWAYS!

© Mats Alaküla
L2 - modulation
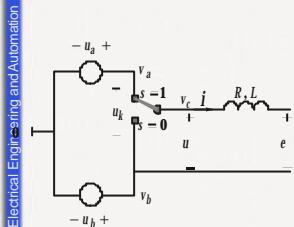
## Modulation - Control of voltage time area



$$v_c = \begin{cases} v_a & \text{when } s=1 \\ v_b & \text{when } s=0 \end{cases}$$


$$u = s \cdot (v_a - v_b) = s \cdot u_k = \begin{cases} u_k & \text{when } s=1 \\ 0 & \text{when } s=0 \end{cases}$$

© Mats Alaküla

L2 - modulation



## Output voltage

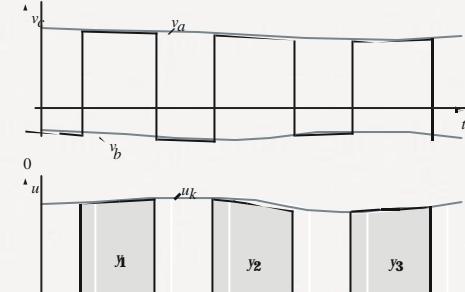


© Mats Alaküla

L2 - modulation


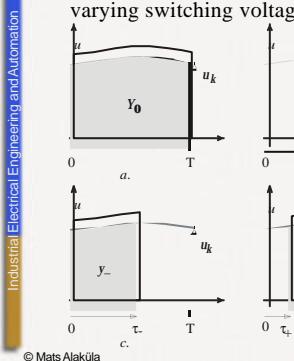
## Voltage control options

Assume a limited pulse interval  $T$  and a slowly varying switching voltage  $u_k$



$$Y_0 = \int_0^T u_k(t) \cdot dt$$

$$u_k(t_+) = -\frac{dy(t_+)}{dt_+}$$


$$u_k(t_-) = \frac{dy(t_-)}{dt_-}$$

© Mats Alaküla

L2 - modulation







## Control with positive flank




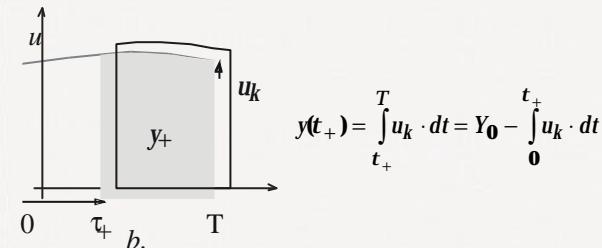


© Mats Alaküla

L2 - modulation



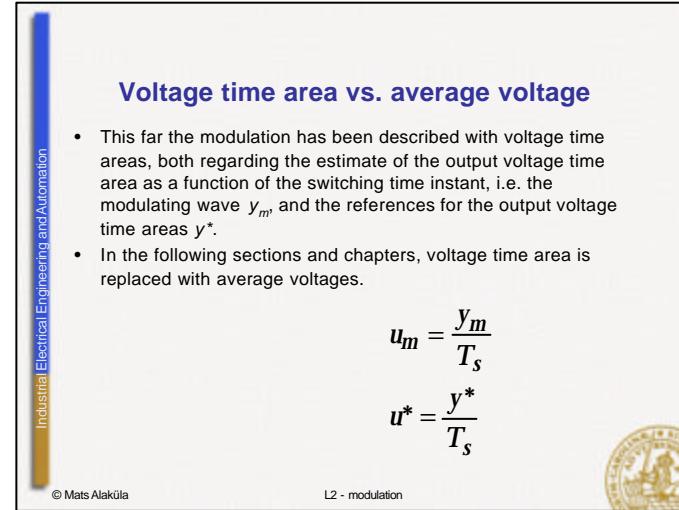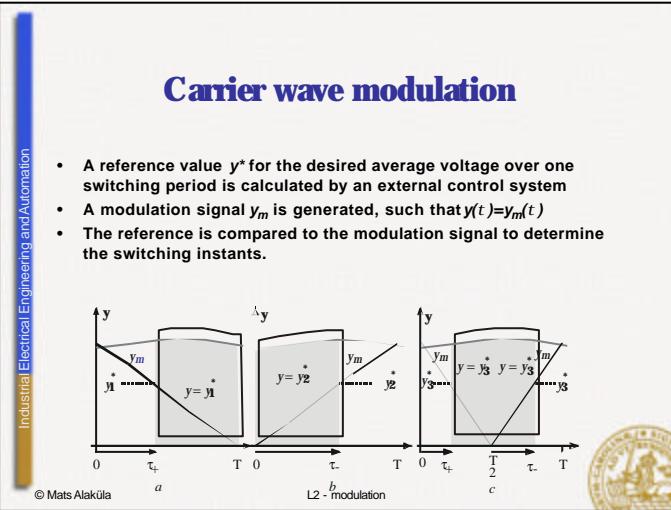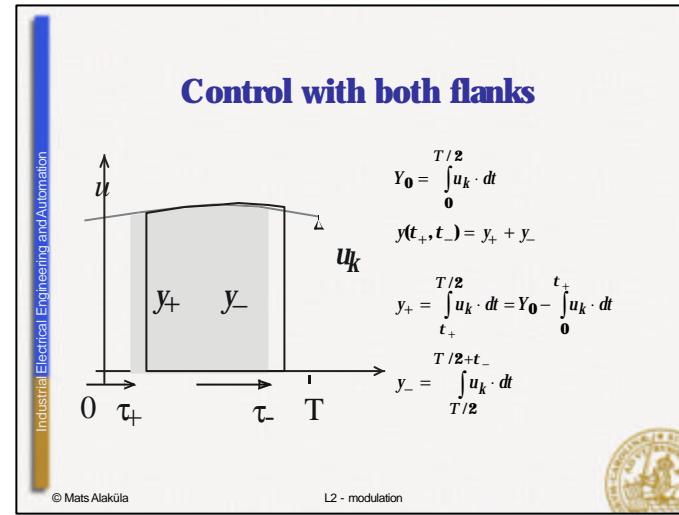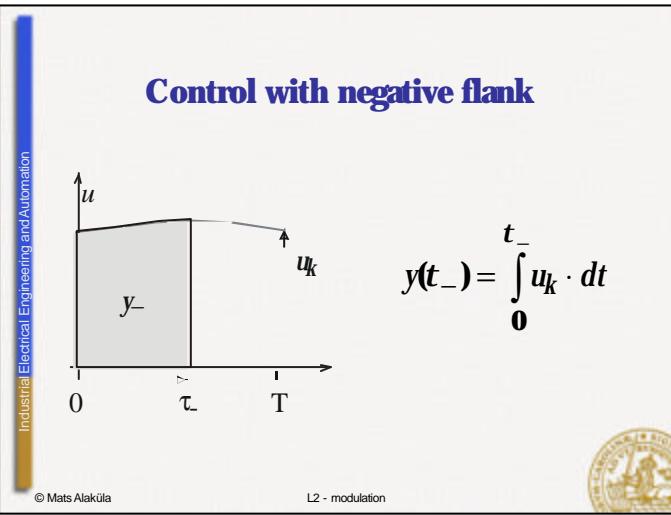


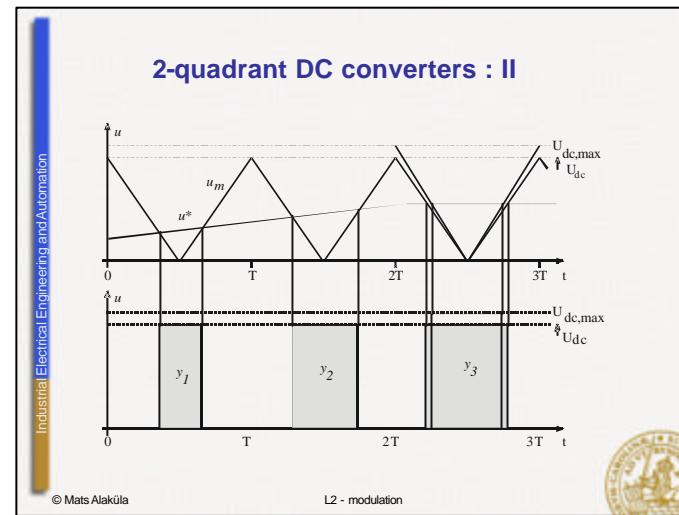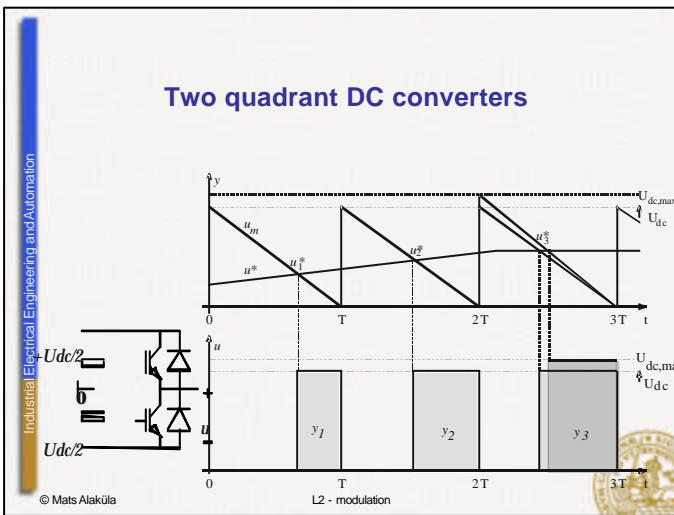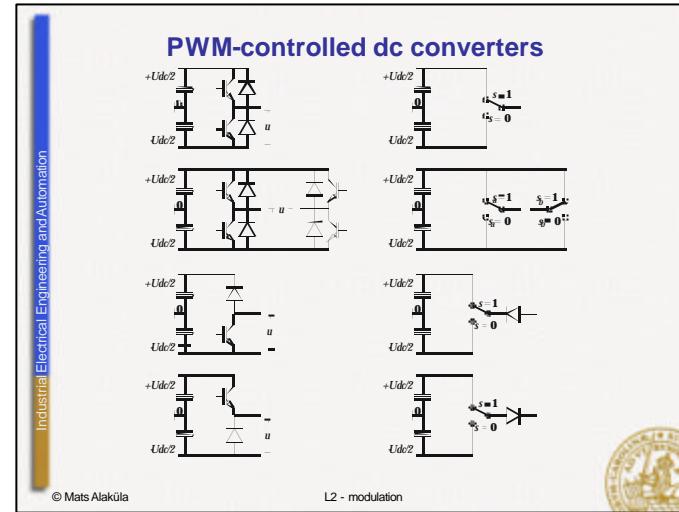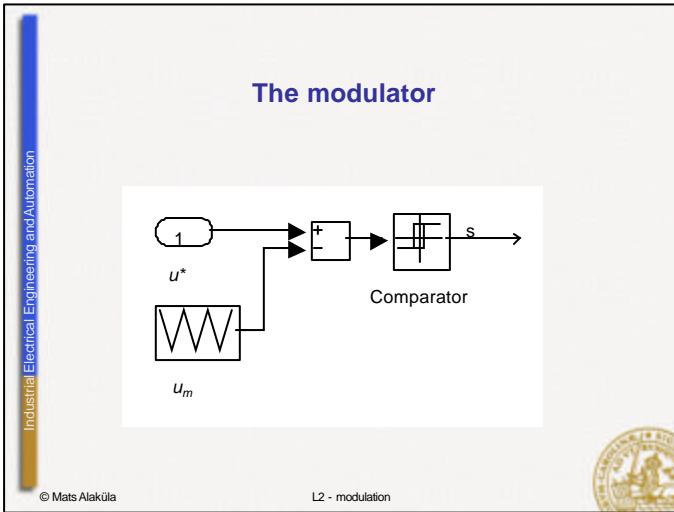

## 2-quadrant DC converters : III
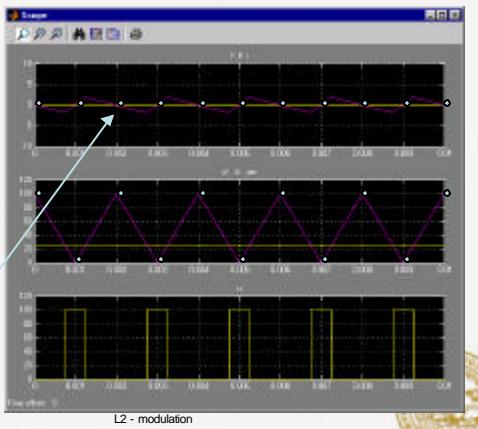
## Current sampling – how often?


- When the carrier turns,  
i.e. With twice  
the switching  
frequency!



© Mats Alaküla

## Example


- Sampling of current

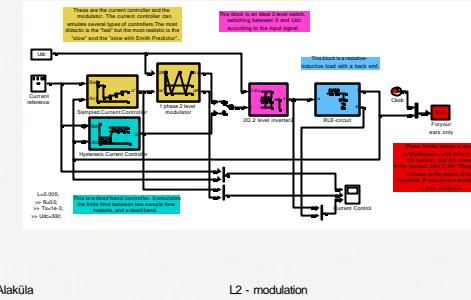

© Mats Alaküla

L2 - modulation

## 4 – quadrant DC converters

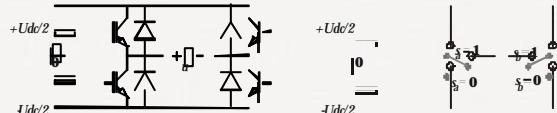

Bridge connected

2 phase potentials, only 1 output voltage = 1 degree of freedom to be used for other purposes.

© Mats Alaküla

## L2 - modulation

## 4-quadrant DC converters

$$u^* = v_a^* - v_b^*$$

$$alt1: v_a^* = sign(u^*) \cdot \frac{U_{dc}}{2} \Rightarrow v_b^* = v_a^* - u^* = sign(u^*) \cdot \frac{U_{dc}}{2} - u^*$$

$$\text{alt 2: } v_a^* = -v_b^* \Rightarrow v_a^* - v_b^* = 2 \cdot v_a^* \Rightarrow \begin{cases} v_a^* = \frac{u^*}{2} \\ v_b^* = -\frac{u^*}{2} \end{cases}$$

© Mats Alaküla

## L2 - modulation

