


Current Control with 2 and 4-quadrant converters

© Mats Alaküla

L3 – Current Control (DC)



Loops

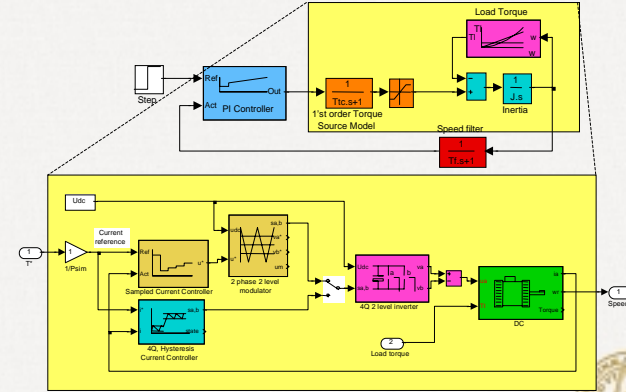


© Mats Alaküla

L3 – Current Control (DC)



So far

Modulation ...

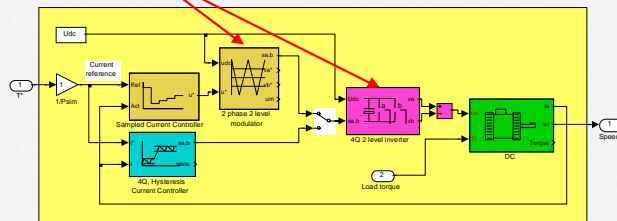

... or, how to convert a voltage reference into a pulse with modulated voltage


© Mats Alaküla

L3 – Current Control (DC)



Next step

Current control ...

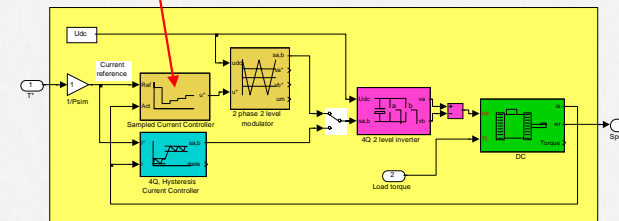

... or, how to convert a current reference into voltage references, or maybe a PWM pattern directly ...

© Mats Alaküla

L3 – Current Control (DC)




Problems and means to control current

- **Problem:**
 - Current dynamics are extremely fast
- **Means**
 - **Analogue controllers**
 - Fast, but prone to drift
 - Difficult to implement non linear control laws
 - **Digital controllers**
 - Not as fast, but exact
 - Easy to implement non linear control laws




Computer speed


Fast:

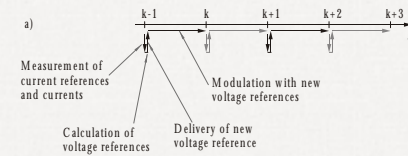


Slow:

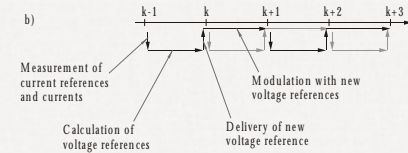

Continuous:

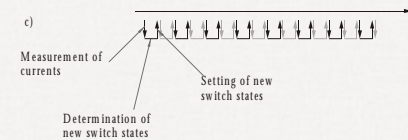

Generic Load

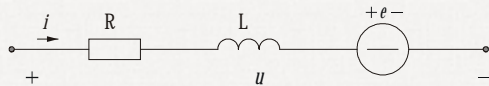

$$u = R \cdot i + L \cdot \frac{di}{dt} + e$$



Current controller with fast computer - I

$$\frac{\int_{kT_s}^{(k+1)T_s} u \cdot dt}{T_s} = \frac{R \cdot \int_{kT_s}^{(k+1)T_s} i \cdot dt + L \cdot \int_{kT_s}^{(k+1)T_s} \frac{di}{dt} \cdot dt + \int_{kT_s}^{(k+1)T_s} e \cdot dt}{T_s} = \bar{u}(k, k+1) = R \cdot \bar{i}(k, k+1) + L \cdot \frac{\bar{i}(k+1) - \bar{i}(k)}{T_s} + \bar{e}(k, k+1)$$

$$\bar{u}(k, k+1) = u^*(k) \quad (a)$$

$$\bar{i}(k+1) = i^*(k) \quad (b)$$

$$\bar{i}(k, k+1) = \frac{i^*(k) + \bar{i}(k)}{2} \quad (c)$$

$$\bar{e}(k, k+1) = \bar{e}(k) \quad (d)$$

$$\bar{i}(k) = \sum_{n=0}^{k-1} (i^*(n) - \bar{i}(n)) \quad (e)$$




Current Controller with a fast computer – II

$$\begin{aligned}
 u^*(k) &= R \cdot \frac{i^*(k) + \hat{i}(k)}{2} + L \cdot \frac{i^*(k) - \hat{i}(k)}{T_s} + e(k) = \\
 &= R \cdot \frac{i^*(k) - \hat{i}(k)}{2} + R \cdot \hat{i}(k) + L \cdot \frac{i^*(k) - \hat{i}(k)}{T_s} + e(k) = \\
 &= \left(\frac{L}{T_s} + \frac{R}{2} \right) (i^*(k) - \hat{i}(k)) + R \cdot \sum_{n=0}^{n=k-1} (i^*(n) - \hat{i}(n)) + e(k) = \\
 &= \left(\frac{L}{T_s} + \frac{R}{2} \right) \cdot \left(\underbrace{i^*(k) - \hat{i}(k)}_{\text{Pr optional}} + \underbrace{\frac{T_s}{R + \frac{T_s}{2}} \cdot \sum_{n=0}^{n=k-1} (i^*(n) - \hat{i}(n))}_{\text{Integral}} \right) + \underbrace{e(k)}_{\text{Feed forward}}
 \end{aligned}$$



Compensation for a slow computer - the Smith predictor

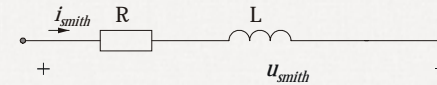- Use a "dummy" system that simulates the current response to voltage references.
- Let the dummy system be purely Resistive-Inductive, i.e. NO EMF!



$$u = R \cdot i_{smith} + L \cdot \frac{di_{smith}}{dt}$$



The Smith Predictor : II

- The SP will have the same dynamics as the real system, but not the same statics.

$$\begin{aligned}
 i_{smith,static} &= \frac{u}{R} & i_{real,static} &= \frac{u - e}{R} \\
 \frac{di_{smith}}{dt} &= \frac{u - R \cdot i_{smith}}{L} & \frac{di_{real}}{dt} &= \frac{u - e - R \cdot i_{smith}}{L}
 \end{aligned}$$

- Think like this:
 - Assume stationarity -> nominator of the current derivative = 0
 - A voltage (u) change gives the same derivative in both cases.



The Smith Predictor : III


- Calculate the current of the next sampling instant as the sum of:
 - The current measured at the last sampling instant
 - The change of the current based on the voltage reference at the last sampling instant.

$$\begin{aligned}
 \hat{i}(k) &= i(k-1) + \Delta i_{smith}(k) \\
 \Delta i_{smith}(k) &= i_{smith}(k) - i_{smith}(k-1) \\
 u^*(k-1) &\approx R \cdot i_{smith}(k-1) + L \cdot \frac{i_{smith}(k) - i_{smith}(k-1)}{T_s} \\
 i_{smith}(k) - i_{smith}(k-1) &= u^*(k-1) \cdot \frac{T_s}{L} - R \cdot i_{smith}(k-1) \cdot \frac{T_s}{L} \\
 i_{smith}(k) &= u^*(k-1) \cdot \frac{T_s}{L} + \left(1 - R \cdot \frac{T_s}{L} \right) \cdot i_{smith}(k-1)
 \end{aligned}$$



The Smith Predictor : IV
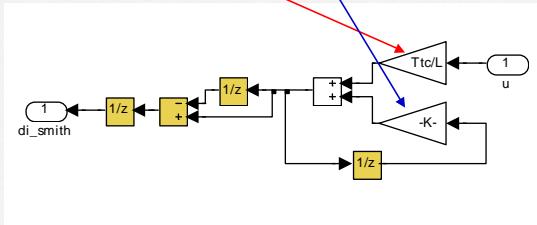
$$i_{smith}(k) = u^*(k-1) \cdot \frac{T_s}{L} + \left(1 - R \cdot \frac{T_s}{L}\right) \cdot i_{smith}(k-1)$$



© Mats Alaküla

L3 – Current Control (DC)


Current Control with a slow computer – II

$$u^*(k) = \left(\frac{L}{T_s} + \frac{R}{2}\right) \cdot \left(i^*(k) - \hat{i}(k) \right) + \frac{T_s}{\left(\frac{L}{R} + \frac{T_s}{2}\right)} \cdot \sum_{n=0}^{k-1} \left(i^*(n) - \hat{i}(n) \right) + \hat{e}(k)$$

© Mats Alaküla

L3 – Current Control (DC)

Example – 2-quadrant

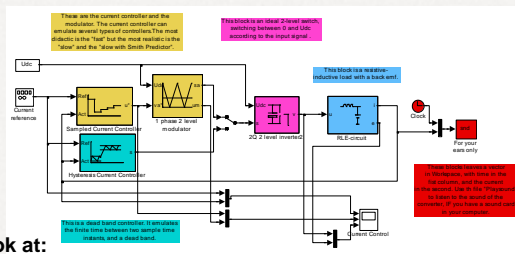


- Look at:
 - Step response fast computer
 - Step response slow computer (with "fast" parameters)
 - Step response adjusted parameters
 - Step response with the Smith Predictor
- Parameter sensitivity

© Mats Alaküla

L3 – Current Control (DC)

Current control with a 4-quadrant converter

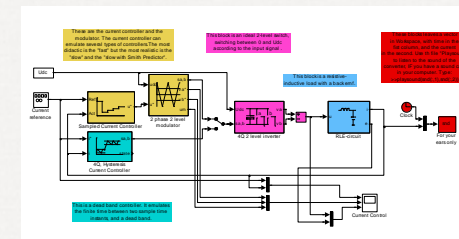- Basically the same situation as with 2-quadrant, BUT negative voltage references are allowed since the amplifier can provide them to the load.



© Mats Alaküla

L3 – Current Control (DC)


Direct Current Control

- Switch state only a function of current error
- No intermediate current control or modulation




2-Quadrant Direct Current Controller
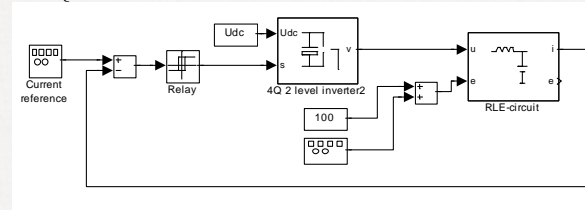
$$s = \begin{cases} 1 & \text{if } i < i^* - \frac{\Delta i}{2} \\ -1 & \text{if } i > i^* + \frac{\Delta i}{2} \\ s & \text{if } i^* - \frac{\Delta i}{2} < i < i^* + \frac{\Delta i}{2} \end{cases}$$




Example

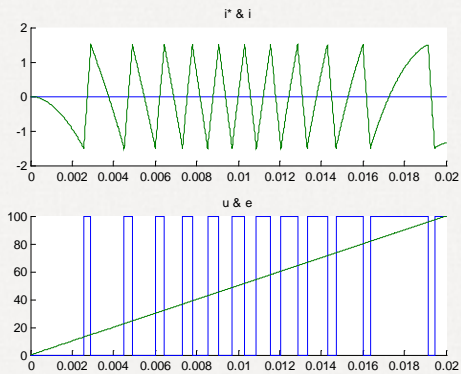

4-Quadrant Direct Current Controller

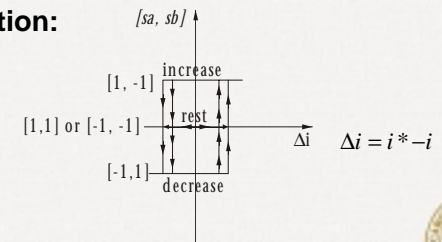- More tricky:
 - 4 states ([-1,-1] , [1,1] , [1,-1] & [-1,1]), but
 - Only 3 output voltages (-Udc, 0, Udc)
- One solution:



Example

