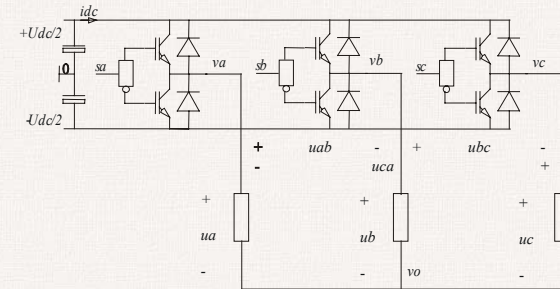


Modulation of 3-phase converters

Industrial Electrical Engineering and Automation
Lund University, Sweden



3 – phase converters




- In AC motor drives
- In grid connected converters

© Mats Alaküla

L5 – 3-phase modulation




The generic 3-phase load

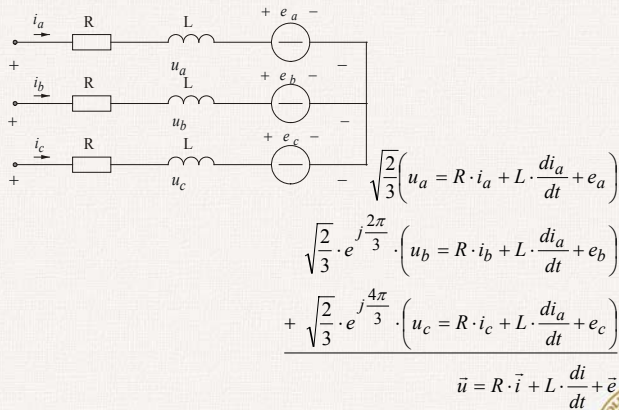


© Mats Alaküla

L5 – 3-phase modulation

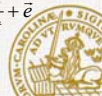

Vectors in 3-phase systems

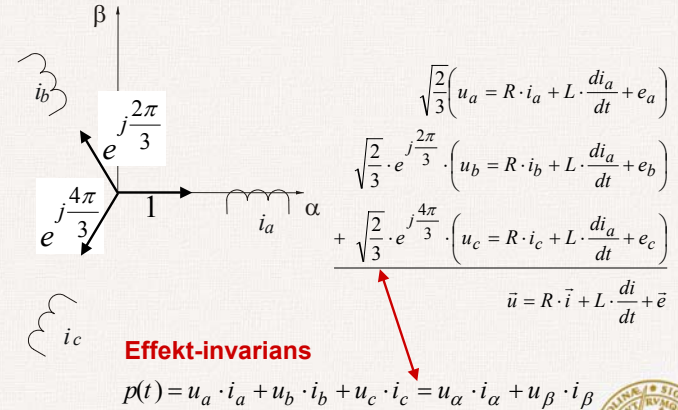

Effekt-invariants


$$p(t) = u_a \cdot i_a + u_b \cdot i_b + u_c \cdot i_c = u_\alpha \cdot i_\alpha + u_\beta \cdot i_\beta$$

© Mats Alaküla

L5 – 3-phase modulation



Symmetric emf

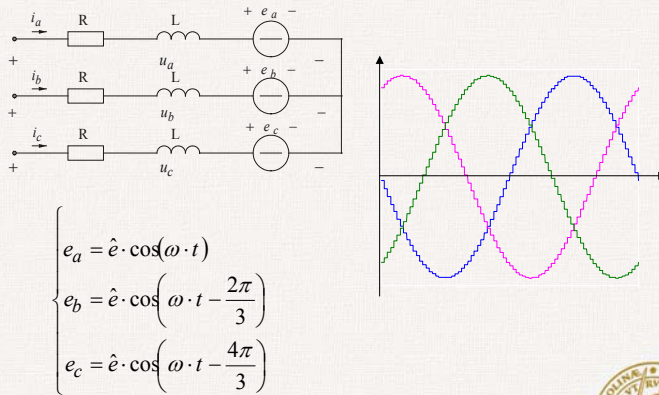

Example, grid voltage vector


$$\begin{aligned} \vec{e} &= \sqrt{\frac{2}{3}} \cdot \left(e_a + e_b \cdot e^{j\frac{2\pi}{3}} + e_c \cdot e^{j\frac{4\pi}{3}} \right) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left(\cos(\omega \cdot t) + \cos\left(\omega \cdot t - \frac{2\pi}{3}\right) \cdot \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) + \cos\left(\omega \cdot t - \frac{4\pi}{3}\right) \cdot \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \right) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left(\cos(\omega \cdot t) + \left(\cos(\omega \cdot t) \cdot \cos\left(\frac{2\pi}{3}\right) + \sin(\omega \cdot t) \cdot \sin\left(\frac{2\pi}{3}\right) \right) \cdot \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) + \right. \\ &\quad \left. + \left(\cos(\omega \cdot t) \cdot \cos\left(\frac{4\pi}{3}\right) + \sin(\omega \cdot t) \cdot \sin\left(\frac{4\pi}{3}\right) \right) \cdot \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \right) = \\ &= \sqrt{\frac{2}{3}} \cdot \hat{e} \cdot \left(\cos(\omega \cdot t) \cdot \left(1 + \frac{1}{4} + \frac{1}{4}\right) + j \cdot \sin(\omega \cdot t) \cdot \left(\frac{3}{4} + \frac{3}{4}\right) \right) = \\ &= \sqrt{\frac{3}{2}} \cdot \hat{e} \cdot (\cos(\omega \cdot t) + j \cdot \sin(\omega \cdot t)) = \boxed{E \cdot e^{j\omega t}} \end{aligned}$$



Rotating reference frame

Use the integral of
The grid back emf
vector:
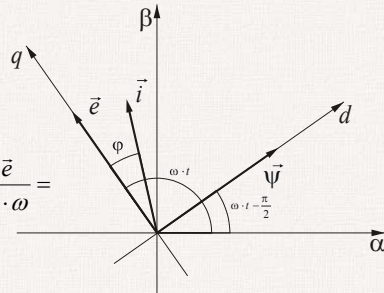
$$\begin{aligned} \vec{\psi} &= \int_0^t \vec{e} \cdot dt = \int_0^t E \cdot e^{j\omega \cdot t} dt = \frac{\vec{e}}{j \cdot \omega} = \\ &= \frac{E}{\omega} e^{j\left(\omega \cdot t - \frac{\pi}{2}\right)} \end{aligned}$$



Voltage equation in the (d,q)-frame

$$\vec{u} = R \cdot \vec{i} + L \cdot \frac{d\vec{i}}{dt} + j \cdot \omega \cdot L \cdot \vec{i} + \vec{e}$$



Active power ...

$$\vec{u} = R \cdot \vec{i} + L \cdot \frac{d\vec{i}}{dt} + j \cdot \omega \cdot L \cdot \vec{i} + \vec{e}$$

$$p(t) = \text{Re}\{\vec{u} \cdot \vec{i}^*\} = \text{Re}\left\{R \cdot \vec{i} \cdot \vec{i}^* + L \cdot \frac{d\vec{i}}{dt} \cdot \vec{i}^* + j \cdot \omega \cdot L \cdot \vec{i} \cdot \vec{i}^* + \vec{e} \cdot \vec{i}^*\right\} =$$

$$= \underbrace{Ri_d^2 + Ri_q^2}_1 + \underbrace{L \frac{di_d}{dt} i_d + L \frac{di_q}{dt} i_q}_2 + \underbrace{e_q i_q}_3$$


Resistive losses Energizing inductances Power absorbed by the grid back emf

Stationarity:

$$p(t) = E \cdot \sqrt{\frac{3}{2}} \cdot |\vec{i}| \cdot \cos(\varphi) = \sqrt{3} \cdot E \cdot I_{rms, phase} \cdot \cos(\varphi)$$



3-phase converters – 8 switch states

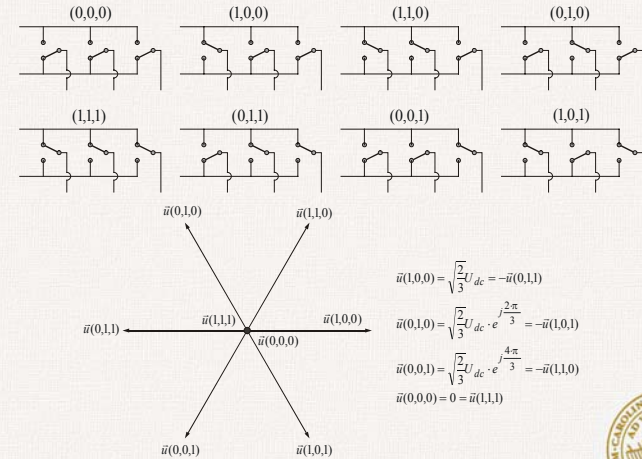

3-phase converters - sinusoidal references

$$\vec{u}^* = u^* \cdot e^{j\omega t} = u^* \cdot (\cos(\omega t) + j \cdot \sin(\omega t)) = u_\alpha^* + j \cdot u_\beta^*$$

$$u_a^* = \sqrt{\frac{2}{3}} u_\alpha^*$$

$$u_b^* = \frac{1}{\sqrt{2}} u_\beta^* - \frac{1}{\sqrt{6}} u_\alpha^*$$

$$u_c^* = -\frac{1}{\sqrt{2}} u_\beta^* - \frac{1}{\sqrt{6}} u_\alpha^*$$

$$u_a^* = \sqrt{\frac{2}{3}} \cdot u^* \cos(\omega t)$$


$$u_b^* = \sqrt{\frac{2}{3}} \cdot u^* \cos(\omega t - \frac{2\pi}{3})$$

$$u_c^* = \sqrt{\frac{2}{3}} \cdot u^* \cos(\omega t - \frac{4\pi}{3})$$



3-phase converters modulation

Simplest with sinusoidal references...

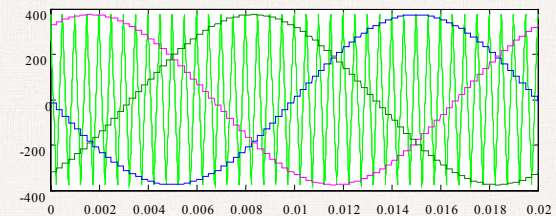

... but the DC link voltage is badly utilized.



3-phase converters – symmetrization


3 phase potentials, only 2 vector components. One degree of freedom to be used for other purposes.

$$\begin{aligned} v_{az}^* &= u_a^* - v_z^* \\ v_{bz}^* &= u_b^* - v_z^* \\ v_{cz}^* &= u_c^* - v_z^* \end{aligned}$$



3-phase symmetrized modulation
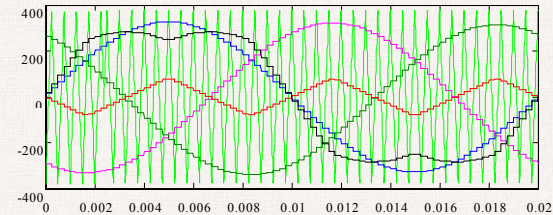
$$v_z^* = \frac{\max(u_a^*, u_b^*, u_c^*) + \min(u_a^*, u_b^*, u_c^*)}{2}$$




Maximum phase voltage with sinusoidal modulation : $U_{dc}/2$

Maximum phase-to phase voltage with symmetrized modulation : $U_{dc} \rightarrow$ Phase voltage $U_{dc}/\sqrt{3}$, i.e. $2/\sqrt{3} \approx 1.15$ times larger than with sinusoidal modulation.



3-phase minimum switching modulation


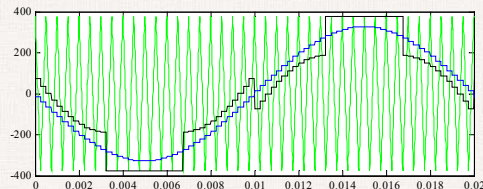
$$v_z^* = -\min\left(\frac{U_{dc}}{2} - \max(u_a^*, u_b^*, u_c^*), \frac{U_{dc}}{2} - \min(u_a^*, u_b^*, u_c^*)\right)$$




One phase is not switching for 2 60 degree intervals ...



Modulation sequence vs. ripple

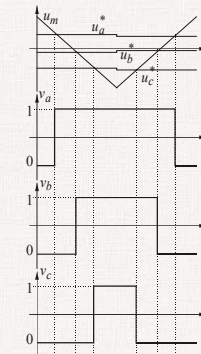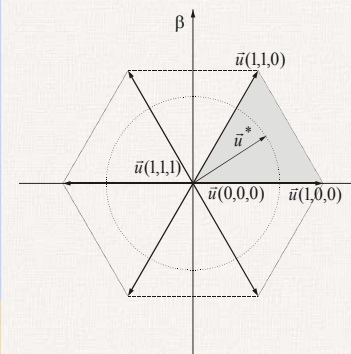

Modulation sequence vs. ripple

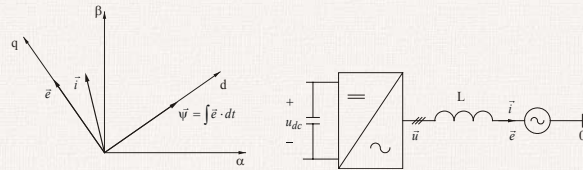

$$\frac{d\vec{i}}{dt} = \frac{\vec{u} - \vec{e}}{L}$$

Current ripple in the (d,q)-frame

